

Université d'Ottawa  
Faculté de génie

École d'ingénierie et de technologie de  
l'information



uOttawa

L'Université canadienne  
Canada's university

University of Ottawa  
Faculty of Engineering

School of Information Technology and  
Engineering

**ELG3336**  
Electronics for Mechanical Engineering

**MIDTERM EXAMINATION**

**Length of Examination: 90 minutes**

**October, 2016**

**Professor: Riadh Habash**

**Page 1 of 7**

Family Name: \_\_\_\_\_

Other Names: \_\_\_\_\_

Student Number: \_\_\_\_\_

Signature \_\_\_\_\_

Closed book.

If you do not understand a question, clearly state an assumption and proceed.

At the end of the exam, when time is up:


- Stop working and turn your exam upside down.
- Remain silent.
- Do not move or speak until all exams have been picked up, and a TA or the Professor gives the go-ahead to leave.

**QUESTION 1 (5 marks):**

**Follow the procedure of solution, answer questions, identify mistakes (circle) and correct them, if any!**


Consider the small-signal amplifier shown in Figure 1. Assume  $V_{CC} = 24\text{ V}$ ,  $R_S = 1.5\text{ k}\Omega$ ,  $R_1 = 8.6\text{ k}\Omega$ ,  $R_2 = 200\text{ k}\Omega$ ,  $R_C = 5\text{ k}\Omega$ ,  $R_L = 2\text{ k}\Omega$ ,  $\beta = 75$ , and  $\pi = 750\ \Omega$ .

- Draw the DC bias circuit and prove that the BJT operates in the active region.
- Draw the small-signal equivalent circuit and find the voltage gain of the amplifier.

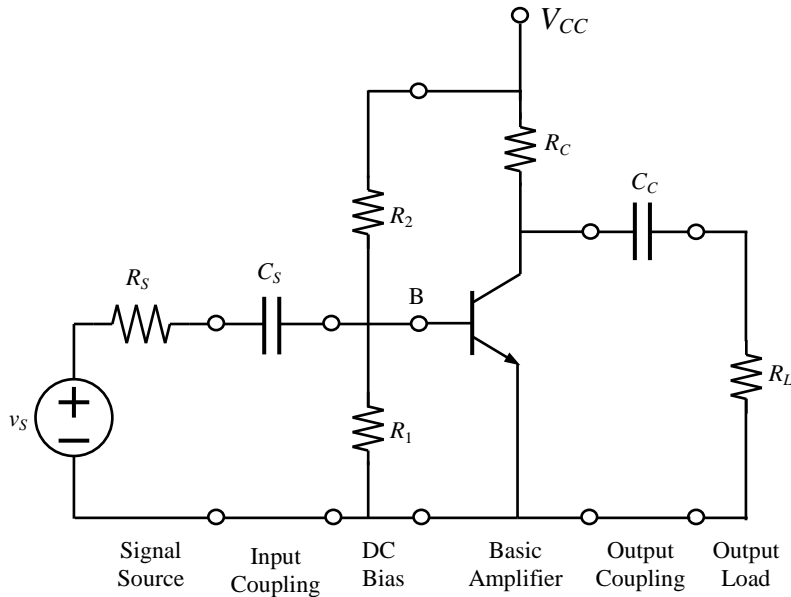

**Figure 1** A stage of an amplifier circuit.

**Solution:**

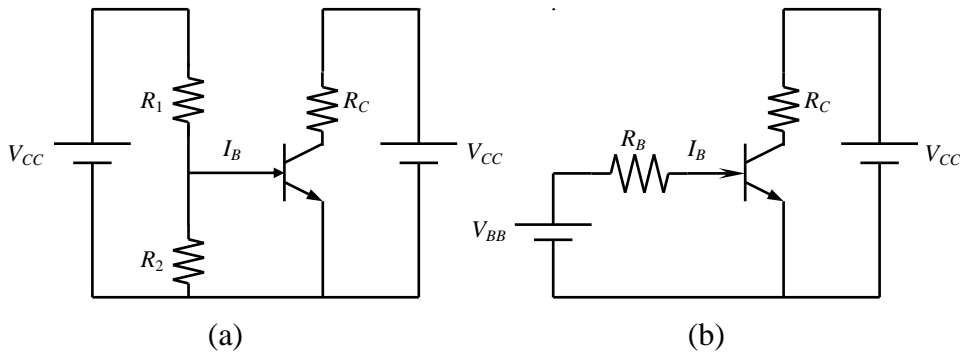

**Figure 2** (a) DC bias circuit. (b) Equivalent of the input portion.

**Step One: The DC analysis**

The open-circuit base DC bias voltage is

	$V_{BB} = 24 \times \frac{8.6}{8.6 + 200} = -1.99\text{ V}$
--	---

The DC output impedance of the bias network is

	$R_B = 8.6/200 = 8.25 \text{ k}\Omega$	
--	--	--

A silicon transistor requires a threshold voltage of  $V_{BE} = 0.7 \text{ V}$  to turn ON the base-emitter junction, therefore

	$I_B = \frac{V_{BB} - 0.7}{R_B} = \frac{0.99 - 0.7}{8.25 \text{ k}\Omega} = 35.1 \text{ A}$	
	$I_C = \beta I_B = 75 \times 35.1 \times 10^{-6} = 2.63 \text{ A}$	

Now consider the closed loop path in the output circuit of the amplifier and apply KVL in order to find the collector-emitter voltage  $V_{CE}$ .

	$-V_{CC} + I_C R_C + V_{CE} = 0$	
	$V_{CE} = 24 - 5 \times 2.63 = 10.8 \text{ V}$	

Therefore, the BJT is operating in the saturation region.

### Step Two: AC Analysis

Draw the Small-signal circuit of the BJT amplifier (1 mark).


**Figure 4** Small-signal circuit of the BJT amplifier.

Consider the circuit in stage one, first.

- Let us find the equivalent resistance of the four resistors: 1.5, 200, 8.6, and 0.75

$\frac{1}{R_T} = \frac{1}{1.5} + \frac{1}{200} + \frac{1}{8.6} + \frac{1}{0.75}$
$R_T = 0.472 \Omega$

Stage one circuit will turn into the following circuit

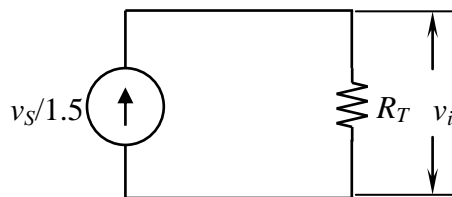

**Figure 4:** Equivalent circuit of stage-one circuit.

$$v_i = \frac{v_S}{1.5} \times R_T = 0.314 v_S$$

This value of  $v_i$  is same across each element in the circuit of Figure 3. Now, apply ohm's law to find  $i_b$

$$i_b = \frac{v_i}{r_\pi} = \frac{0.314 v_S}{0.75} = 0.416 v_S$$

Now, consider stage two circuit

$$v_{out} = -75 i_b \times (2/5) = -75 \times 0.416 v_S \times 1.42 = 446 v_S$$

Accordingly, the gain is  $v_{out}/v_S = 446$ .

### QUESTION 2 (2 marks)

A safety system shown has three inputs. If two or more of these are 1 at the same time, an alarm should sound. Draw a figure for the system; give its truth table; give its Boolean function; simplify the results; and draw the logic circuit to perform the alarm using NAND gates only.

**QUESTION 3 (3 marks)**

Design and draw a DC power supply that provides a nominal DC voltage of 5 V and be able to supply a load current  $I_{\text{load}}$  as large as 25 mA; that is  $R_{\text{load}}$  can be as low as 200  $\Omega$ . The power supply is fed from a 120-V (rms) 60 Hz AC line. Assume the availability of a 5.1-V zener diode having  $r_z = 10 \Omega$  at  $I_z = 20$  mA (and use  $V_{z0} = 4.9$  V), and that the required minimum current through the zener diode is  $I_{z\text{min}} = 5$  mA.