

Université d'Ottawa
Faculté de génie

École de science informatique
et de génie électrique



uOttawa

L'Université canadienne
Canada's university

University of Ottawa
Faculty of Engineering

School of Electrical Engineering
and Computer Science

ELG4157 Modern Control Engineering: Midterm 1 February 13, 2018

Name:

Number:

You are given an inductor, $L =$ mH, a capacitor, $C =$ mF, and a resistance, $R =$ Ω , a diode switch with PWM duty cycle of % to design and implement a Buck DC to DC converter.

Q1/2 Draw the circuit diagram of the buck converter with idealized waveform and the related equivalent circuits.

Q2/1 Write the differential equations of the Buck converter.

Q3/2 Model the Buck converter in the state variable form by averaging.

Q4/1

Obtain the transfer function of the system in the frequency domain.

Q5/2

Design the state feedback gains to obtain OS of () and settling time of ().

Q6/2 Realize and draw the state feedback gains as estimated from Q5.