

Short introduction to VHDL for Max+plus II

Daniel Amyot
damyot@site.uottawa.ca

VHDL

- Very High Speed Integrated Circuit (VHSIC) Hardware Description Language
- IEEE Std. 1076 (-1998, -1993, ...)
 - Description and analysis of logic circuits
- IEEE Std. 1164
 - Multivalued logic
 - 9 are defined (0, 1, X, high impedance, ...)
 - Used in VHDL for the logic variables

Why VHDL?

- Description (systems and components)
- Simulation and analysis
- Synthesis of circuits
- Implementation
- We will concentrate on the first 2 aspects.

Temporal and Functional Analysis

- Temporal Analysis
 - Takes into account delays (see assignment 1)
- Functional Analysis
 - Logical aspects only
 - No delays

Example: adder (assignment 1)

```
-- Realisation of  $S(X,Y) = XY' + X'Y$  and  $C(X,Y) = XY$ 

LIBRARY ieee;
USE ieee.std_logic_1164.all;


-- Inout/output function variables
ENTITY adder IS
    PORT(X, Y      : IN  STD_LOGIC; -- Inputs
          S, C      : OUT STD_LOGIC); -- Outputs
END adder ;

-- Outputs as function of inputs
ARCHITECTURE logic OF adder IS
BEGIN
    S <= (X AND (NOT Y)) OR ((NOT X) AND Y);
    C <= X AND Y;
END logic;
```


Operators and constants

- Supported core operators
 - NOT
 - AND
 - OR
 - XOR
 - XNOR
 - NAND
 - NOR
- Constants
 - '1'
 - '0'

Temporal Analysis (with delays)

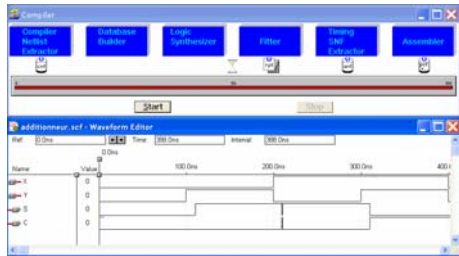

Generation of truth tables

 

Truth Table (placed in file .tbl) - Temporal Analysis


%	X	Y	S	C	%
0.0>	0	0	=	0	0
100.0>	0	1	=	0	0
110.4>	0	1	=	1	0
200.0>	1	0	=	1	0
209.9>	1	0	=	0	1
210.4>	1	0	=	1	0
300.0>	1	1	=	1	0
310.4>	1	1	=	0	1
400.0>	0	0	=	0	1

- Note
 - Change happens after the delay, but not when X and Y changes...
 - Similar combinations of X and Y leads to different outputs!
 - Some tables generated are difficult to understand
- Need to preserve the time interval necessary for verifying all combinations
- Put X and Y in order!

Looking into functional analysis...



Temporal Analysis (without delays)

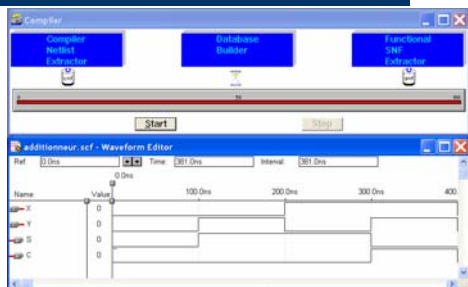

Truth Table (placed in file .tbl) - Functional Analysis

%	X	Y	S	C	%
0.0>	0	0	=	0	0
100.0>	0	1	=	1	0
200.0>	1	0	=	1	0
300.0>	1	1	=	0	1
400.0>	0	0	=	0	0
500.0>	0	1	=	1	0
600.0>	1	0	=	1	0
700.0>	1	1	=	0	1
800.0>	0	0	=	0	0
900.0>	0	1	=	1	0
1000.0>	X	X	=	X	X

- Only the combinations from 0.0 to 300.0 are necessary
 - 2 variables, 100 ns are necessary
 - For assignment # 2?