

REGISTER

A SEQUENTIAL CIRCUIT WHICH CONSISTS OF A GROUP OF FF'S AND (POSSIBLY) EXTERNAL GATES CONTROLLING THE FF INPUTS


WHERE

FF'S HOLD BINARY INFO AND



EXTERNAL GATES CONTROL WHEN & HOW NEW BINARY INFO IS PUT INTO FF'S

- * (THE CONTENT OF A REGISTER = WORD = BIT STREAM STORED IN FF'S)
- * (THE LENGTH OF A REGISTER = WORD LENGTH = # OF FF'S IN A REGISTER)
- * ALL REGISTERS (EXCEPT GATED LATCHES) ARE BUILT BY USING FF'S THAT ARE SENSITIVE TO PULSE TRANSITION RATHER THAN TO PULSE DURATION

(A) Pulse Duration

 

(B) Pulse Transition

  

Basic clocking methods and symbols: (a) a level-sensitive latch; (b) a positive edge-triggered flip-flop; (c) a negative edge-triggered flip-flop.

* THE TRANSFER OF NEW BINARY INFO INTO A REGISTER IS CALLED LOADING

126

* **SERIAL LOAD (TRANSFER IN SERIAL MODE)**

TRANSFER OF NEW BINARY INFO INTO A REGISTER BIT BY BIT

(# OF CLOCK PULSES NEEDED TO LOAD THE REGISTER = # OF FF'S IN THE REGISTER)

e.g., Let A and B be two n-bit registers

$A_n \dots A_2 A_1$

$B_n \dots B_2 B_1$

1 bit / pulse

* **PARALLEL LOAD (TRANSFER IN PARALLEL MODE)**

TRANSFER OF NEW BINARY INFO INTO A REGISTER AS A WHOLE WORD

(# OF CLOCK PULSES NEEDED TO LOAD THE REGISTER = 1)


e.g., Let A and B be two n-bit registers

$A_n \dots A_2 A_1$

$B_n \dots B_2 B_1$


e.g., 4-Bit Register with Parallel Load

READ

 

e.g., 4-Bit Register with Parallel Load

After write, turn load to 0.

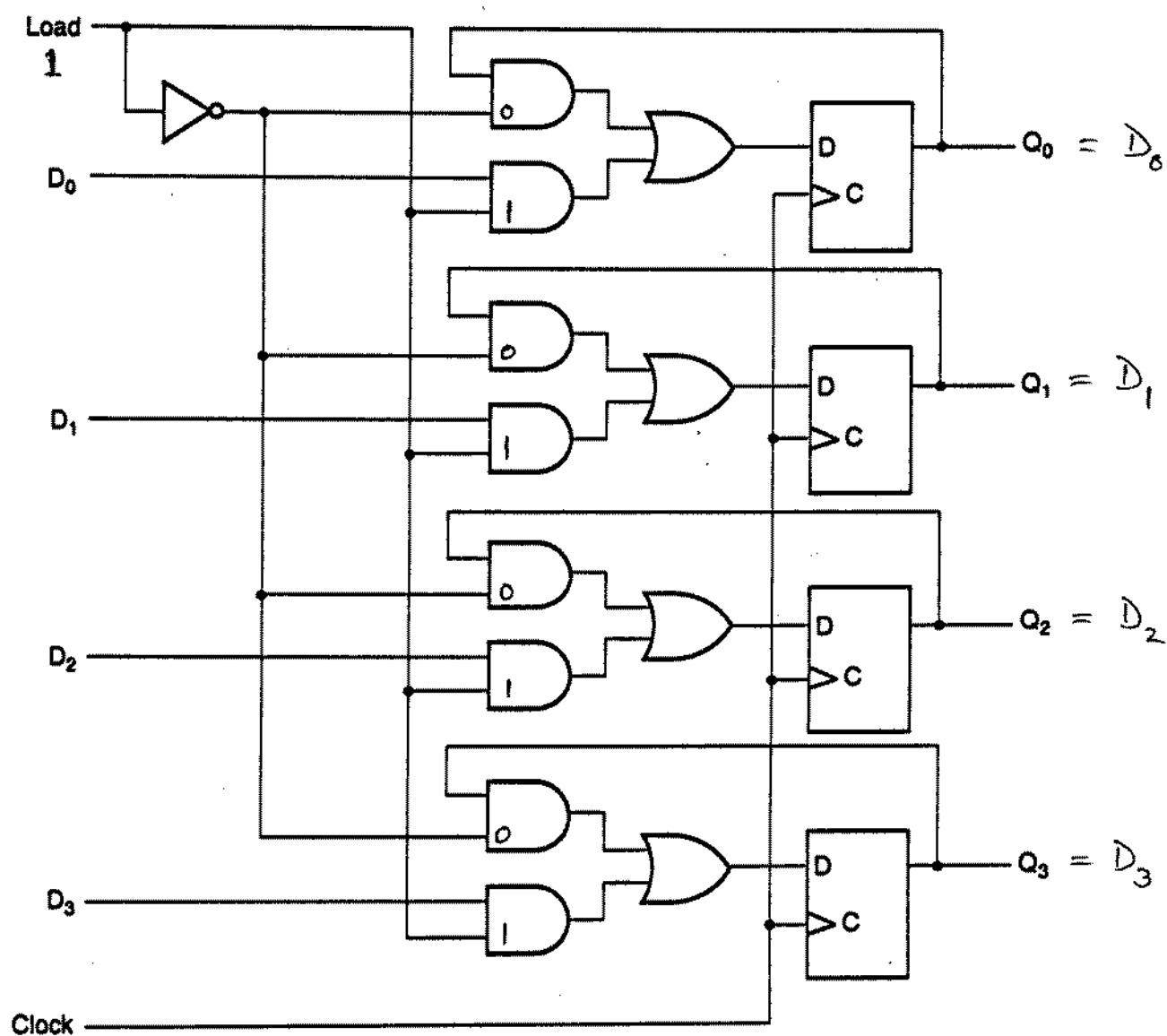

SHIFT REGISTER


A REGISTER CAPABLE OF SHIFTING ITS BINARY INFO TO ITS LEFT OR RIGHT
A REGISTER WHERE RS OR D FF'S ARE CONNECTED IN CASCADE

- UNIDIRECTIONAL SHIFT REGISTER
- BIDIRECTIONAL SHIFT REGISTER

If all the flip-flop outputs of a shift register are accessible, then information entered serially by shifting can be taken out in parallel from the outputs of all of the flip-flops. If a parallel load capability is also added to a shift register, then data entered in parallel can be taken out in serial fashion by shifting out the data in the register. Thus, a shift register with accessible flip-flop outputs and parallel load can be used for converting incoming parallel data to outgoing serial data and vice versa.

Shift Register with Parallel Load


Shift	Load	Operation	$Q_i(t+1)$
0	0	No change	$Q_i(t)$
0	1	Load parallel data	D_i
1	x	Shift down from Q_0 to Q_3	$Q_{i-1}(t)$

 

Shift Register with Parallel Load

Write

Shift	Load	Operation
0	0	No change
0	1	Load parallel data
1	x	Shift down from Q_0 to Q_3

 

- Supply a value by serial input.

Shift Register with Parallel Load

Shift	Load	Operation
0	0	No change
0	1	Load parallel data
1	X	Shift down from Q_0 to Q_3

