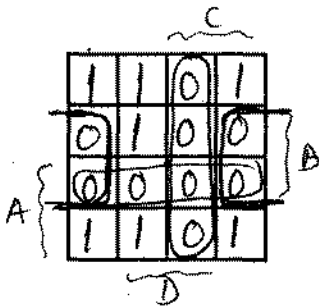


GIVEN $f = e$ IN CSOP, OBTAIN MINIMAL POS

Procedure-CSOP-to-POS

- 1- MARK f ON THE MAP
- 2- f' IS DEFINED BY THOSE SQUARES NOT MARKED AS 1
(f' IS DEFINED BY THOSE SQUARES MARKED AS 0)
- 3 - OBTAIN A MINIMAL e FOR f' IN SOP BY COVERING ALL 0-SQUARES WITH MINIMAL NUMBER OF LARGEST POSSIBLE AREAS OF SIZE 2^k , $k = 0, 1, 2, \dots$ FORMED BY COMBINING ADJACENT 0-SQUARES
- 4- TAKE COMPLEMENT OF f' IN SOP TO OBTAIN f IN POS

e.g., $f(A,B,C,D) = \sum m(0, 1, 2, 5, 8, 9, 10) = B'D' + B'C' + A'C'D$



$$f' = AB + CD + BD'$$

$$\begin{aligned}
 f &= (f')' = (AB + CD + BD')' \\
 &= (AB)' \cdot (CD)' \cdot (BD')' \\
 &= (A' + B')(C' + D')(B' + D)
 \end{aligned}$$

GIVEN $f = e$ in CPOS, OBTAIN MINIMAL SOP

- 1) Obtain CSOP from the given CPOS
- 2) Apply Procedure-CSOP-to-SOP

GIVEN $f = e$ IN CPOS, OBTAIN MINIMAL POS

- 1) Obtain CSOP from the given CPOS
- 2) Apply Procedure-CSOP-to-POS

e.g., Given $f(x,y,z) = \Pi M(0, 2, 5, 7)$ in CPOS,

A) Obtain minimal SOP

$f(x,y,z) = \Pi M(0, 2, 5, 7)$ in CPOS is $f(x,y,z) = \Sigma m(1, 3, 4, 6)$ in CSOP

		y	
		$\begin{array}{ c c } \hline 0 & 1 \\ \hline \end{array}$	
$x \{$	0	1	0
	1	0	1
		z	

$$f = xz' + x'z$$

B) Obtain minimal POS

$f(x,y,z) = \Pi M(0, 2, 5, 7)$ in CPOS is $f(x,y,z) = \Sigma m(1, 3, 4, 6)$ in CSOP

		y	
		$\begin{array}{ c c } \hline 0 & 1 \\ \hline \end{array}$	
$x \{$	0	1	0
	1	0	1
		z	

$$f' = xz + x'z'$$

$$\Rightarrow f = (x' + z')(x + z)$$

SIMPLIFICATION OF FUNCTIONS WITH DON'T CARE CONDITIONS

$\times$ = DON'T CARE is a value of a function f corresponding to an input combination that will never occur

e.g.,

w	x	y	z	f
0	0	0	0	$\times$
0	0	0	1	0
0	0	1	0	$\times$
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	$\times$

$$\Rightarrow f(w,x,y,z) = \sum m(4, 5, 6, 8, 9, 10, 12, 13, 14) + d(0, 2, 15)$$

y			
x			x
1	1		1
1	1	x	1
1	1		1
z			

w is indicated by a bracket on the left, and x by a bracket on the right.

y			
x	0	0	x
		0	
		x	
		0	
z			

w is indicated by a bracket on the left, and x by a bracket on the right.

A) Obtain minimal SOP

$$f = z' + xy' + wy'$$

B) Obtain minimal POS

$$f' = w'x' + yz$$

$$f = (w+x)(y'+z')$$

FROM STANDARD TO CANONICAL FORMS OF EXPRESSIONS

A) SOP $\rightarrow$ CSOP

EXAMINE EACH TERM IN e

IF TERM IS A MINTERM

THEN CONTINUE WITH THE NEXT TERM

ELSE FOR EACH MISSING x_i , PERFORM $(x_i + x'_i)$ AND TERM
SIMPLIFY AND ELIMINATE REDUNDANT TERMS

$$\begin{aligned}
 \text{e.g., } f(x,y,z) &= x'y + z' + xyz \\
 &= (x'y) \cdot (z + z') + (x + x') \cdot (y + y') \cdot z' + xyz \\
 &= x'yz + x'yz' + xyz' + xy'z' + x'yz' + x'y'z' + xyz \\
 &= x'yz + x'yz' + xyz' + xy'z' + x'y'z' + xyz \\
 &= m_3 + m_2 + m_6 + m_4 + m_0 + m_7 \\
 &= \sum m(0, 2, 3, 4, 6, 7)
 \end{aligned}$$

B) POS $\rightarrow$ CPOS

EXAMINE EACH TERM IN e

IF TERM IS A MAXTERM

THEN CONTINUE WITH THE NEXT TERM

ELSE FOR EACH MISSING x_i , PERFORM $(x_i + x'_i)$ OR TERM
SIMPLIFY AND ELIMINATE REDUNDANT TERMS

$$\begin{aligned}
 \text{e.g., } f(x,y,z) &= x' \cdot (y' + z) \\
 &= (x' + yy' + zz') \cdot (y' + z + xx') \\
 &= [(x' + y + z) \cdot (x' + y + z') \cdot (x' + y' + z) \cdot (x' + y' + z')] \cdot [(x + y' + z) \cdot (x' + y' + z)] \\
 &= (x' + y + z) \cdot (x' + y + z') \cdot (x' + y' + z) \cdot (x' + y' + z') \cdot (x + y' + z) \\
 &= M_4, M_5, M_6, M_7, M_2 \\
 &= \prod M(2, 4, 5, 6, 7)
 \end{aligned}$$

(IF THE VALUE OF A FUNCTION

IS INDEPENDENT OF THE VALUE OF SOME TERM/LITERAL

THEN THAT TERM/LITERAL IS REDUNDANT)

$$\begin{aligned}
 \text{e.g., } f(x,y,z) &= x'y'z + yz + xz \\
 &= z \cdot (x'y' + y + x) \\
 &= z \cdot (x' + y + x) \\
 &= z \cdot (y + 1) \\
 &= z \cdot 1 \\
 &= z
 \end{aligned}$$

since $y + x'y' = (y + x')(y + y')$
 $= y' + x'$
 by (p4)

SHORT-CUT FOR SOP $\rightarrow$ CSOP AND MORE ...

$$f(x,y,z) = x'y + z' + xyz \text{ in SOP}$$

$$f(x,y,z) = y + z' \text{ in minimal SOP}$$

$$f(x,y,z) = \sum m(0,2,3,4,6,7) \text{ in CSOP}$$

$$f(x,y,z) = \prod M(1,5) \text{ in CPOS}$$

$$f'(x,y,z) = \sum m(1,5) \text{ in CSOP}$$

$$f'(x,y,z) = \prod M(0,2,3,4,6,7) \text{ in CPOS}$$

5) IMPLEMENTATION OF $f(x_1, x_2, \dots, x_n)$

in a BOOLEAN EXPRESSION

each LITERAL

each TERM




in a CIRCUIT

an INPUT to a gate


a GATE


LOGIC GATES

Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = xy$	<table> <tr><th>x</th><th>y</th><th>F</th></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table> <tr><th>x</th><th>y</th><th>F</th></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table> <tr><th>x</th><th>F</th></tr> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table> <tr><th>x</th><th>F</th></tr> <tr><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td></tr> </table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	
NAND		$F = (xy)'$	<table> <tr><th>x</th><th>y</th><th>F</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = (x + y)'$	<table> <tr><th>x</th><th>y</th><th>F</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$F = xy' + x'y$ $= x \oplus y$	<table> <tr><th>x</th><th>y</th><th>F</th></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$F = xy + x'y'$ $= x \odot y$	<table> <tr><th>x</th><th>y</th><th>F</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

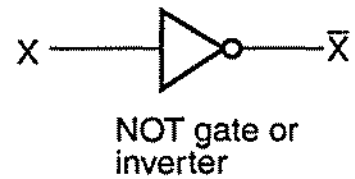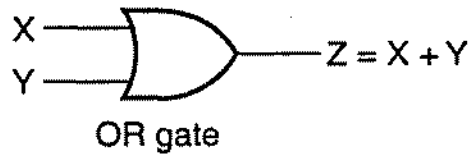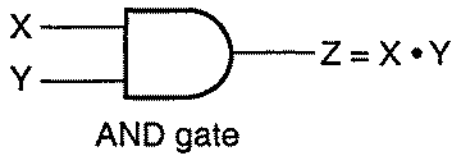


(a) Graphic symbols


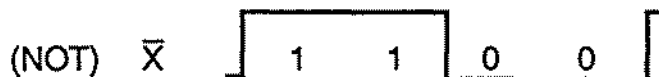


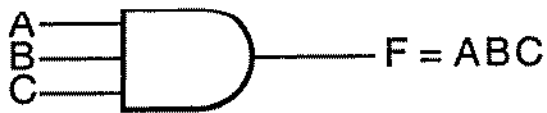


Three-input AND gate

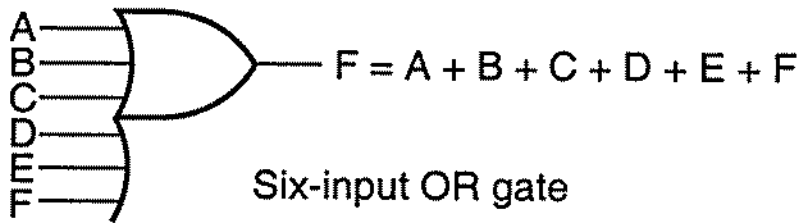


Six-input OR gate

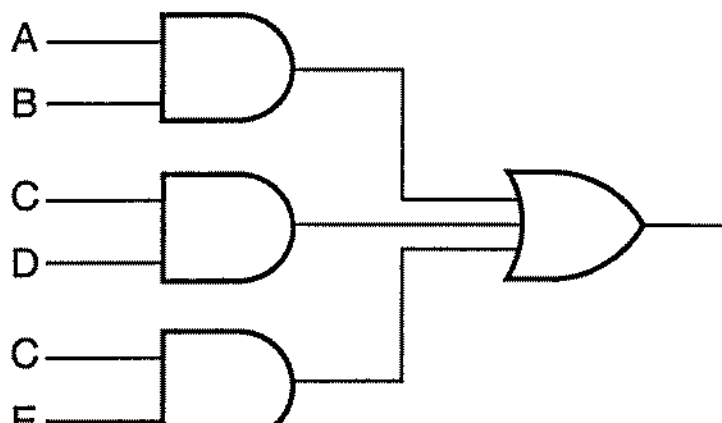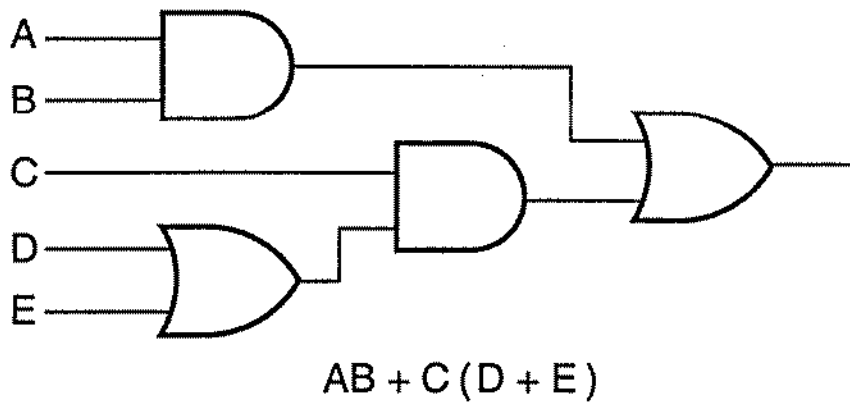


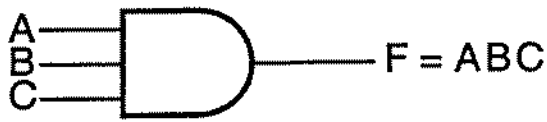


Three-input AND gate

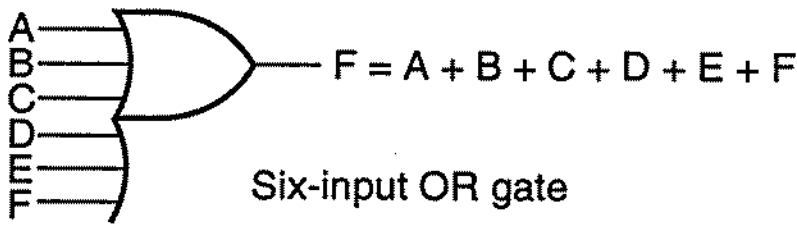

Six-input OR gate

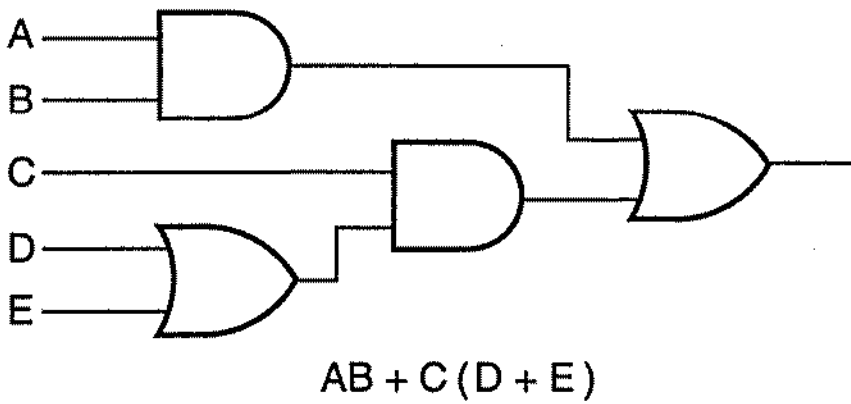

$AB + C(D + E)$


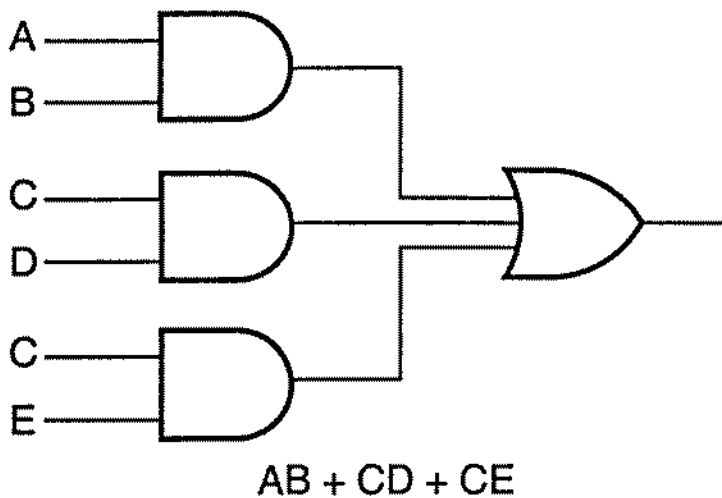


$AB + CD + CE$

AND - OR - INVERT FORM A FUNCTIONALLY COMPLETE SET

NAND



FORMS A FUNCTIONALLY COMPLETE SET

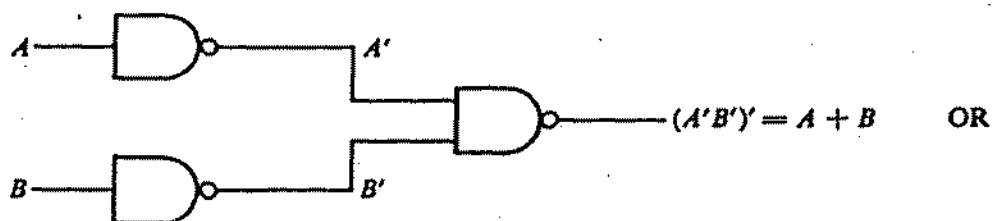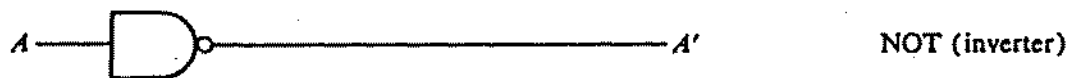

Implementation of NOT, AND, and OR by NAND gates

NOR

FORMS A FUNCTIONALLY COMPLETE SET

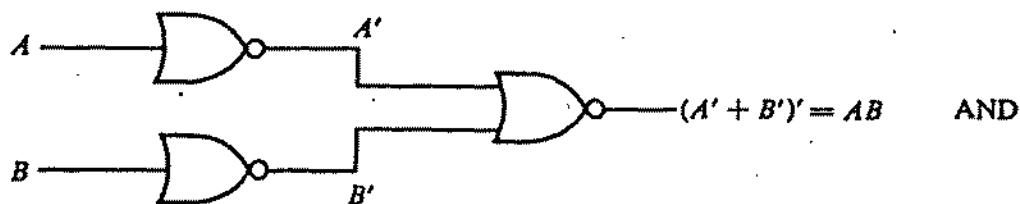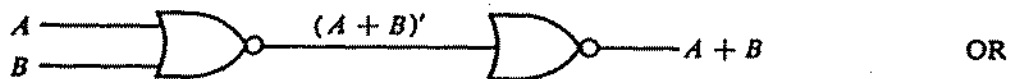

Implementation of NOT, OR, and AND by NOR gates