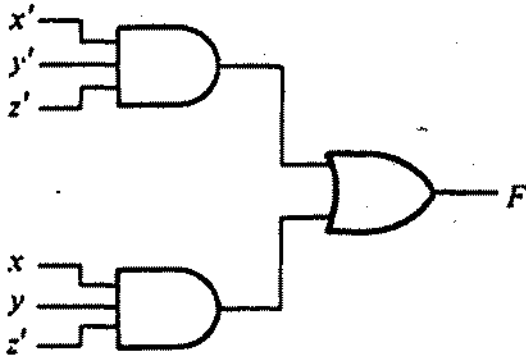


IMPLEMENTATION of $f = e$ in SOP using

A) AND, OR, INVERT gates


e.g., $f(x,y,z) = x'y'z' + xyz'$



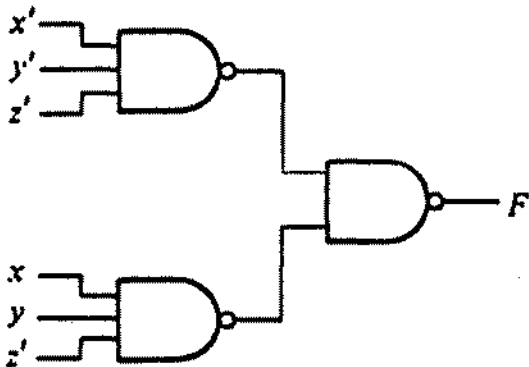B) NAND gates

e.g., $f(x,y,z) = x'y'z' + xyz'$

$$= \left[(x'y'z')' \cdot (xyz')' \right]'$$




C) NOR gates

(implement $(f)'$ and invert the output)

e.g., $f(x,y,z) = x'y'z' + xyz'$

$$(x+y+z)' + (x'+y'+z)'$$
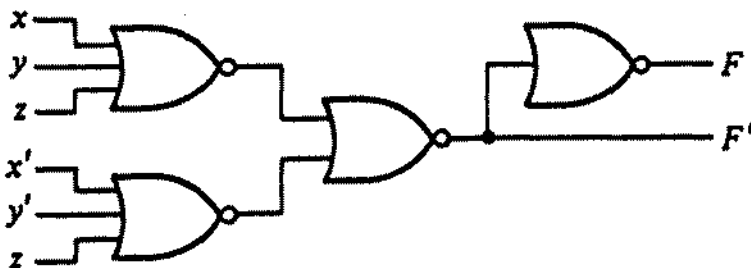
$$\begin{aligned} f' &= (x'y'z' + xyz')' \\ &= (x'y'z')' \cdot (xyz')' \\ &= (x+y+z) \cdot (x'+y'+z) \end{aligned}$$




$$\begin{aligned} f &= (x+y+z)' + (x'+y'+z)' \\ &= \left[(x+y+z)' + (x'+y'+z)' \right]' \end{aligned}$$

IMPLEMENTATION of $f = e$ in POS using

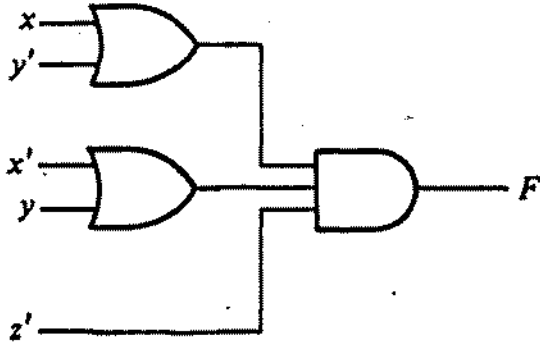
A) AND, OR, INVERT gates

e.g., $f(x,y,z) = (x + y') \cdot (x' + y) \cdot z'$



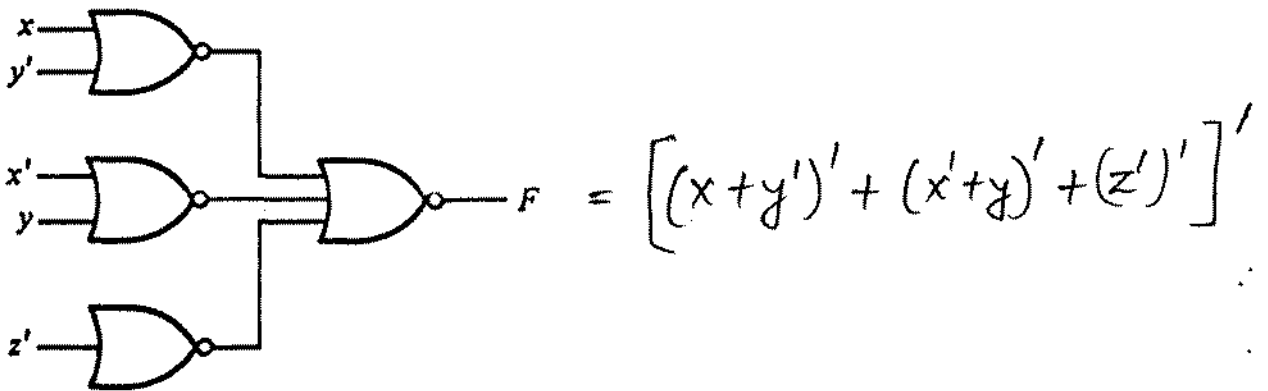B) NOR gates

e.g., $f(x,y,z) = (x + y') \cdot (x' + y) \cdot z'$




C) NAND gates

(implement $(f)'$ and invert the output)

e.g., $f(x,y,z) = (x + y') \cdot (x' + y) \cdot z'$
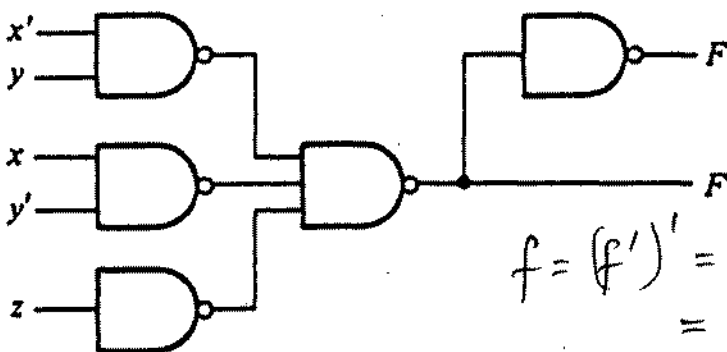
$$\begin{aligned} f' &= (x + y')' + (x' + y)' + z \\ &= x'y + xy' + z \quad \text{Sop form} \end{aligned}$$



$$f' = [(x'y)'(xy')'z']'$$

$$\begin{aligned} f &= (f')' = (x'y)' \cdot (xy')' \cdot z' \\ &= (x + y') \cdot (x' + y) \cdot z' \end{aligned}$$