

MAGNITUDE COMPARATOR

Problem 3.47

⊙ exclusive nor

$$A = A_3 A_2 A_1 A_0$$


$$B = B_3 B_2 B_1 B_0$$

$$\text{Let } X_i = A_i B_i + A_i' B_i' = A_i \odot B_i, \text{ i.e. } X_i = 1 \text{ if } A_i = B_i$$

$$(A=B) = X_3 \cdot X_2 \cdot X_1 \cdot X_0$$

$$(A>B) = A_3 B_3' + X_3 A_2 B_2' + X_3 X_2 A_1 B_1' + X_3 X_2 X_1 A_0 B_0'$$

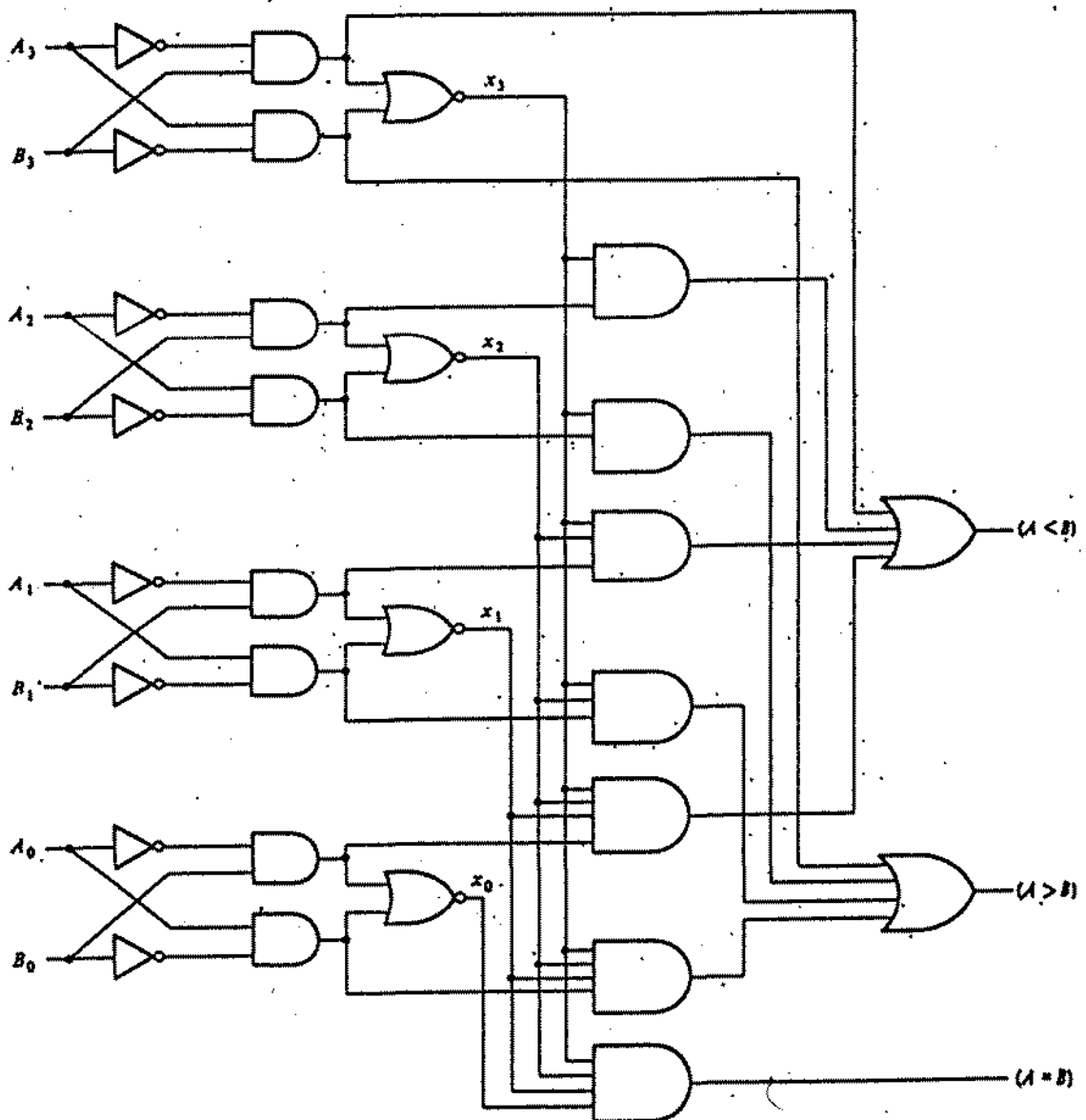
$$(A<B) = A_3' B_3 + X_3 A_3' B_2 + X_3 X_2 A_1' B_1 + X_3 X_2 X_1 A_0' B_0$$




4-bit magnitude comparator

CODE CONVERTER


e.g.

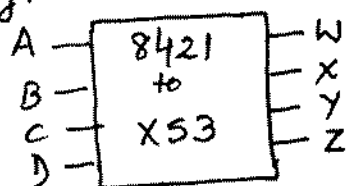


Decimal Digit	Input BCD				Output Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10		1	0	1	0	x	x	x
⋮		⋮					⋮	
15		1	1	1	1	x	x	x

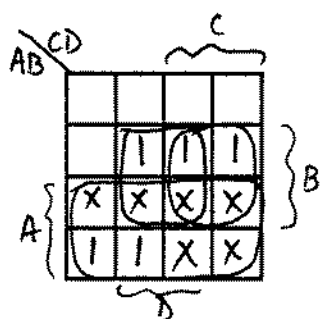


$$W = A + BC + BD$$

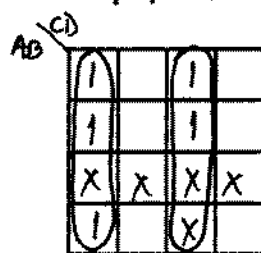


$$Y = CD + C'D'$$

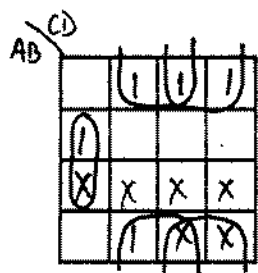

$$X = B'C + B'D + BC'D'$$

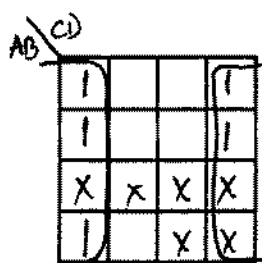

$$Z = D'$$

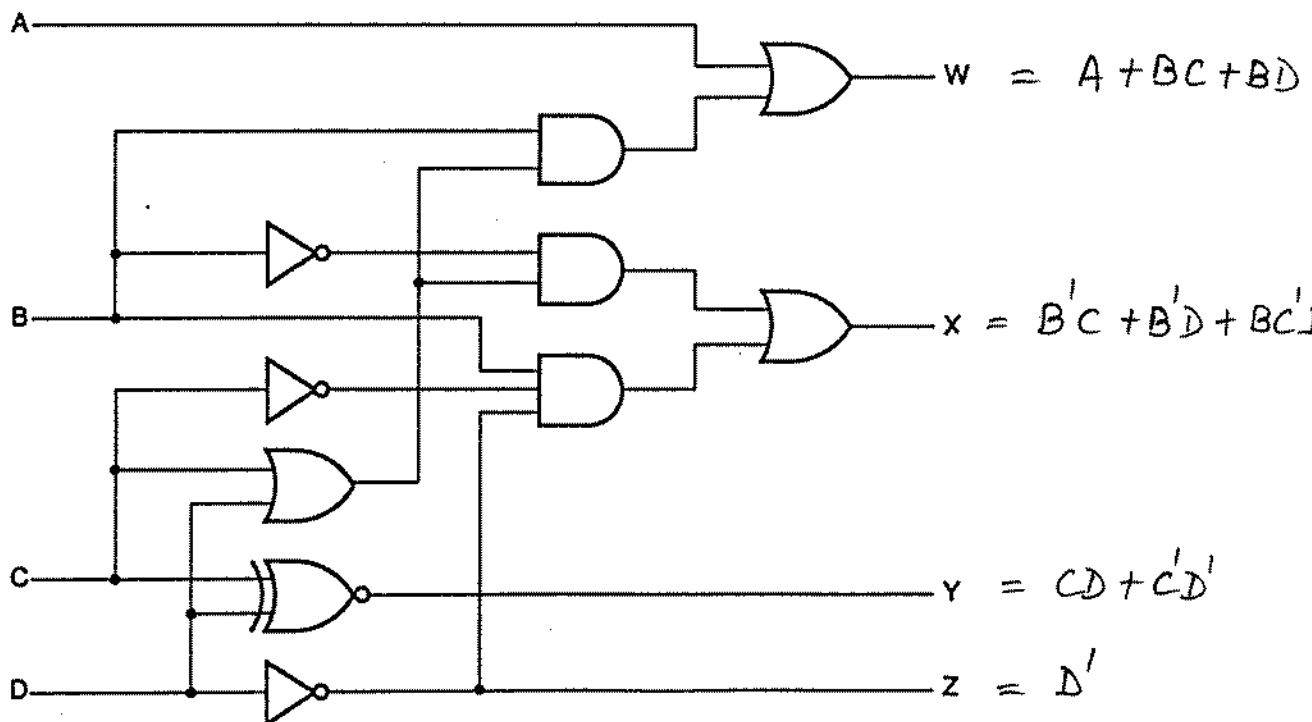

DECODER

DECODES A GIVEN BINARY CODE WORD

n INPUTS



$m \leq 2^n$ OUTPUTS


The output is 2^n possible minterms.

Example: 3-to-8 Decoder (3×8 Decoder)

Truth Table of a 3-to-8-Line Decoder

Inputs			Outputs							
x	y	z	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	1	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$(x'yz) = (101)$

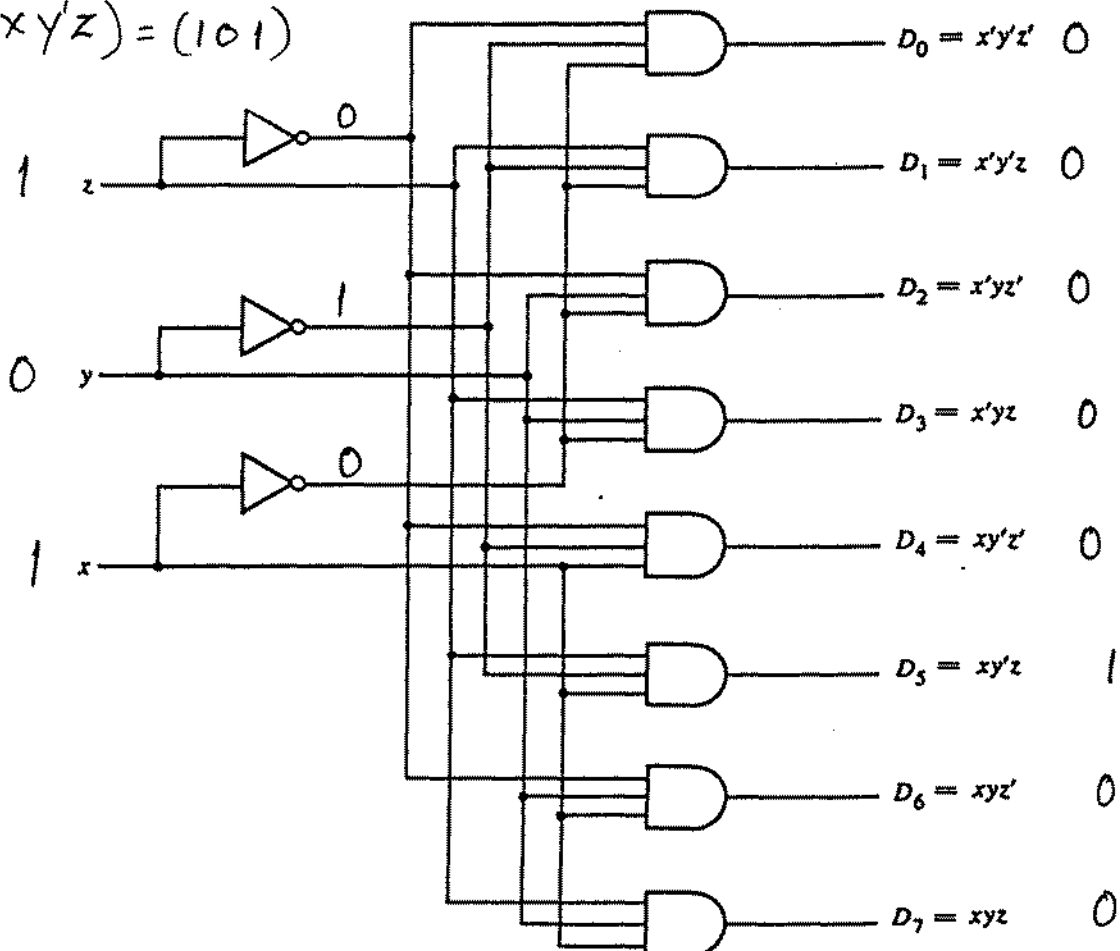


Any boolean function $f(x_1, \dots, x_n)$ can be implemented by an $n \times 2^n$ DECODER & an OR gate.

e.g., FULL ADDER

$$S(x,y,z) = \sum (1,2,4,7)$$

$$C(x,y,z) = \sum (3,5,6,7)$$

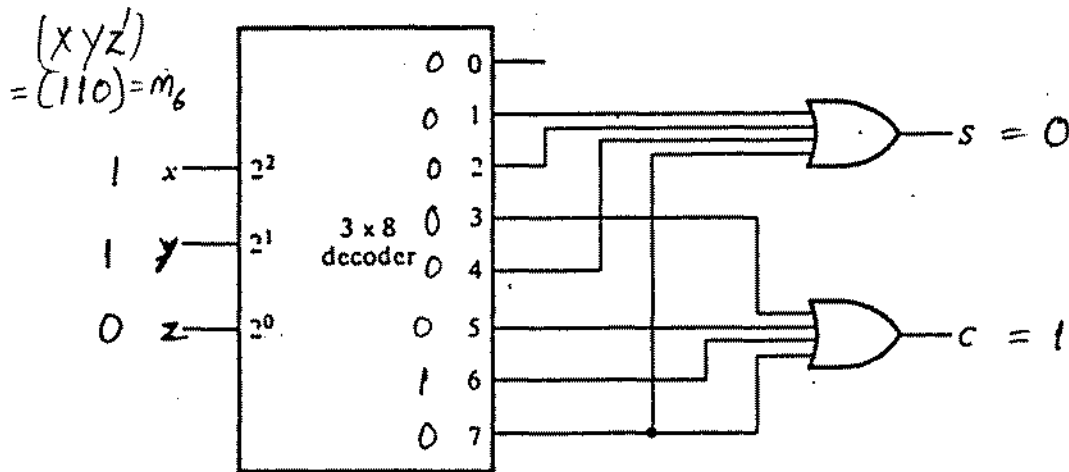Two boolean functions defined over 3 variables need a 3×8 decoder and two OR gates




Implementation of a full-adder with a decoder

VARIOUS DECODERS

n	$n \times 2^n$	Function Table	Block Diagram	Reduced Block Diagram																														
1	1x2	<table><tr><td>x</td><td>D_0</td><td>D_1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr></table>	x	D_0	D_1	0	1	0	1	0	1																							
x	D_0	D_1																																
0	1	0																																
1	0	1																																
2	2x4	<table><tr><td>x</td><td>y</td><td>D_0</td><td>D_1</td><td>D_2</td><td>D_3</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td></tr></table>	x	y	D_0	D_1	D_2	D_3	0	0	1	0	0	0	0	1	0	1	0	0	1	0	0	0	1	0	1	1	0	0	0	1		
x	y	D_0	D_1	D_2	D_3																													
0	0	1	0	0	0																													
0	1	0	1	0	0																													
1	0	0	0	1	0																													
1	1	0	0	0	1																													
3	3x8	Already given	Already shown																															


DECODERS WITH ENABLE INPUT

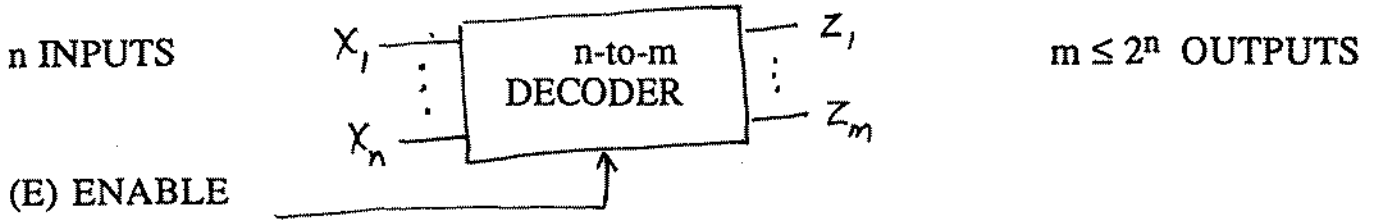

If $E = 0$, ALL OUTPUTS ARE 0

If $E = 1$, ONLY ONE OUT OF m OUTPUTS IS 1, REMAINING OUTPUTS ARE 0
(THAT OUTPUT IS DETERMINED BY THE COMBINATION OF VALUES OF n INPUTS)


e.g., 3x8 DECODER WITH ENABLE INPUT

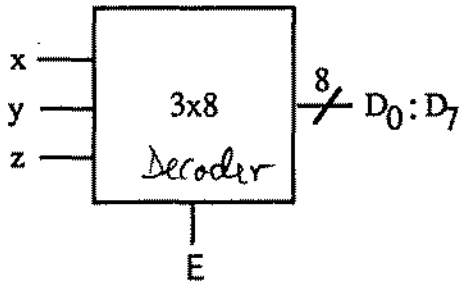

DECODERS CONSTRUCTED USING OTHER DECODERS

e.g., 4x16 DECODER CONSTRUCTED USING TWO 3x8 DECODERS WITH ENABLE INPUTS

$(wxyz) = (0100)$


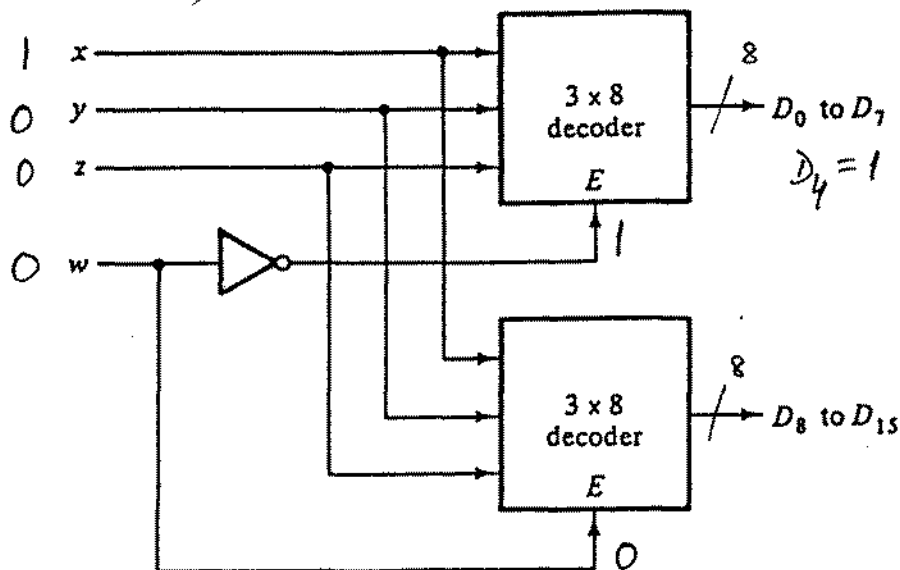


w	x	y	z
0	0	0	0
⋮	⋮	⋮	⋮
0	1	1	1
1	0	0	0
⋮	⋮	⋮	⋮
1	1	1	1

A 4×16 decoder constructed with two 3×8 decoders

e.g.,

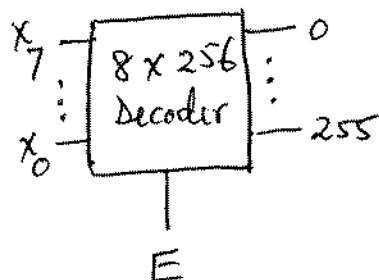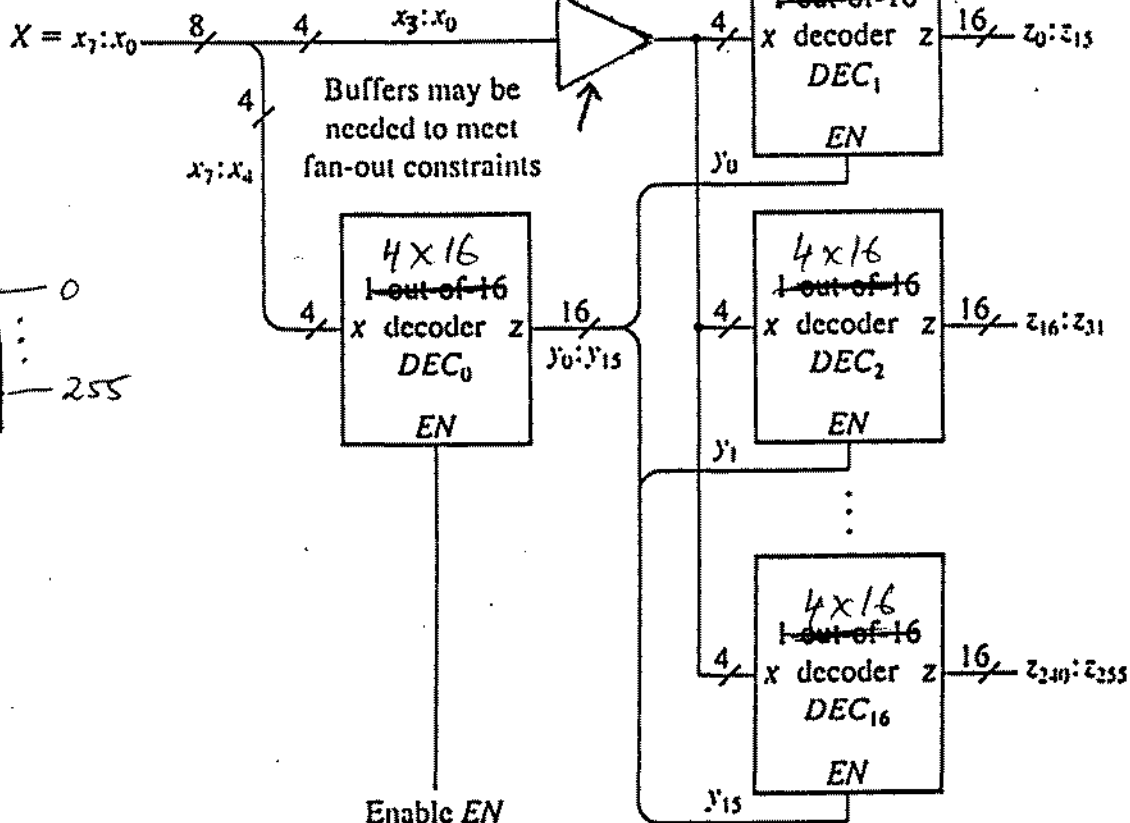8x256 DECODER CONSTRUCTED USING 4x16 DECODERS WITH ENABLE INPUTS



$x_7 x_6 x_5 x_4$ $x_3 x_2 x_1 x_0$

A ~~1-out-of-256~~ decoder tree constructed from ~~1-out-of-16~~ decoders.

