

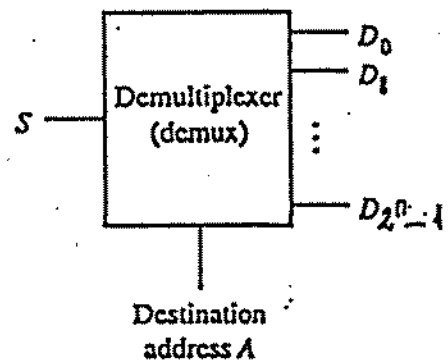
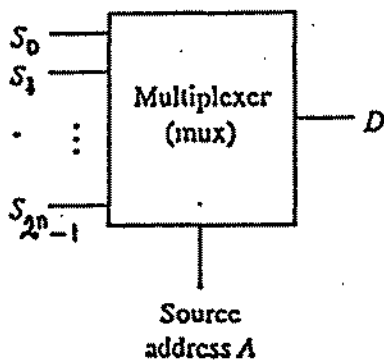
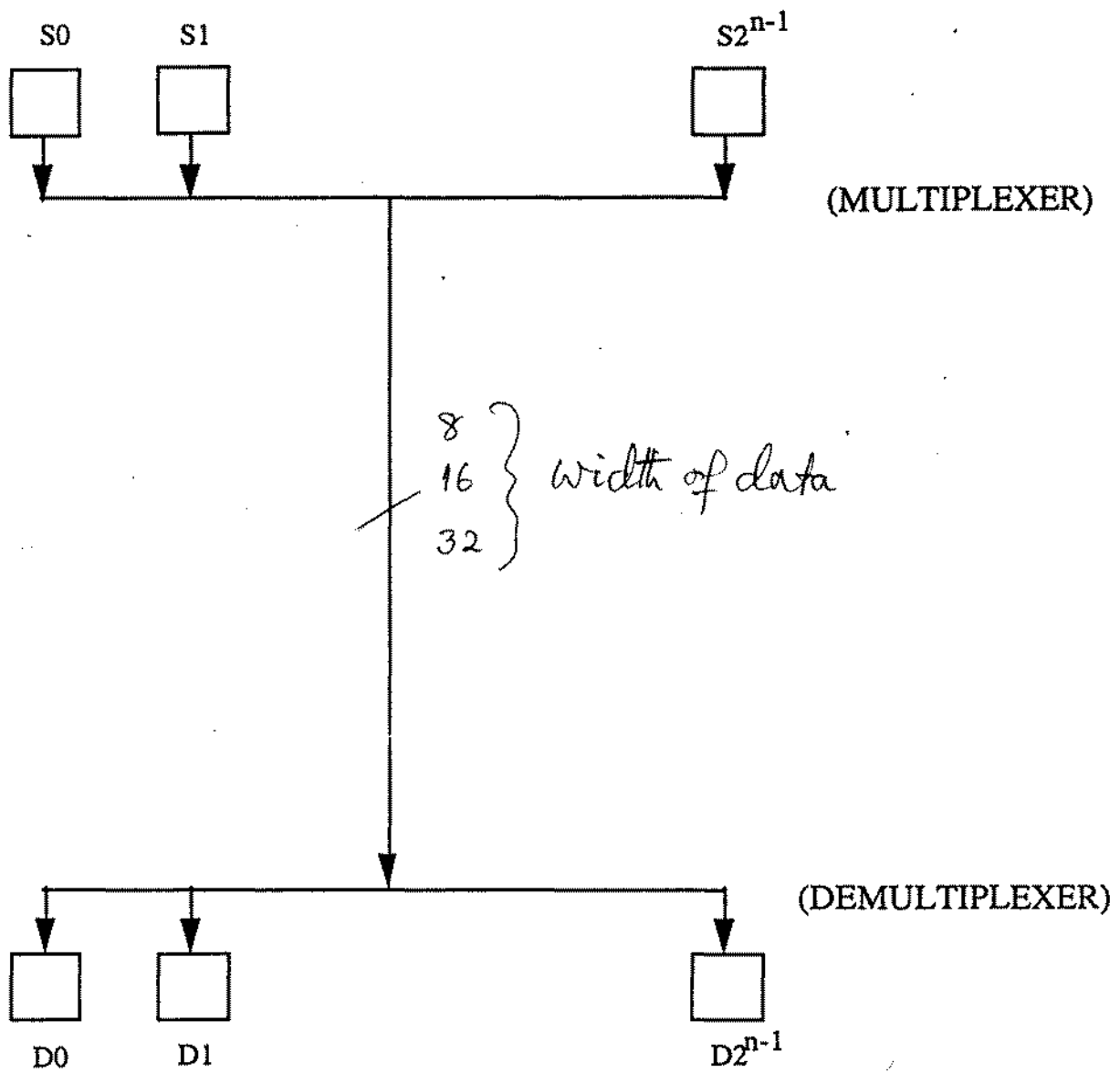
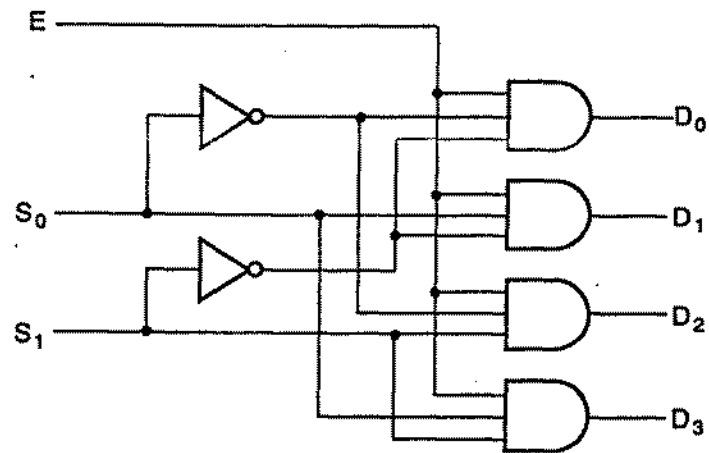


DATA TRANSFER

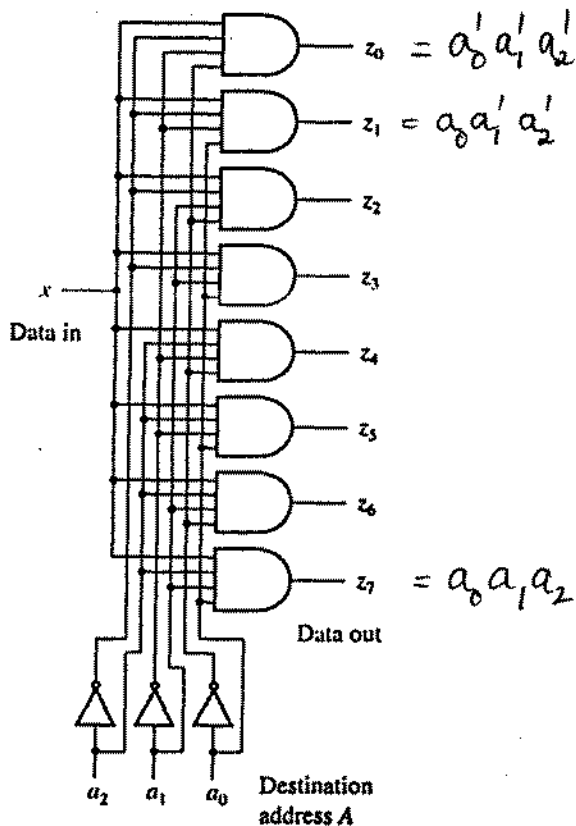

DEMULTIPLEXER (DATA DISTRIBUTOR)

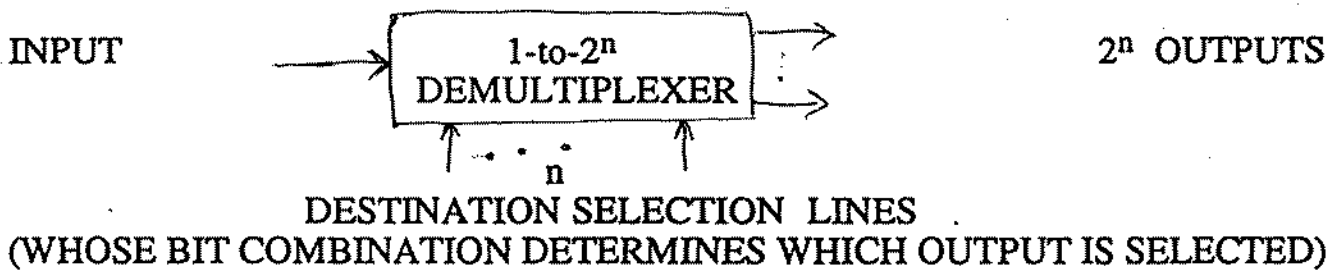DIRECTS THE INPUT TO ONE OUT OF 2^n OUTPUTS



a_2	a_1	a_0	z
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	4
1	0	1	5
1	1	0	6
1	1	1	7

S_1	S_0	D
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

IN GENERAL:



1-to- 2^n DEMULTIPLEXER = n-to- 2^n DECODER

with enable input

MULTIPLEXER (DATA SELECTOR)


Section 3.7

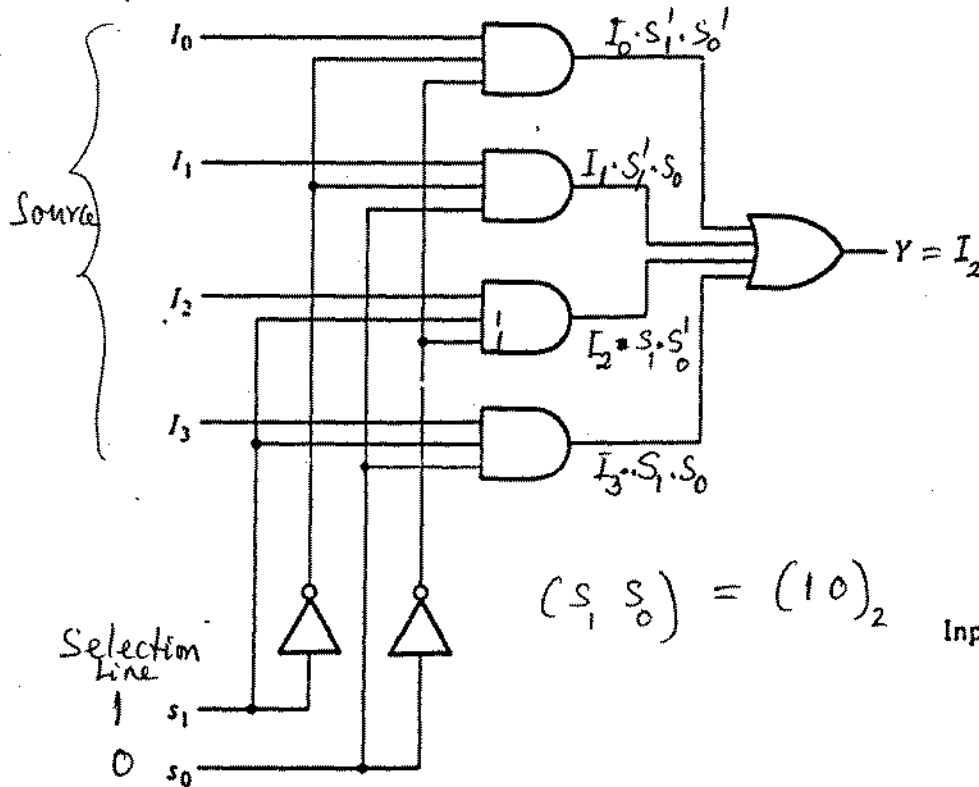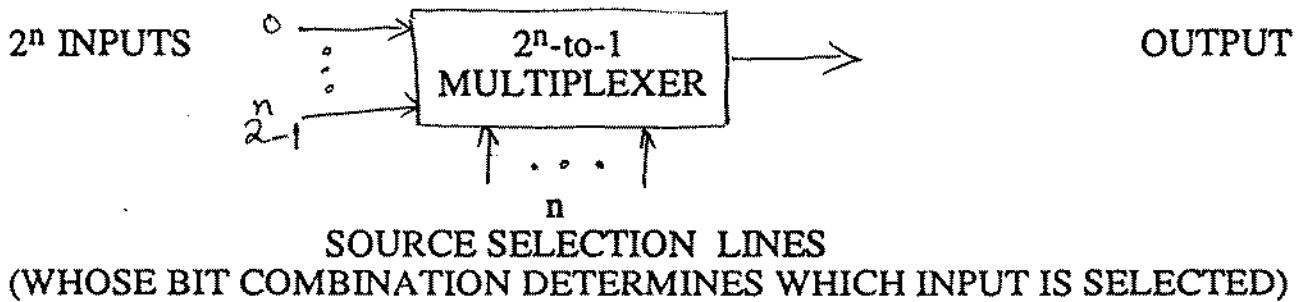SELECTS ONE OUT OF 2^n INPUTS AND DIRECTS IT TO THE OUTPUT



s_1	s_0	$Y = f(s_1, s_0)$
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

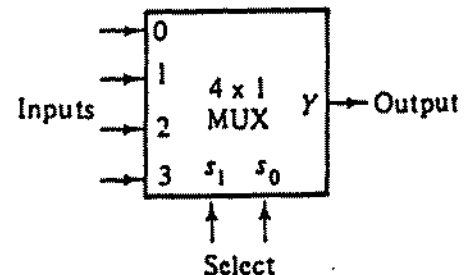

(c) Block diagram

A 4-to-1-line multiplexer

(a) Logic diagram

IN GENERAL:

2^n -to-1 MULTIPLEXER = n -to- 2^n DECODER

+
 2^n INPUT LINES (ONE TO EACH AND GATE)


+
OR GATE (COLLECTING OUTPUTS OF AND GATES)

$\therefore$ Any boolean function $f(x_1, \dots, x_n)$ can be implemented by a 2^{n-1} -to-1 MULTIPLEXER

GIVEN A BOOLEAN FUNCTION $f(x_1, \dots, x_n)$
 IMPLEMENT IT USING A 2^{n-1} -to-1 MULTIPLEXER

PROCEDURE:

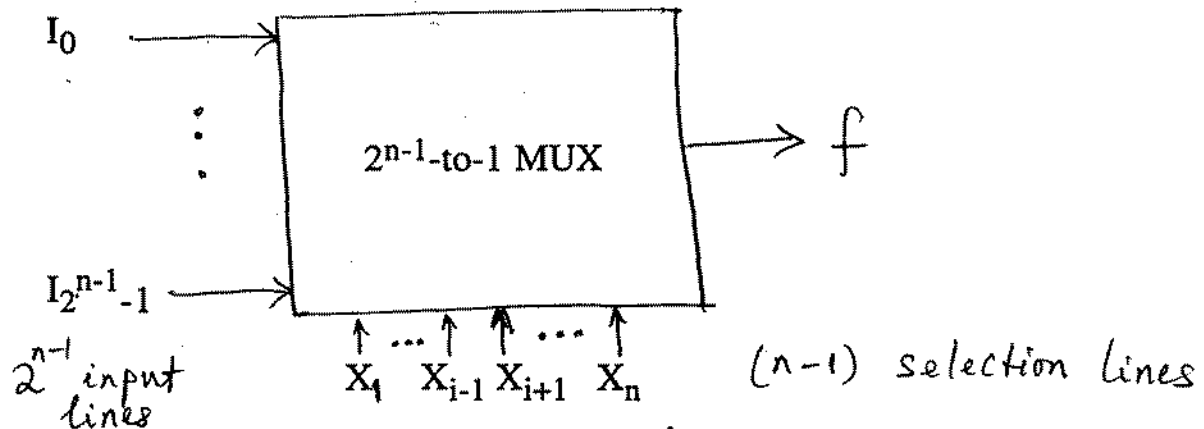1. GIVEN $f(x_1, \dots, x_n)$ in CSOP $= \sum m(\dots)$



(NOTE THAT X_i IS NOT USED AS A SELECTION LINE)

2. FIND THE VALUE OF I_j , for $j = 0, 1, 2, \dots, 2^{n-1}-1$
 BY USING THE TABLE WHOSE FORMAT SHOWN BELOW

	I_0 I_1 I_2 $I_{2^{n-1}-1}$
X'_i	minterms where X_i is primed
X_i	minterms where X_i is unprimed
$\Rightarrow$	VALUES OF I_j

- A) PUT MINTERMS IN THE TABLE
 B) CIRCLE THOSE MINTERMS IN CSOP
 C) INSPECT COLUMN I_j , $j = 0, 1, 2, \dots, 2^{n-1}-1$

if both minterms are NOT circled; $I_j \leftarrow 0$
 if both minterms are circled; $I_j \leftarrow 1$
 if top minterm is circled only; $I_j \leftarrow X'_i$
 if bottom minterm is circled only; $I_j \leftarrow X_i$

GIVEN $f(A, B, C)$ in CSOP,
 PUT MINTERMS IN THE TABLE
 DEPENDING ON THE VARIABLE NOT USED AS A SELECTION LINE.

$f(A, B, C)$		A	B	C	
m0		0	0	0	$A'B'C'$
m1		0	0	1	$A'B'C$
m2		0	1	0	$A'BC'$
m3		0	1	1	$A'BC$
m4		1	0	0	$AB'C'$
m5		1	0	1	$AB'C$
m6		1	1	0	ABC'
m7		1	1	1	ABC

$2^2 = 4$ address can be located.

VARIABLE NOT USED AS A SELECTION LINE IS:

1) A

	I_0	I_1	I_2	I_3
A'	0	1	2	3
A	4	5	6	7

2) B

	I_0	I_1	I_2	I_3
B'	0	1	4	5
B	2	3	6	7

3) C

	I_0	I_1	I_2	I_3
C'	0	2	4	6
C	1	3	5	7

Given F , find a multiplexer implementation.


62

Minterm	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

(b) Truth table

	I_0	I_1	I_2	I_3
A'	0	①	2	③
A	4	⑤	⑥	7
	0	1	A	A'


(c) Implementation table

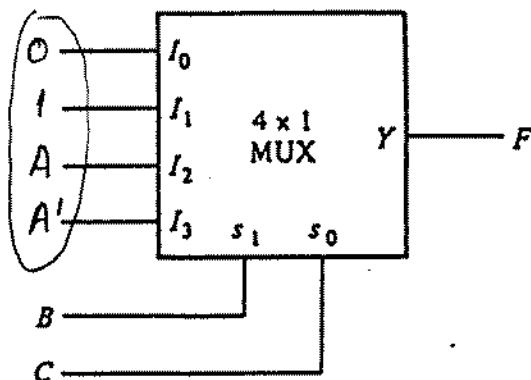

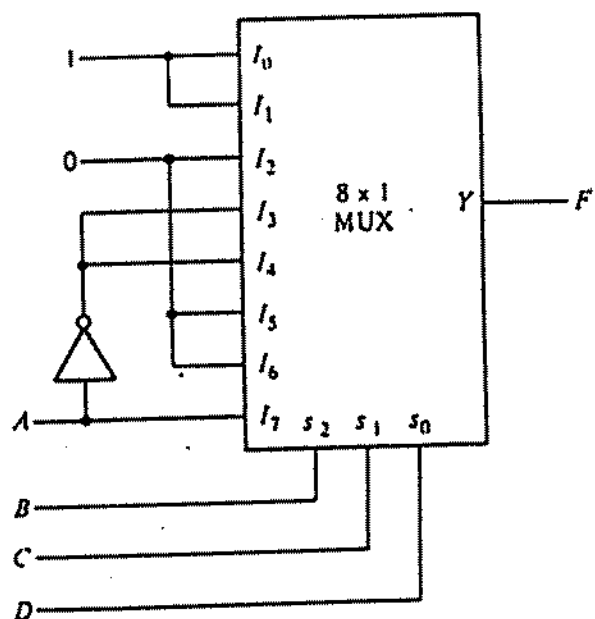(a) Multiplexer implementation

Implementing $F(A, B, C) = \sum (1, 3, 5, 6)$ with a multiplexer

Given a multiplexer implementation, find F .




	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
A'	①	②	3	④	5	6	7	
A	⑧	⑨	10	11	12	13	14	⑮
	1	1	0	A'	A'	0	0	A

Implementing $F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15)$




Must each source be 1 bit? No!

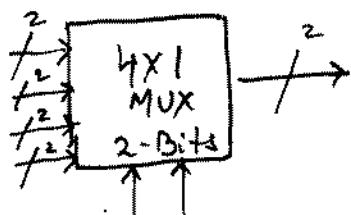

$$z_0 = \bar{a}_1 \bar{a}_0 x_{0,0} + \bar{a}_1 a_0 x_{1,0} + a_1 \bar{a}_0 x_{2,0} + a_1 a_0 x_{3,0}$$

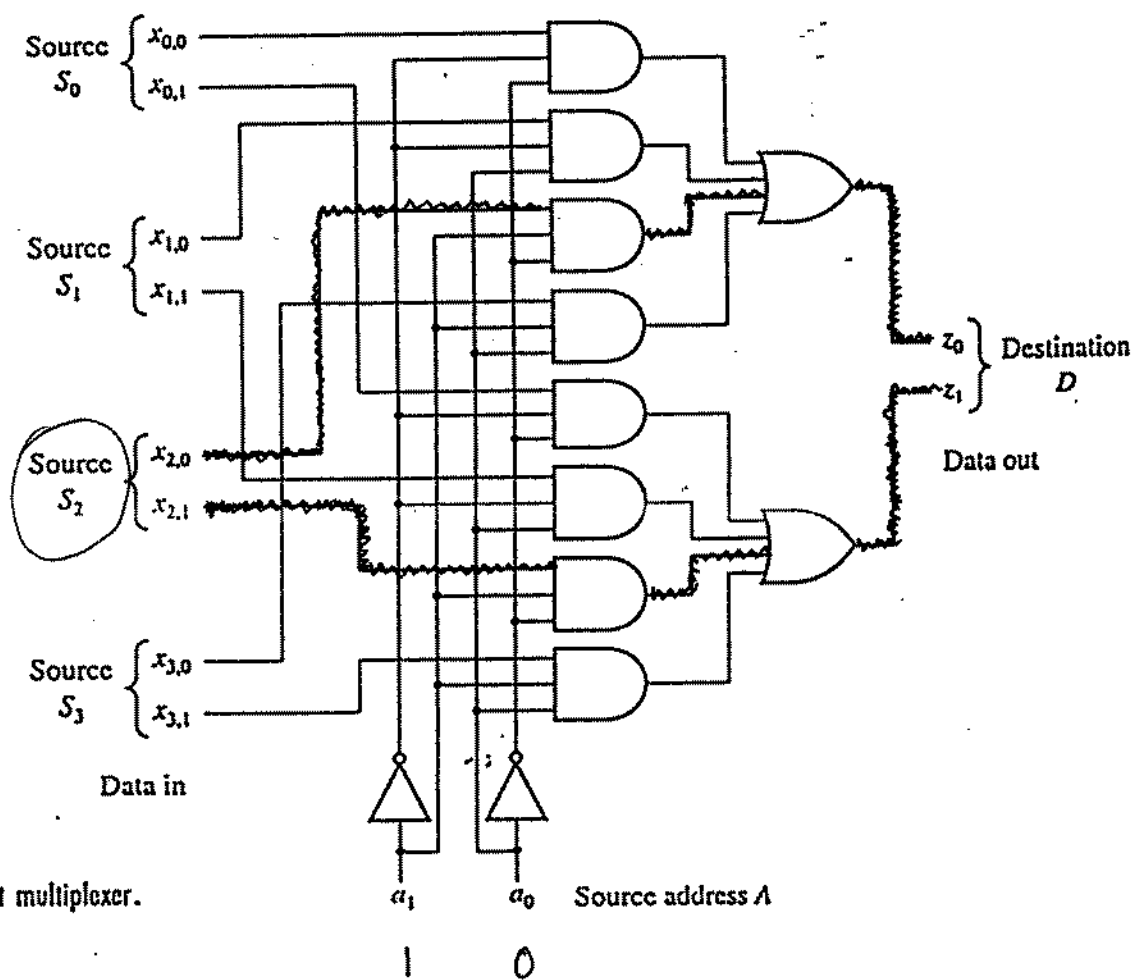
$$z_1 = \bar{a}_1 \bar{a}_0 x_{0,1} + \bar{a}_1 a_0 x_{1,1} + a_1 \bar{a}_0 x_{2,1} + a_1 a_0 x_{3,1}$$






A four-way, 2-bit multiplexer.

4x1


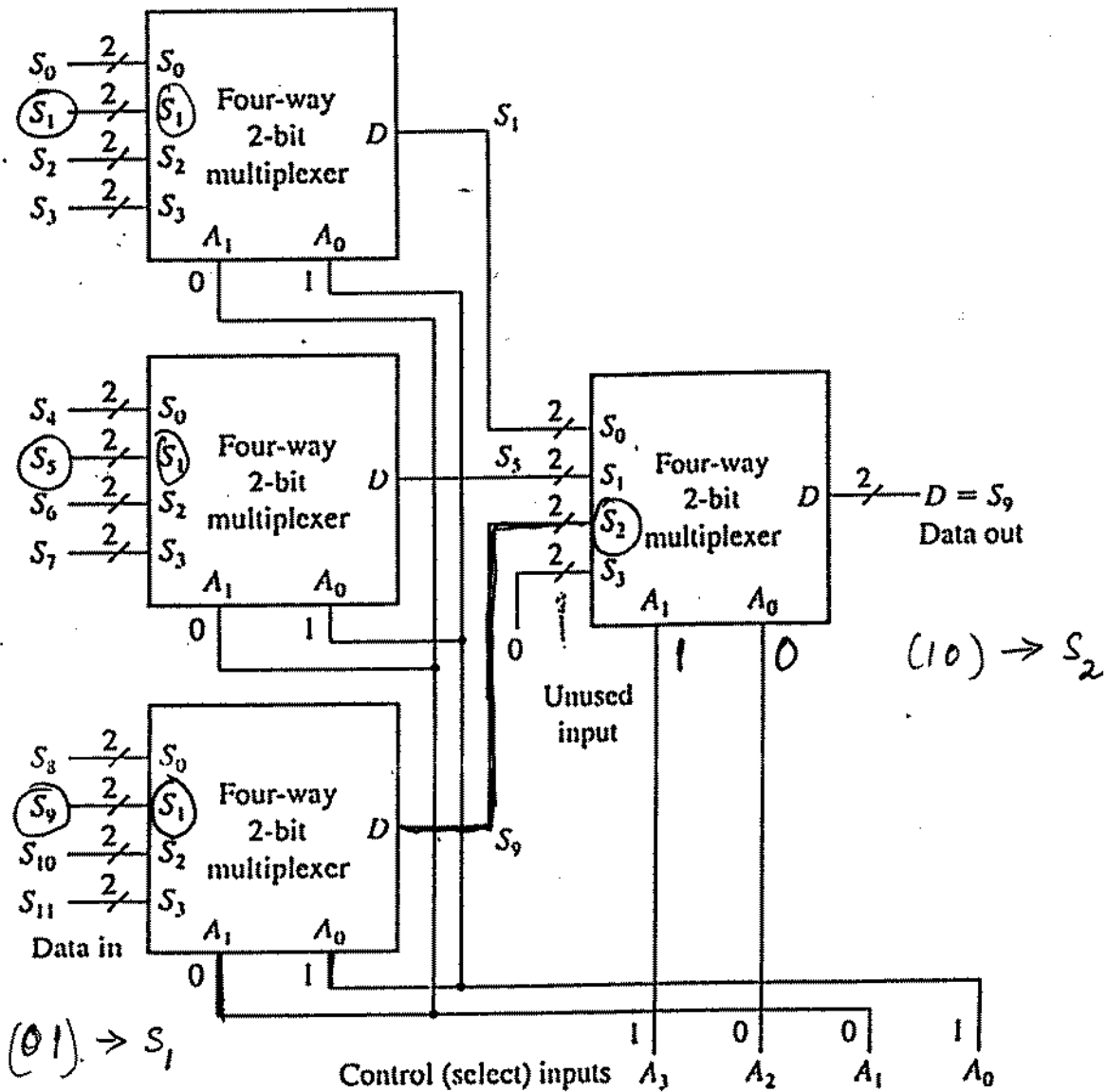
Example: 1 out of 12 is selected by an address of 4 bits. 64



A 12-way multiplexer tree constructed from four-way multiplexers.

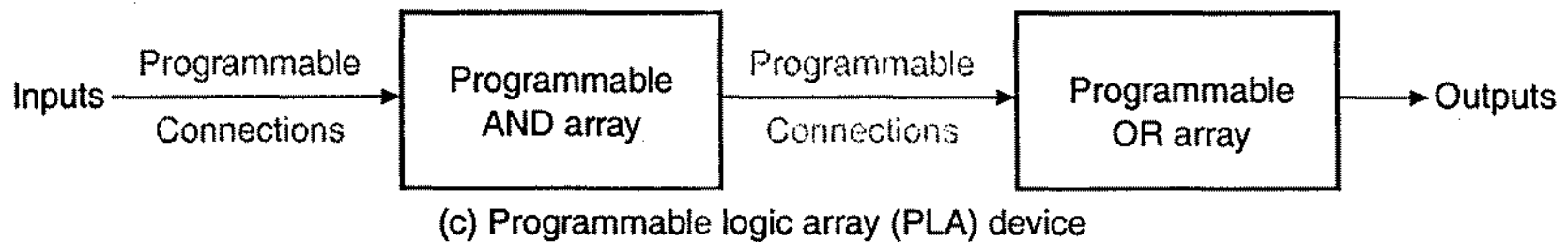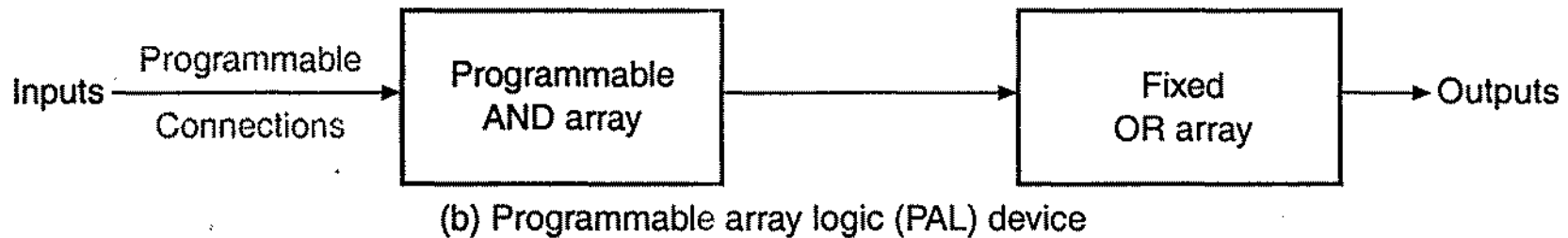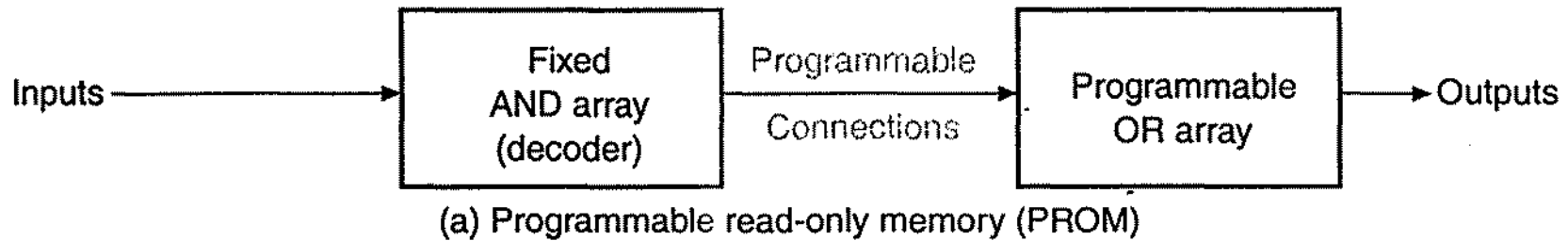Basic Configuration of Three PLDs*Programmable Logic Devices*

ROM (READ-ONLY MEMORY)

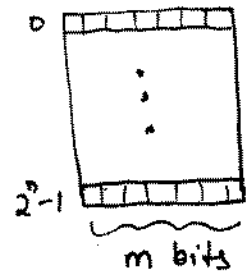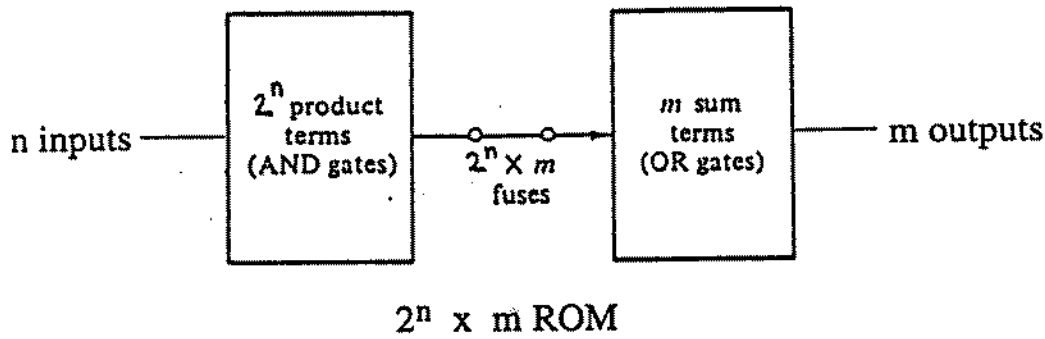

IMPLEMENTING AN n-INPUT, m-OUTPUT COMBINATIONAL CIRCUIT

=
A $2^n \times m$ ROM and one level of PROGRAMMING

e.g., Given the following two functions in CSOP form $n = 2, m = 2$


$$f_1(A_1, A_0) = \sum m(1, 2, 3)$$

$$f_2(A_1, A_0) = \sum m(0, 2)$$


a) Obtain the $2^2 \times 2$ ROM Truth Table for f_1 and f_2

A_1	A_0	F_1	F_2
0	0	0	1
0	1	1	0
1	0	1	1
1	1	1	0

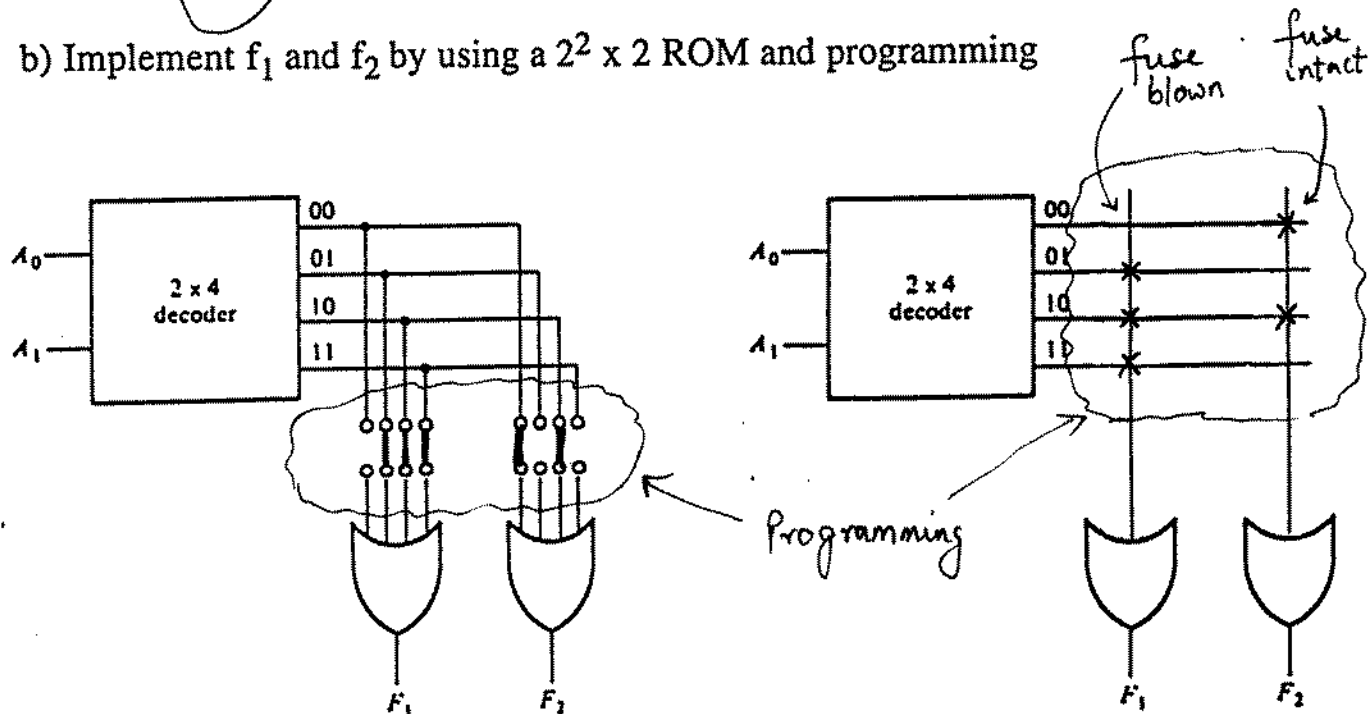b) Implement f_1 and f_2 by using a $2^2 \times 2$ ROM and programming



PLA (PROGRAMMABLE LOGIC ARRAY)

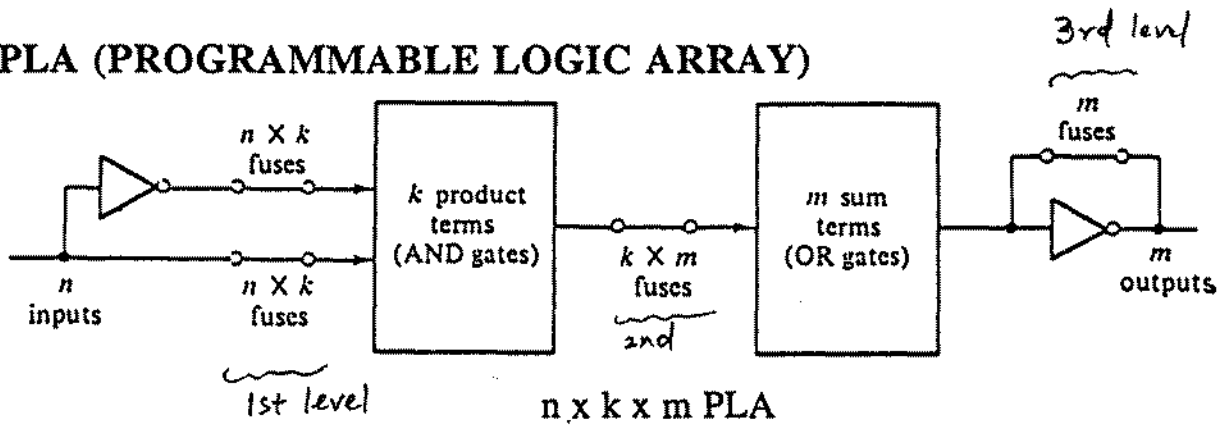

IMPLEMENTING AN n -INPUT, m -OUTPUT COMBINATIONAL CIRCUIT

=
An $n \times k \times m$ PLA and three levels of PROGRAMMING

e.g., Given the following two functions in CSOP form

$$f_1(A, B, C) = \sum m(4, 5, 7)$$

$$f_2(A, B, C) = \sum m(0, 1, 2, 4, 6)$$

a) Obtain the minimal SOP form of f_1 , f_1' , f_2 , and f_2'

1	1	1	

$f_1 = AB' + AC$

1	1		1
1			1

$f_2 = C' + A'B'$

0	0	0	0
			0

$f_1' = A' + BC'$

		0	
	0	0	

$f_2' = AC + BC$

b) Determine the minimal number of product terms that will be sufficient to implement (f_1 or f_1') and (f_2 or f_2')

$$f_1 \text{ \& } f_2' \Rightarrow 3 \text{ product terms}$$

c) Construct the PLA Program Table for f_1 and f_2

		A	B	C	f_1	f_2
1	AB'	1	0	—	1	—
2	AC	1	—	1	1	1
3	BC	—	1	1	—	1
		T C			T	C
					T/C	

T: function itself
C: complement of function

— : don't need this term

		A	B	C	f1	f2
1	AB'	1	0	-	1	-
2	AC	1	-	1	1	1
3	BC	-	1	1	-	1
		T		C	T/C	

d) Implement f_1 and f_2 by using a 3 x 3 x 2 PLA and programming

