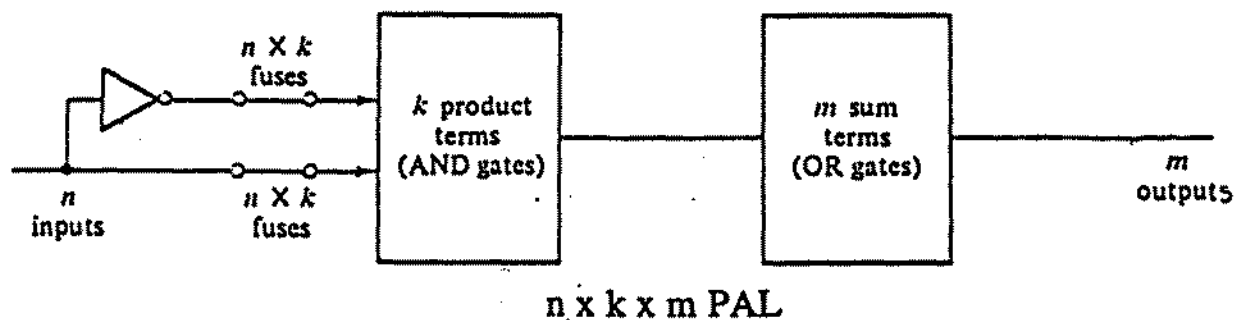


PAL (PROGRAMMABLE ARRAY LOGIC)



IMPLEMENTING AN n -INPUT, m -OUTPUT COMBINATIONAL CIRCUIT

=
An $n \times k \times m$ PAL and one level of PROGRAMMING

e.g., Given the following four functions in CSOP form





$$w(A, B, C, D) = \Sigma(2, 12, 13)$$

$$x(A, B, C, D) = \Sigma(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \Sigma(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A, B, C, D) = \Sigma(1, 2, 8, 12, 13)$$

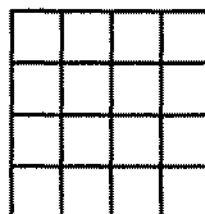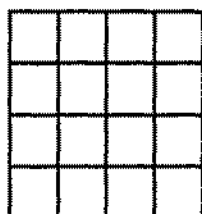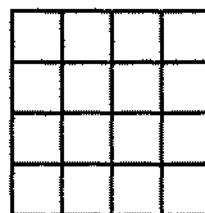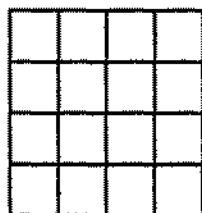a) Obtain the minimal SOP form of w, x, y, z



$$w = ABC' + A'B'CD'$$

$$x = A + BCD$$

$$y = A'B + CD + B'D'$$


$$z = ABC' + A'B'CD' + AC'D' + A'B'C'D$$

$$= w + AC'D' + A'B'C'D$$

b) Construct the PAL Program Table for w, x, y, z



Product Term	AND inputs					Outputs
	A	B	C	D	W	
1	1	1	0	-	-	$w = ABC' + A'B'CD'$
2	0	0	1	0	-	
3	-	-	-	-	-	
4	1	-	-	-	-	$x = A + BCD$
5	-	1	1	1	-	
6	-	-	-	-	-	
7	0	1	-	-	-	$y = A'B + CD + B'D'$
8	-	-	1	1	-	
9	-	0	-	0	-	
10	-	-	-	-	1	$z = w + AC'D' + A'B'C'D$
11	1	-	0	0	-	
12	0	0	0	1	-	

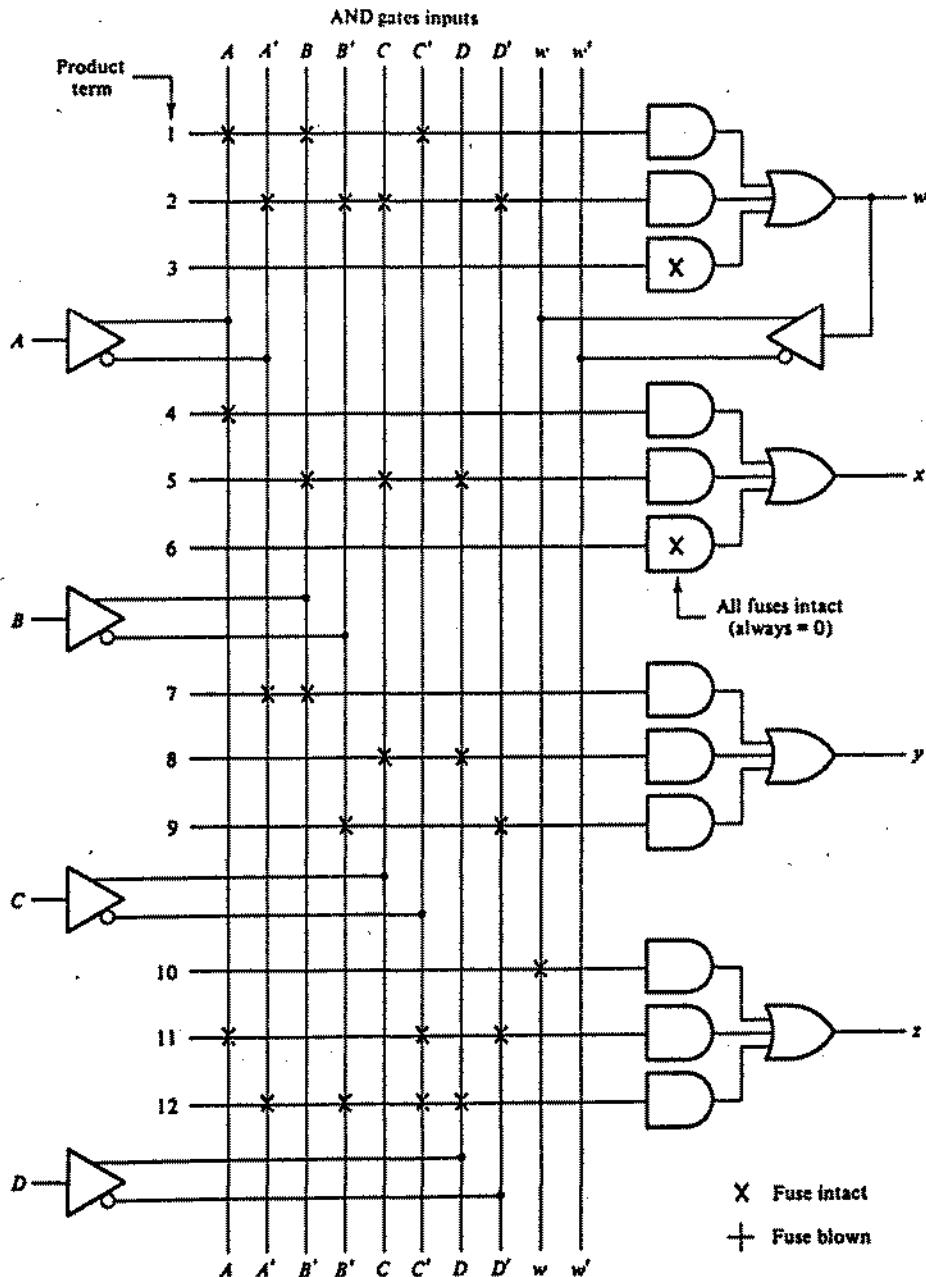c) Implement w, x, y, z using a 4 x 3 x 4 PAL and programming




ALU (Arithmetic Logic Unit)


Section 7.7

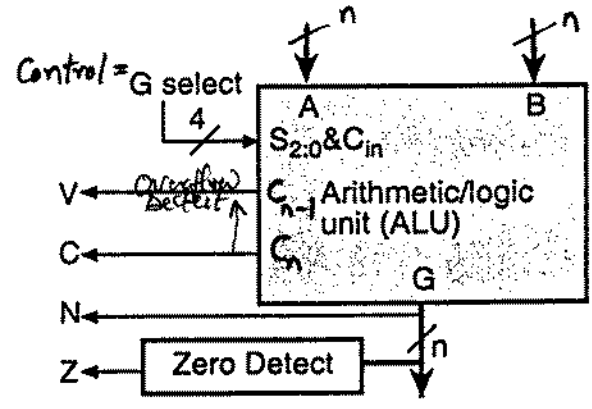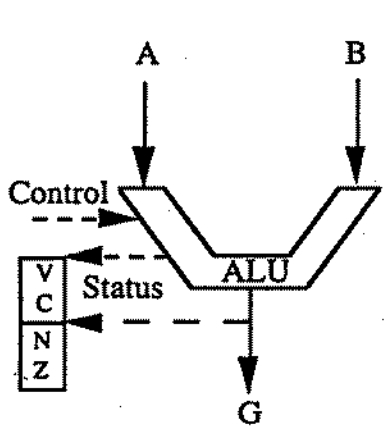

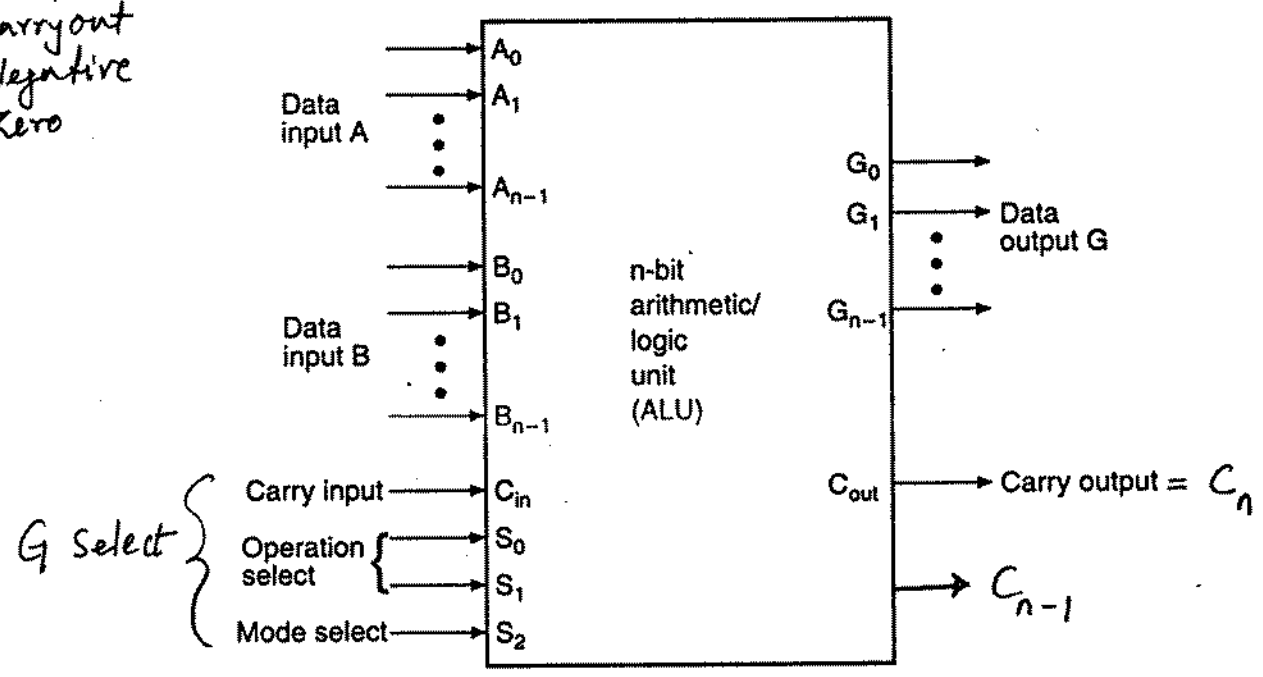V: Overflow detect
 C: Carryout
 N: Negative
 Z: Zero




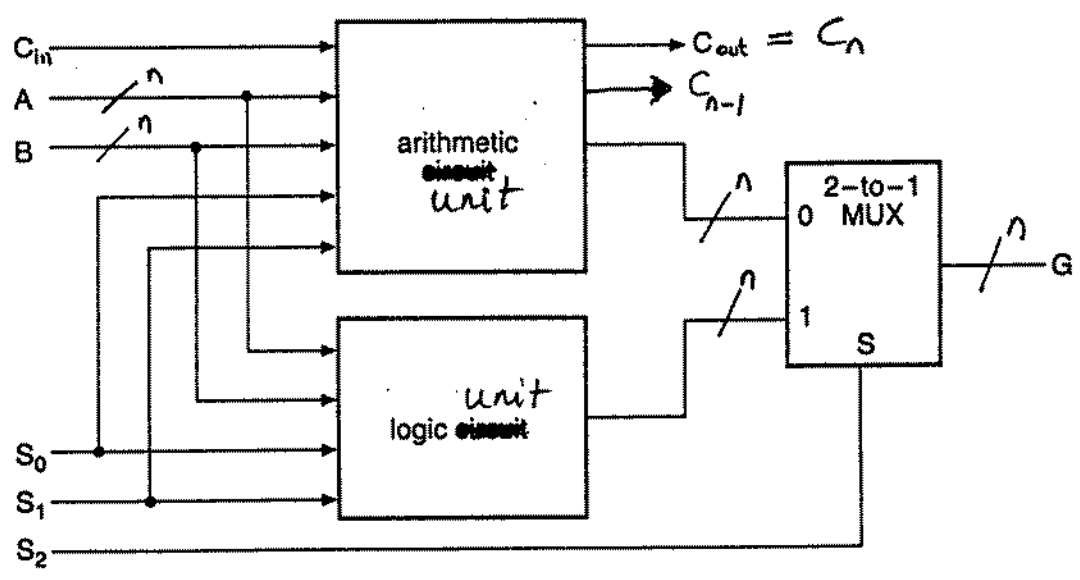$S_2 = 0 \Rightarrow$ Arithmetic unit
 $S_2 = 1 \Rightarrow$ Logic Unit




One stage of ALU ($0 \leq i \leq n-1$)





72

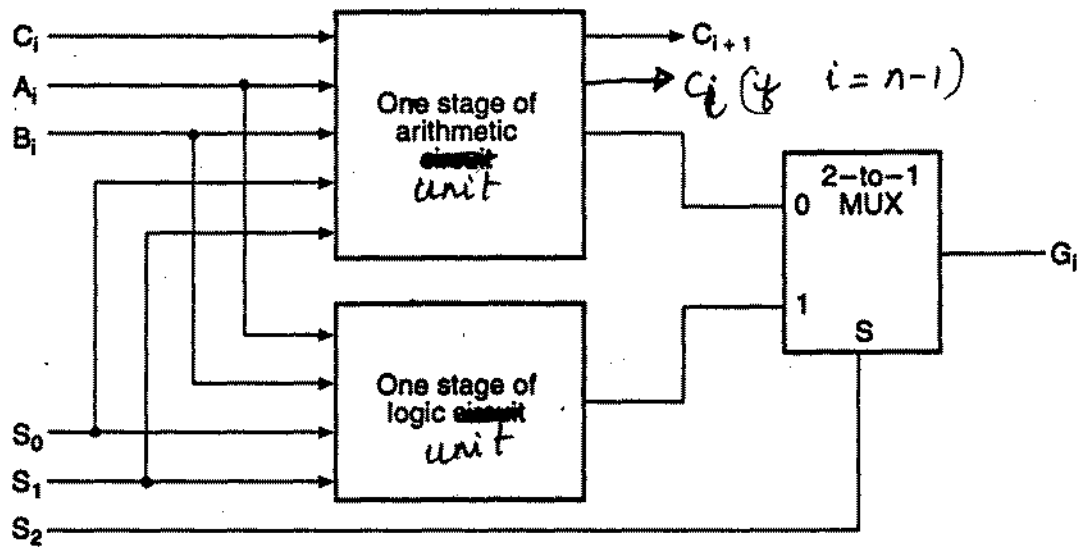

S_1	S_0	Output	Operation
0	0	$G_i = A_i \wedge B_i$	AND
0	1	$G_i = A_i \vee B_i$	OR
1	0	$G_i = A_i \oplus B_i$	XOR
1	1	$G_i = \bar{A}_i$	NOT

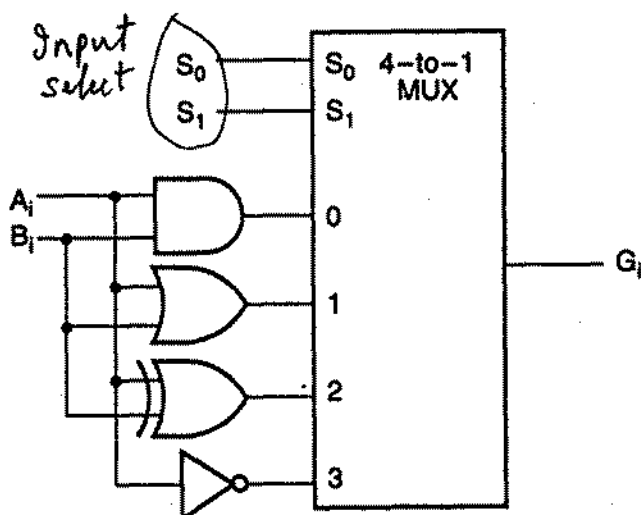


All stages of logic unit when $n=4$ 73

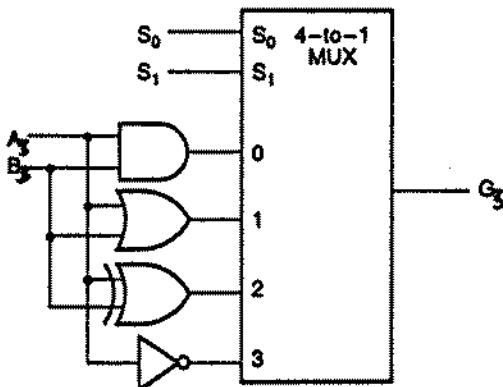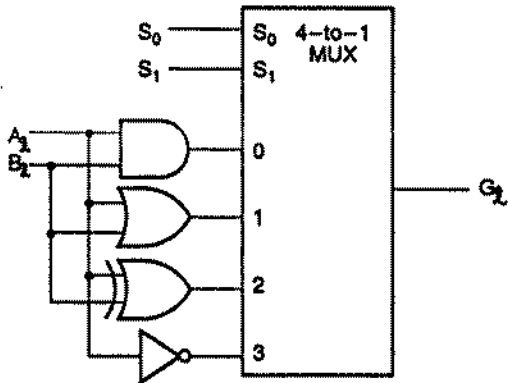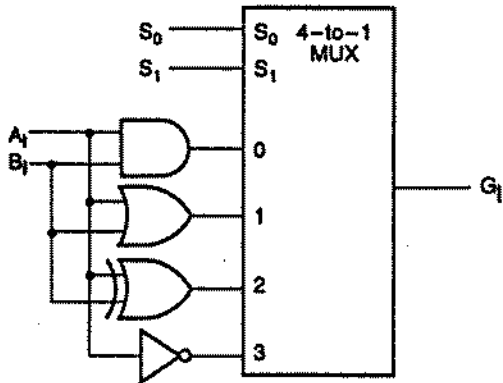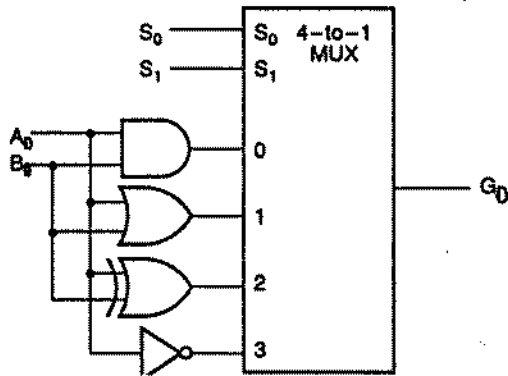

S_1	S_0	Output	Operation
0	0	$G = A \wedge B$	AND
0	1	$G = A \vee B$	OR
1	0	$G = A \oplus B$	XOR
1	1	$G = \bar{A}$	NOT

One stage of arithmetic unit


74

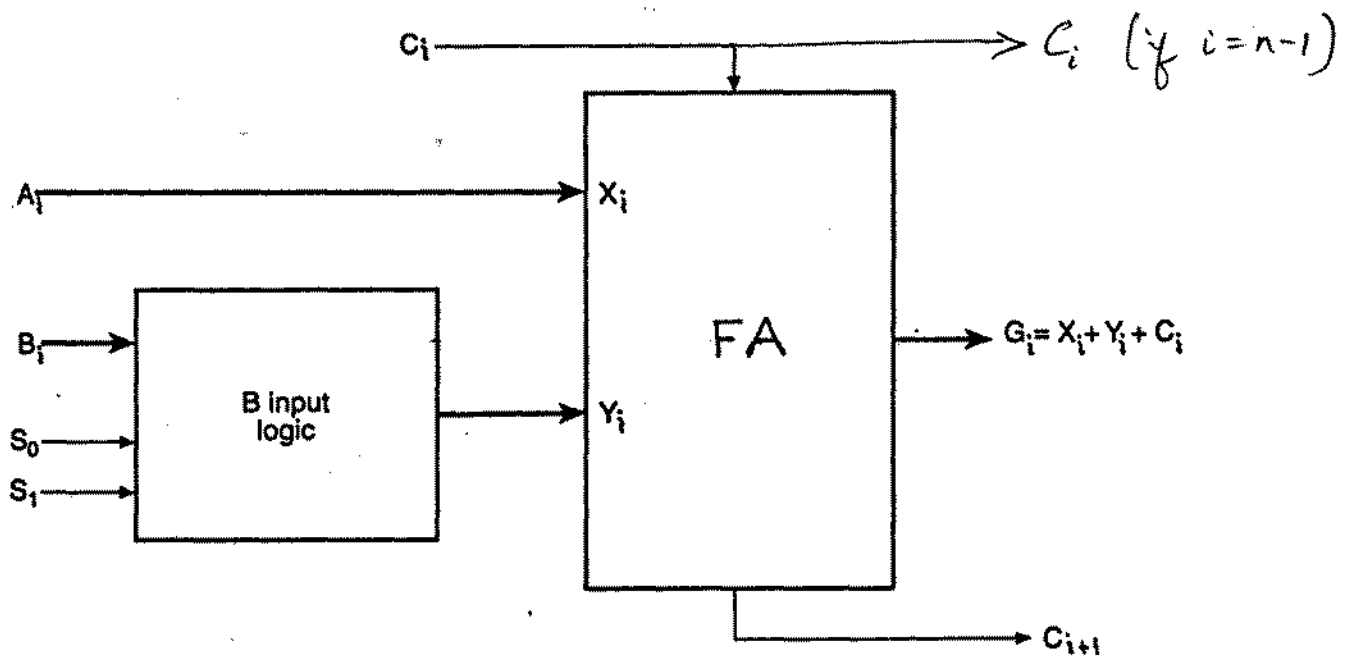

Inputs			Output	
S_1	S_0	B_i	Y_i	
0	0	0	0	$Y_i = 0$
0	0	1	0	
0	1	0	0	$Y_i = B_i$
0	1	1	1	
1	0	0	1	$Y_i = \bar{B}_i$
1	0	1	0	
1	1	0	1	$Y_i = 1$
1	1	1	1	



			S_0			
			00	01	11	10
S_1	0				1	
	1		1		1	1
			B_i			

$$Y_i = S_0 B_i + S_1 B_i'$$

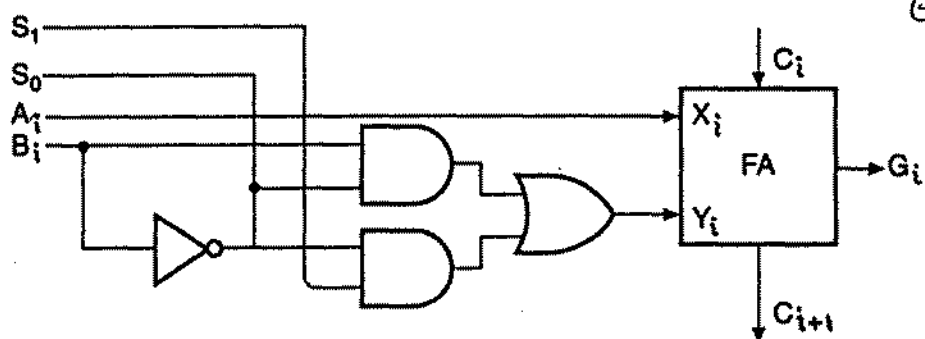


All stages of arithmetic unit when $n=4$

75

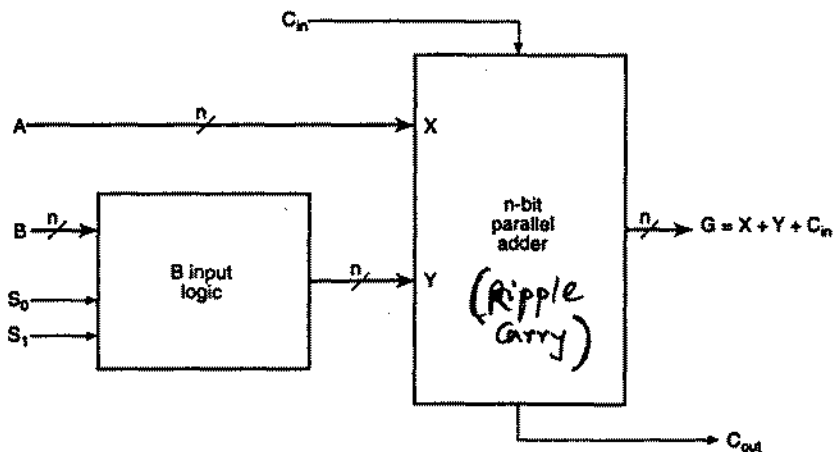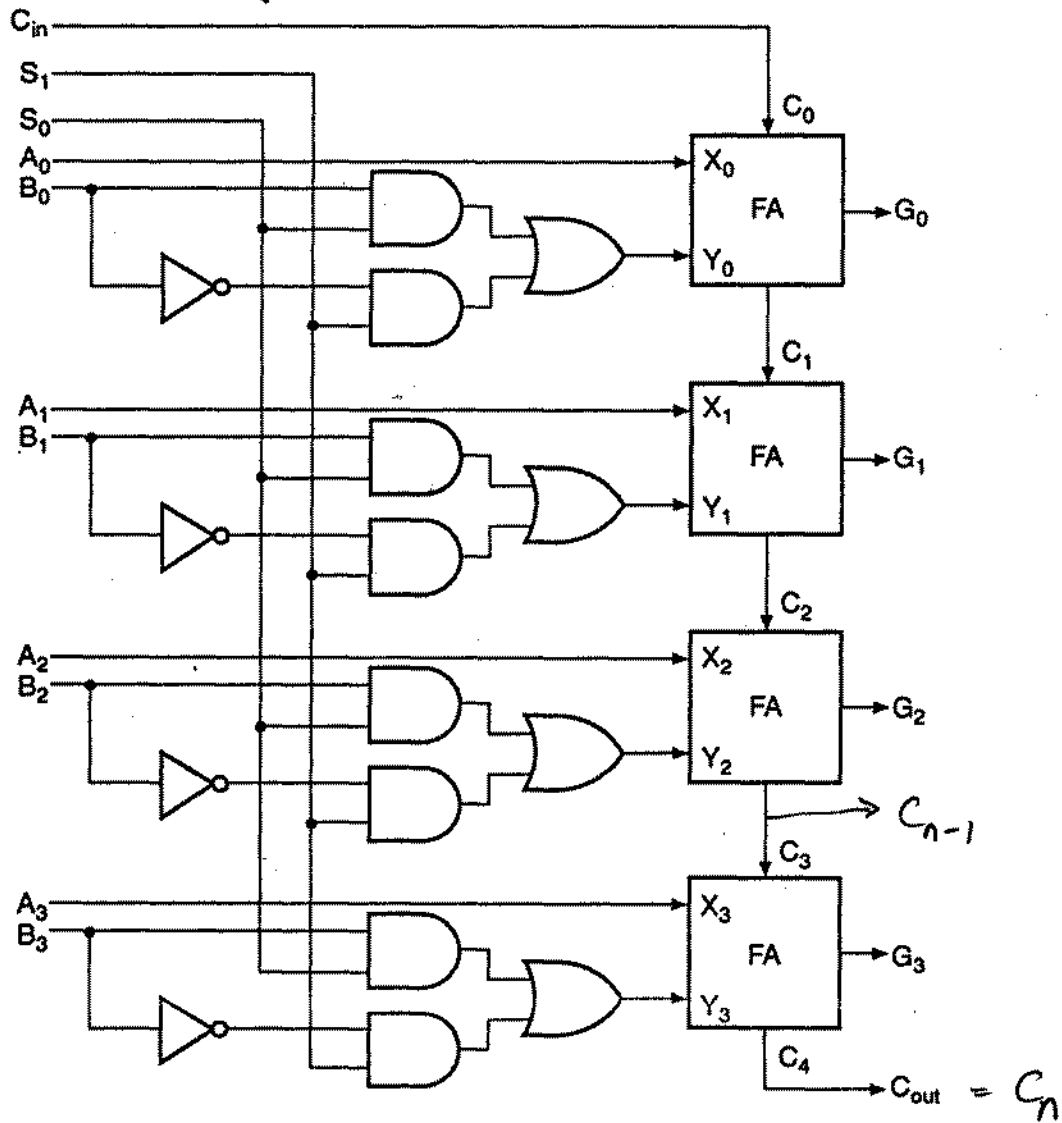

Select		Input	$G = A + Y + C_{in}$	
S_1	S_0	Y	$C_{in} = 0$	$C_{in} = 1$
0	0	all 0's	$G = A$ (transfer)	$G = A + 1$ (increment) $= A + 0 + 1$
0	1	B	$G = A + B$ (add)	$G = A + B + 1$
1	0	$\bar{B}$	$G = A + \bar{B}$	$G = A + \bar{B} + 1$ (subtract) in 2CF $(A - B)$
1	1	all 1's	$G = A - 1$ (decrement) $= A + (-1)$ in 2CF	$G = A$ (transfer) $= A + (-1) + 1$ in 2CF

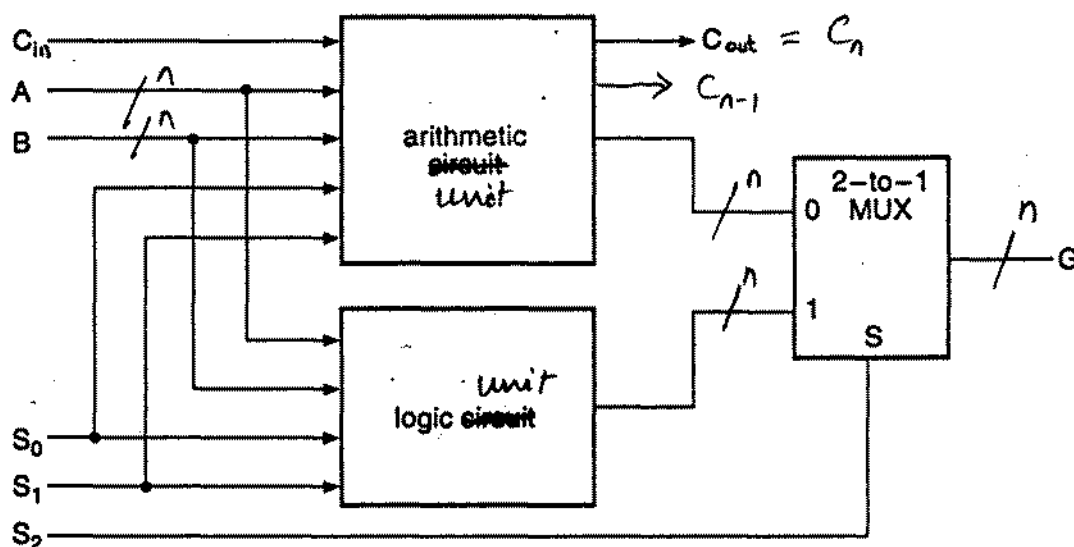

Function Table for ALU

Control Operation Select G-select

S_2	S_1	S_0	C_{in}	Operation	Function
arithmetic	0	0	0	$G = A$	Transfer A
	0	0	1	$G = A + 1$	Increment A
	0	0	1	$G = A + B$	Addition
	0	0	1	$G = A + \overline{B} + 1$	Add with carry input of 1
	0	1	0	$G = A + \overline{B}$	A plus 1's complement of B
	0	1	0	$G = A + \overline{B} + 1$	Subtraction
	0	1	1	$G = A - 1$	Decrement A
	0	1	1	$G = A$	Transfer A
logic	1	0	X	$G = A \wedge B$	AND
	1	0	1	$G = A \vee B$	OR
	1	1	0	$G = A \oplus B$	XOR
	1	1	1	$G = \overline{A}$	NOT (1's complement)

Status Bits

Overflow: $V = C_{n-1} \oplus C_n$

Carry-out: $C = C_n$

Negative: $N = G_{n-1}$

Zero : $Z = G'_{n-1} \cdot G'_{n-2} \cdots G'_1 \cdot G'_0$
 $= (G_{n-1} + G_{n-2} + \cdots + G_1 + G_0)'$