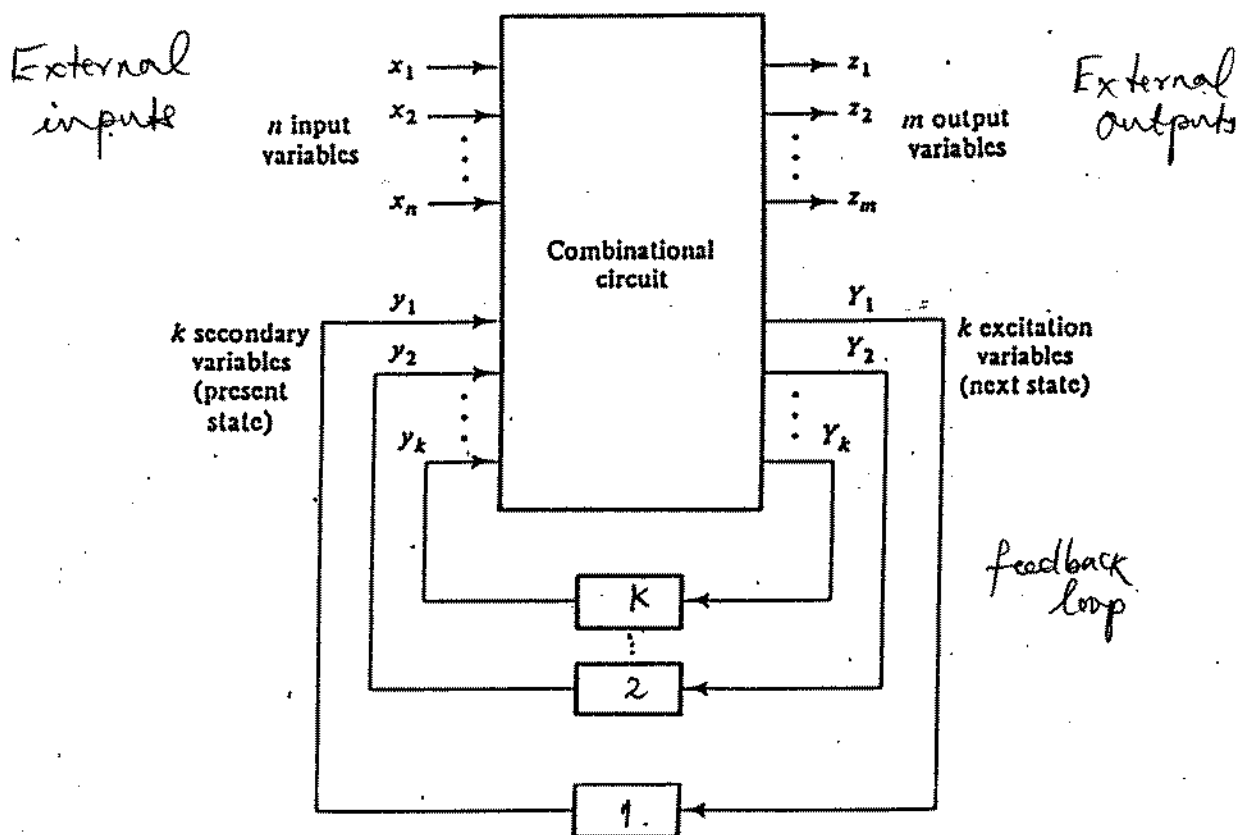


SEQUENTIAL CIRCUITS



* Content of k memory cells = **STATE** of the sequential circuit
 e.g., $k = 3 \Rightarrow [] [] []$

* Since each memory cell stores one bit (0 or 1),
 there are 2^k possible states of the sequential circuit

e.g., $k = 3 \Rightarrow 2^3$ possible states

$\Rightarrow 2^3$ possible contents of 3 memory cells

$\Rightarrow 000, 001, 010, 011, 100, 101, 110, 111$

* present content of k memory cells = PRESENT STATE $\Rightarrow y_1 y_2 \dots y_k$

* next content of k memory cells = NEXT STATE $\Rightarrow Y_1 Y_2 \dots Y_k$

* $z_i = f(y_1, y_2, \dots, y_k, x_1, x_2, \dots, x_n), 1 \leq i \leq m$


$Y_j = f(y_1, y_2, \dots, y_k, x_1, x_2, \dots, x_n), 1 \leq j \leq k$

present state external inputs

e.g.,

Every output is a function of all inputs

80

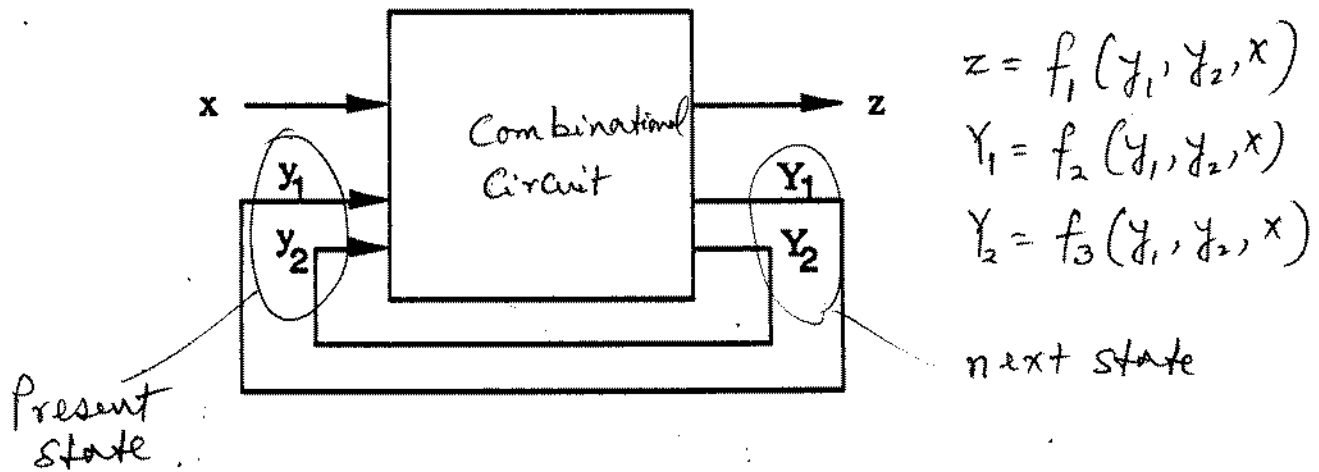

ASYNCHRONOUS SEQUENTIAL CIRCUITS


RESPONDS TO A CHANGE IN ONE OF THE INPUTS

OPERATES IN THE FUNDAMENTAL MODE:

(input signals change one at a time and only when the circuit is in a stable state)

MEMORY ELEMENTS: LATCHES

$$y_i = Y_i, 1 \leq i \leq k$$

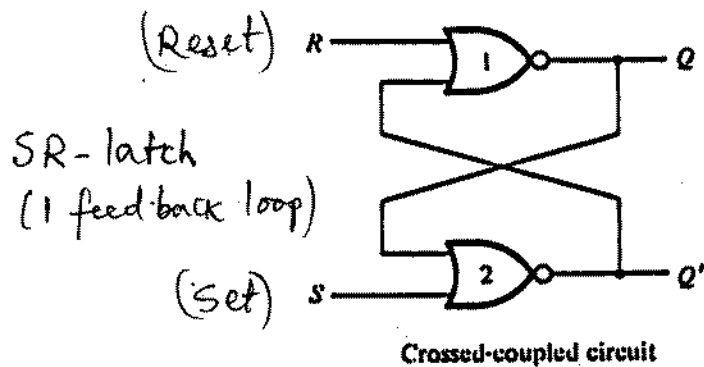

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0


Set state

(After SR = 10)

Reset state


(After SR = 01)

undefined

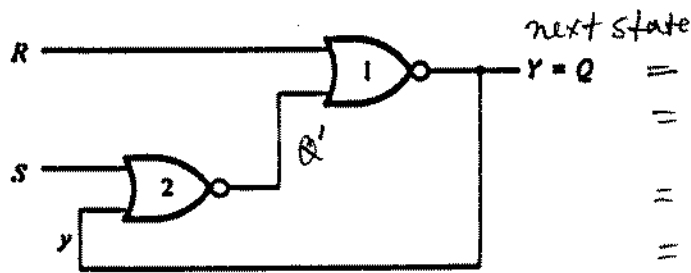

Circuit showing feedback

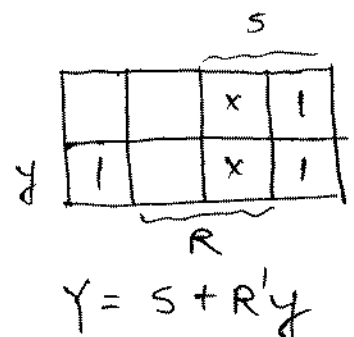
9f it is ensured that both R & S will never be 1 Then



SYNCHRONOUS SEQUENTIAL CIRCUITS

RESPONDS TO THE CLOCK PULSE (CP)
MEMORY ELEMENTS: FLIPFLOPS

RS-Flip flop

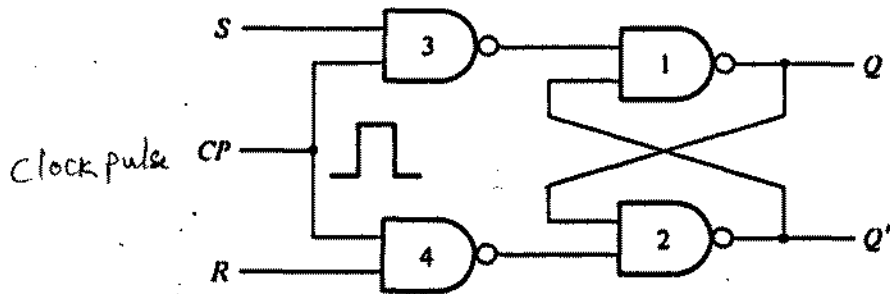

(a) Logic diagram

S	R	$Q(t+1)$		$Q(t)$	S	R	$Q(t+1)$
0	0	$Q(t)$	No change	0	0	0	0
0	1	0	Reset	0	0	1	0
1	0	1	Set	0	1	0	1
1	1	?	Unpredictable	0	1	1	Indeterminate
				1	0	0	1
				1	0	1	0
				1	1	0	1
				1	1	1	Indeterminate


(b) Characteristic tables

		S			
		00	01	11	10
Q	0			X	1
	1	1		X	1
		R			

$$Q(t+1) = S + R'Q(t) \text{ when } SR = 0$$

(c) Characteristic equation

D-Flip flop

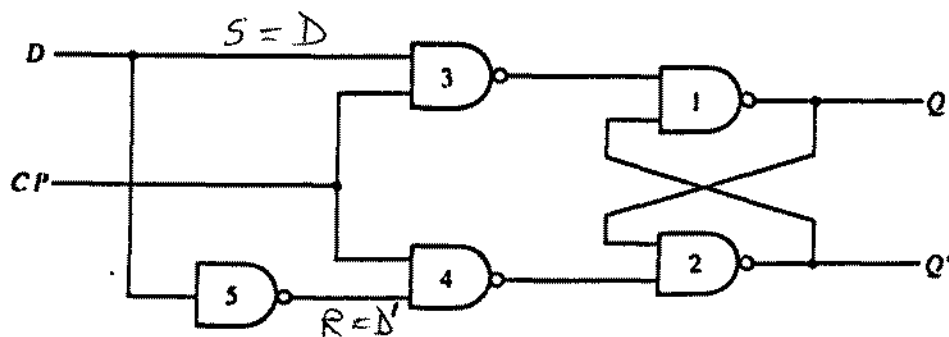

(a) Logic diagram

D	$Q(t+1)$	
0	0	Reset
1	1	Set

(b) Characteristic tables

$Q(t)$	D	$Q(t+1)$
0	0	0
0	1	1
1	0	0
1	1	1

		D	
		0	1
Q	0		1
	1		1


$$Q(t+1) = D$$

(c) Characteristic equation

JK-Flipflop

When $J=1$ & $K=1$

$$Q(t+1) = Q'(t)$$

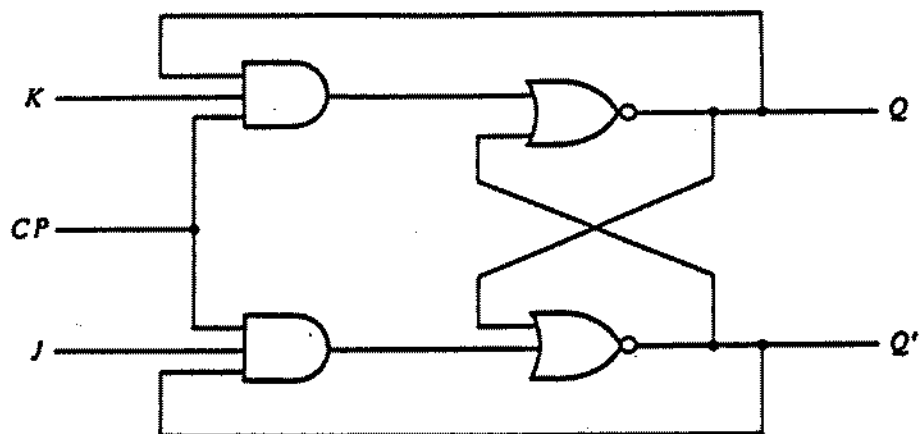

(a) Logic diagram

J	K	$Q(t+1)$
0	0	$Q(t)$ No change
0	1	0 Reset
1	0	1 Set
1	1	$Q'(t)$ Complement

$Q(t)$	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

		J			
		JK		11	10
Q		00	01		
0				1	1
1		1			1

$Q(t+1) = JQ'(t) + K'Q(t)$

(b) Characteristic tables


(c) Characteristic equation

T-Flipflop

Single input version of JK-FF.

When $T=1$,

$$Q(t+1) = Q'(t)$$

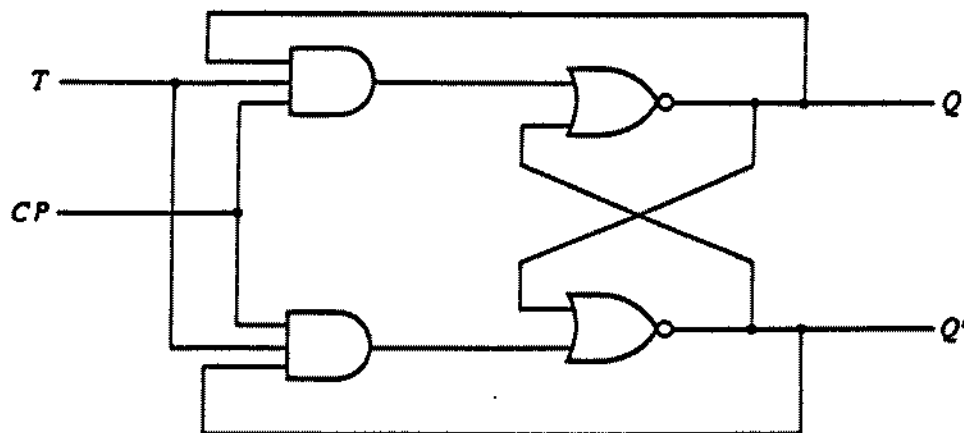

(a) Logic diagram

T	$Q(t+1)$
0	$Q(t)$ No change
1	$Q'(t)$ Complement

$Q(t)$	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

		T	
		0	1
Q			
0			1
1		1	

$$Q(t+1) = TQ'(t) + T'Q(t)$$

(b) Characteristic tables

(c) Characteristic equation

FLIP FLOP CHARACTERISTIC TABLES

Flip-Flop Characteristic Tables

JK Flip-Flop			
J	K	$Q(t+1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

RS Flip-Flop			
S	R	$Q(t+1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Unpredictable

D Flip-Flop		
D	$Q(t+1)$	
0	0	Reset
1	1	Set

T Flip-Flop		
T	$Q(t+1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Given present state & inputs, find next state
 $Q(t)$ $Q(t+1)$

FLIP FLOP EXCITATION TABLES

Flip-Flop Excitation Tables

$Q(t)$	$Q(t+1)$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

(a) RS

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

(b) JK

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

(c) D

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

(b) T

Given present state & next state, find inputs.
 $Q(t)$ $Q(t+1)$