

Chapter 4 Solutions

1.


BLF/KHz	TRcal/us	DR
640	33.33	64/3
320	66.7	64/3
	25	8
160	133.3	64/3
	50	8
80	100	8

2. Solution (in hex)

- (a) E2F0
- (b) CCAE
- (c) 968F
- (d) 78F6

3. To prevent a glitch at the clock net.

4.

 

5. The advantage is that the signal is shifted to BLF, immune to low-frequency noise. The disadvantage is that there is a lower data rate.

6.

Factors	Low power techniques
Power supply	Multi-Voltage tech., Sub-threshold tech.
Clock frequency	DET Flip-flop, Multi-clock
Activity probability	Clock-gating, operator isolation

7. Rounding methods:

[DISP]

Round to nearest; round towards zero; round down/floor; round up/ceil; round away from 0,...

[DISPX]

[FT]In the module to quantize and compute TRcal, RTcal and other parameters, the rounding method selected should guarantee that the mean quantization error introduced is zero, otherwise the BLF/decoding margin calculated will suffer a non-zero offset.

8.

[DISP]

$$P_{tag,th} = -14 \text{ dBm} = 40 \mu\text{W}. \eta = P_{load} / P_{tag,th} = 12 / 40 = 30\%.$$

[DISPX]

9. A feasible way to supply voltage generation is to have three different voltage levels of 0.65 V for Demod, clock generator and baseband, 0.85 V for RNG, POR generator, bias and regulator,

and finally 1.5 V for EEPROM.

10. M_b should be operating in the subthreshold region. During the turn-on period of this stage, the voltage drop V_{drop} on M_i equals to (in fact is a little larger than) $V_{th} - V_{GSb}$, where V_{th} is the threshold voltage and V_{GSb} is the gate-source voltage of M_b . V_{drop} needs to be close to zero to reduce the power loss on this stage. On the other hand, V_{GSb} must be smaller than V_{th} to reduce the reverse leakage current. Therefore, M_b operates in the subthreshold region.

11. In the tag system, the duty cycle of the fast clock may not be precisely equal to 50%. For example, if we use a D flip-flop, assuming the duty cycle of fast clock is 40%, the probabilities of 0 sampling and 1 sampling equal to $P(0) = 0.6$, $P(1) = 0.4$, respectively. However, T flip-flop does not have such problems. The output probability of a T-flip-flop equals

[DISP]

$$P_{n+1}(0) = P(0)P_n(0) + P(1)P_n(1) \quad (4.1)$$

$$P_{n+1}(1) = P(0)P_n(1) + P(1)P_n(0) \quad (4.2)$$

[DISPX]

[FT]where $P_n(0)$ and $P_n(1)$ are the n^{th} sample probabilities for 0 and 1, $P_{n+1}(0)$ and $P_{n+1}(1)$ are the $(n+1)^{\text{th}}$ sample probabilities for 0 and 1. By (4.1) and(4.2), we can have

[DISP]

$$P_{n+1}(0) = \frac{1}{2} \left[P(0) + P(1)^n + P(0) - P(1)^n \right] P_1(0) + \frac{1}{2} \left[P(0) + P(1)^n - P(0) - P(1)^n \right] P_1(1) \quad (4.3)$$

$$P_{n+1}(1) = \frac{1}{2} \left[P(0) + P(1)^n - P(0) - P(1)^n \right] P_1(0) + \frac{1}{2} \left[P(0) + P(1)^n + P(0) - P(1)^n \right] P_1(1) \quad (4.4)$$

[DISPX]

[FT][Since $P_n(0) + P_n(1) = 1$ and $0 < |P_n(0) + P_n(1)| < 1$, the possibilities for 0 sampling and 1 sampling in a long run are

[DISP]

$$\lim_{n \rightarrow \infty} P_{n+1}(0) = \frac{1}{2} P_1(0) + P_1(1) = 0.5 \quad (4.5)$$

$$\lim_{n \rightarrow \infty} P_{n+1}(1) = \frac{1}{2} P_1(0) + P_1(1) = 0.5 \quad (4.6)$$

[DISPX]

