

ELG4135: DGD on Op Amp Circuit

Q1 (10.22): Fourth Edition

Consider the 741 input stage as modeled in Fig. 10.6, with two additional *npn* diode-connected transistors, Q_{1a} and Q_{2a} , connected between the present *npn* and *pnp* devices, one per side. Convince yourself that the additional devices will each be biased at the same current as Q_1 to Q_4 —that is, $9.5\ \mu\text{A}$. What does R_{id} become? What does G_{m1} become? What is the value of R_{o4} now? What is the output resistance of the first stage, R_{o1} ? What is the new open-circuit voltage gain, $G_{m1} R_{o1}$? Compare these values to the original ones.

Solution:

Series connection of devices assures the same bias currents

$$R_{id} = (\beta + 1)(6r_e)$$

$$r_e = \frac{V_T}{9.5\ \mu\text{A}} = 2.63\text{K}\Omega$$

$$R_{id} = 3.17\text{M}\Omega$$

$$i_e = \frac{v_{id}}{6r_e}; i_o = 2i_e$$

$$\Rightarrow G_{m1} = \frac{i_o}{v_{id}} = \frac{2}{6r_e} = \frac{1}{3r_e} = 127\ \mu\text{A}/\text{V}$$

$$R_{o4} = r_o(1 + g_m(R_E \parallel r_x))$$

$$g_m \cong \frac{1}{r_e}$$

$$R_E = 2r_e = 5.26\text{K}\Omega$$

$$r_x = (\beta_P + 1)r_e = 134\text{K}\Omega$$

$$\text{Thus } R_{o4} = 15.4\text{M}\Omega$$

$$R_{o6} = 18.2\text{M}\Omega \text{ (from text)}$$

$$R_{o1} = R_{o4} \parallel R_{o6} = 8.34\text{M}\Omega$$

$$G_{M1} R_{o1} = 127 \times 8.34 = 1059\text{V}/\text{V}$$

See gain decreases due to negative feedback.

Q2 (D10.23)

What relatively simple change can be made to the mirror load of stage 1 to increase its output resistance, say by a factor of two?

Solution:

$$R_o = r_{o6}(1 + g_{m6}(R_2 \parallel r_{x6}))$$

-need to double the second factor

Since $r_{x6} \gg R_2$

$$R_{o6} \cong r_{o6}(1 + g_{m6}R_2)$$

$$\text{Thus } 1 + g_{m6}R_2' = 2(1 + g_{m6}R_2)$$

$$g_{m6} = \frac{1}{2.63K\Omega}, R_2 = 1K$$

$$\Rightarrow R_2' = 4.63K\Omega$$

Q3 (10.26)

Through a processing imperfection, the β of Q_4 in Fig. 10.1 is reduced to 25, while the β of Q_3 remains at its regular value of 50. Find the input offset voltage that this mismatch introduces. (*Hint*: Follow the general procedure outlined in Example 10.1.)

Solution:

Current in the collector of Q_3 remains unchanged at $9.5\mu A$

$$\text{Thus } I_{E3} = I_{E4} = \frac{51}{50} 9.5\mu A = 9.69\mu A$$

$$I_{C4} = \frac{25}{26} I_{E4} = 9.317\mu A$$

$$\Rightarrow \Delta I = 9.5 - 9.317 = 0.183\mu A$$

$$V_{os} = \frac{\Delta I}{G_{m1}} = 2r_e \Delta I = 2(2.63K\Omega)(0.183\mu A) = 0.96mV$$

Q4 (10.31)

Consider a variation on the design of the 741 second stage in which $R_8 = 50 \Omega$. What R_{i2} and G_{m2} correspond?

Solution:

$$\begin{aligned}
 R_{i2} &= (\beta + 1)[r_{e16} + R_{i17} \parallel R_9] \\
 r_{e16} &= 1.54 K\Omega \\
 r_{e17} &= 45.5 \Omega \\
 R_{i17} &= 201(45.5 + 50) = 19.2 K\Omega \\
 \Rightarrow R_{i2} &= 201(1.54 + 19.2 \parallel 50) K\Omega = 3.1 M\Omega \\
 v_{b17} &= \frac{R_{i17} \parallel R_9}{r_{e16} + R_{i17} \parallel R_9} v_{i2} = 0.9 v_{i2} \\
 i_{c17} &= \frac{\alpha}{r_{e17} + R_8} 0.9 v_{i2} \\
 \Rightarrow G_{m2} &= \frac{\alpha(0.9)}{45.5 + 50} = 9.38 mA/V
 \end{aligned}$$

Q5 (10.32)

In the analysis of the 741 second stage, note that R_{o2} is affected most strongly by the low value of R_{o13B} . Consider the effect of placing appropriate resistors in the emitters of Q_{12} , Q_{13A} , and Q_{13B} on this value. What resistor in the emitter of Q_{13B} would be required to make R_{o13B} equal to R_{o17} and thus R_{o2} half as great? What resistors in each of the other emitters would be required?

Solution:

$$\begin{aligned}
 R_{o17} &= 787 K\Omega \\
 i_{c13B} &= 550 \mu A \\
 g_{m13B} &= 22 mA/V; r_{x13B} = (\beta + 1)/g_m = 2.32 K\Omega \\
 r_o &= \frac{50}{550 \mu A} = 90.9 K\Omega \\
 R_{o13B} &= r_o (1 + g_m (R_E \parallel r_x)) = 90.9 [1 + 22(R_E \parallel 2.32)] = 787 \\
 \Rightarrow R_E \parallel 2.32 &= 0.348 \\
 \text{and } \frac{1}{R_E} &= 2.44 \text{ or } R_E = 0.410 K\Omega = 410 \Omega \\
 \text{Current } \frac{R_{E12}}{R_E} &= \frac{550 \mu A}{730 \mu A} \Rightarrow R_{E12} = 309 \Omega \\
 \frac{R_{E13A}}{R_E} &= \frac{550}{180} \Rightarrow R_{E13A} = 1.25 K\Omega
 \end{aligned}$$