

Tutorial No. 2, ELG2336, winter 2008

Problem 4.54

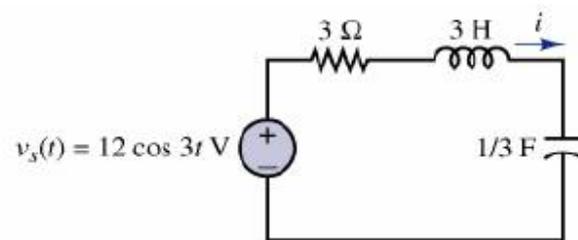


Figure 1: Problem 4.54

Known quantities:

The values of the impedance and the voltage applied to the circuit shown in Figure 1.

Find:

The current $i(t)$ in the circuit.

Analysis:

Assume clockwise current:

$$\omega = 3 \frac{\text{rad}}{\text{s}}, V_s = 12 \angle 0^\circ \text{ V}$$

$$Z_C = \frac{1}{j\omega C} = -j \Omega, Z_L = j\omega L = j9 \Omega \Rightarrow Z_{total} = 3 + j9 - j = 3 + j8 \Omega$$

$$I = \frac{12}{3 + j8} = 0.4932 - j1.3151 \text{ A} = 1.4045 \angle -69.44^\circ \text{ A}, i(t) = 1.4 \cos(\omega t - 69.4^\circ) \text{ A}$$

Problem 4.55

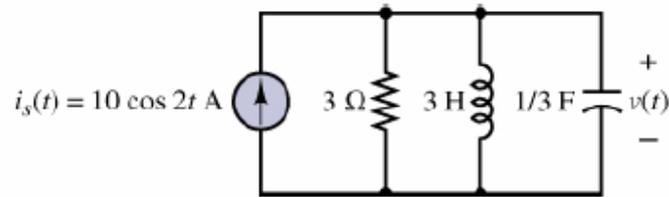


Figure 2: Problem 4.55

Known quantities:

The values of the impedance and the current source shown in Figure 2

Find:

The voltage $v(t)$

Analysis:

Assume clockwise currents:

$$\omega = 2 \frac{\text{rad}}{\text{s}}, I_S = 10 \angle 0^\circ \text{ A}, Z_L = j\omega L = j9 \Omega, Z_C = \frac{1}{j\omega C} = -j\omega 1.5 \Omega$$

$$Z_{eq} = \frac{1}{\frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C}} = \frac{1}{\frac{1}{3} + j\frac{1}{6} + j\frac{2}{3}} = \frac{1}{0.33 + j0.5} = 0.9231 - j1.3846 \Omega$$

$$V = I_S Z_{eq} = 10 \text{ A} \cdot (0.9231 - j1.3846) \Omega = 9.231 - j13.846 \text{ V} = 16.641 \angle -56.31^\circ \text{ V}$$

Problem 4.56

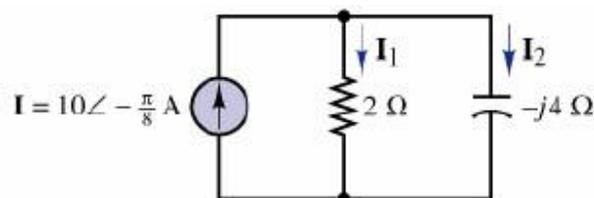


Figure 3: Problem 4.56

Known quantities:

The value of the impedance and the current source for the circuit shown in Figure 3.

Find:

The current I_1

Analysis:

Specifying the positive directions of the currents as in Figure 3:

$$Z_{eq} = \frac{1}{\frac{1}{2} + \left(\frac{1}{-j4}\right)} = 1.79 \angle 26.56^\circ \Omega$$

$$V_S = I_S Z_{eq} = (10 \angle -22.5^\circ) \text{ A} \cdot (1.79 \angle 26.56^\circ) \Omega = 17.9 \angle 4.06^\circ \text{ V}$$

$$I_1 = \frac{V_S}{R} = 8.95 \angle 4.06^\circ \text{ A}$$

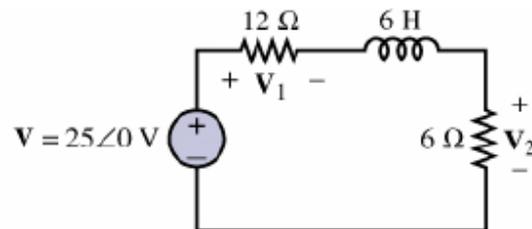
Problem 4.57

Figure 4: Problem 4.57

Known quantities:

The values of the impedance and the voltage source for circuit shown in Figure 4.

Find:

The voltage V_2

Analysis:

Specifying the positive directions as in Figure 4:

$$Z_L = j\omega L = j12 \Omega$$

$$V_2 = \frac{R_{6\Omega}}{R_{12\Omega} + Z_L + R_{6\Omega}} V = \frac{6\Omega}{(12 + j12 + 6)\Omega} 25 \angle 0^\circ \text{ V} = \frac{150 \angle 0^\circ}{18 + j12\Omega} \text{ V} = 6.93 \angle -33.7^\circ \text{ V}$$

Problem 4.60

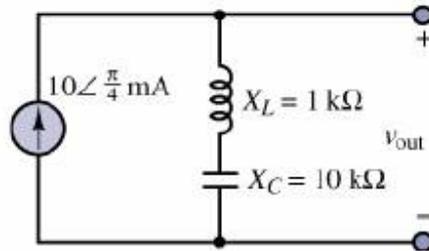


Figure 5: Problem 4.60

Known quantities:

The values of the reactance $X_L = 1 \text{ k}\Omega$, $X_C = 10 \text{ k}\Omega$, and the current source $I = 10\angle 45^\circ \text{ mA}$ for circuit shown in Figure 5.

Find:

The voltage V_{out}

Analysis:

Specifying the positive directions of the currents as in Figure 5:

$$V_{out} = Z_{eq} I = (Z_L + Z_C) I = (0 + jX_L + 0 - jX_C) I = (j1 \text{ k}\Omega - j10 \text{ k}\Omega) \cdot 10\angle 45^\circ \text{ mA}$$

$$\Rightarrow V_{out} = (-j9 \text{ k}\Omega) \cdot 10\angle 45^\circ \text{ mA} = (9\angle -90^\circ \text{ k}\Omega) \cdot 10\angle 45^\circ \text{ mA} = 90\angle -45^\circ \text{ V}$$

$$v_{out} = 90 \cos(\omega t - 45^\circ) \text{ V}$$