ELG2336 Test 2

Number

Name:

Print and bring it to the classroom.

Question 1 (3 marks):



Question 2 (2 marks): What is the full-load speed of a 200 V shunt DC motor that requires a full-load current of A. The armature resistance of the motor is 0.2 Ω and the field resistance is 120 Ω . At no load the motor takes A to run a speed of rpm.