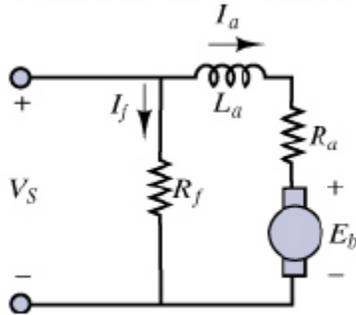


## ELG2336: Tutorial on Electric Machines

### Problem 1

A 200 V DC shunt **motor** with an armature resistance is  $0.1 \Omega$  and series field resistance of  $100 \Omega$ . The speed is 1100 rpm at an input current of 4 A (no load). Find the induced voltage  $E_b$  and the output power at 1100 rpm.

Solution:



Solution:

$$i_S = 4 \text{ A} \quad i_f = \frac{200}{100} = 2 \text{ A} \quad i_a = i_S - i_f = 2 \text{ A}$$

$$\text{Also, } E_b = 200 - 2 \times 0.1 = 199.8 \text{ V}$$

$$P = P_{in} - P_{copper\_loss} = 200 \times 4 - (2^2 \times 100 + 2^2 \times 0.1) = 399.6 \text{ W}$$

**Problem 2 (The Alternator or Synchronous Generator): This is similar to the machine used for diesel generator in the case study.**

Consider a 500 VA, 20 V diesel synchronous **generator**. At rated condition, the power factor is 0.85. The resistance per phase is  $0.05 \Omega$ . The field takes 2 A at 12 V. The friction and windage loss is 25 W while the core loss is 30 W. Find the efficiency of the generator under rated conditions.

Solution:

$$I_a = \frac{500}{20} = 25 \text{ A} \quad P_a = I_a^2 R_a = 31.25 \text{ W}$$

$$P_{out} = 500(0.85) = 425 \text{ W} \quad P_f = 2(12) = 24 \text{ W}$$

$$P_{in} = P_{out} + P_a + 25 + 30 + 24 = 535.25 \text{ W}$$

$$\% = \frac{425}{535.25} \times 100 = 79.4\%$$

### Problem 3

Consider a 230 V, 10 hp, 60 Hz, Y-connected 3-phase synchronous motor that delivers a full load at a power factor of 0.8 leading. The synchronous reactance is 6 ohm. The rotational mechanical losses are 230 W and the field losses are 50 W. Find the armature current, the motor efficiency, and the power angle.

Solution:

$$P_{out} = 10 \text{ hp} = 7460 \text{ W}$$

$$P_{in} = P_{out} + P_r + P_{copper} = 7740$$

$$V_S = \frac{230}{\sqrt{3}} = 132.8 \text{ V}$$

$$\therefore I_S = \frac{2580}{132.8 \times 0.8} = 24.3 \text{ A}$$

$$V_S = 132.8 \angle 0^\circ \text{ V}, I_S = 24.3 \angle 36.87^\circ \text{ A}$$


$$E_b = V_S - I_S(6 \angle 90^\circ) = 249.2 \angle -27.9^\circ \text{ V}$$

$$\text{efficiency} = \frac{7460}{7740} = 0.964 = 96.4\%$$

$$\text{power angle} = -27.9^\circ$$

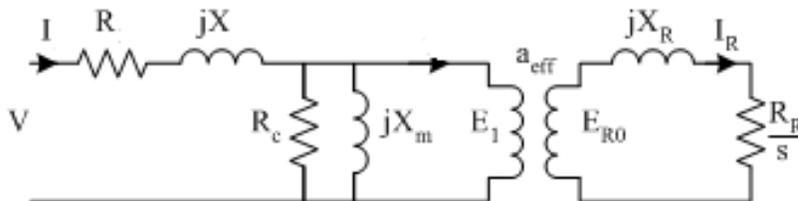**Problem 4 (The Induction Machine):** This is similar to the machine used for the wind turbine in the case study.

Consider a 74.6 kW, 440 V (this voltage is always line-to-line) Y-connected three phase, four pole, 60 Hz induction motor. The equivalent circuit parameters are:  $R_s = 0.06 \Omega$ ,  $R_R = 0.08 \Omega$ ,  $X_s = 0.3 \Omega$ ,  $X_R = 0.3 \Omega$ ,  $X_m = 5 \Omega$ . The no-load power input is 3240 W. Find the line current, the input power, and the developed torque at slip  $s = 0.02$ .



**Solution:**

$$V_S = \frac{400}{\sqrt{3}} = 254 \angle 0^\circ V$$

$$Z_{in} = 0.06 + j0.3 + \frac{j5(4 + j0.3)}{4 + j5.3} = 2.328 + j2.294 = 3.268 \angle 44.59^\circ \Omega$$

$$I_S = 77.7 \angle -44.59 A$$

$$P_{in} = 3 \times 254 \times 77.7 \cos(-44.59^\circ) = 42.16 kW$$

$$I_2 = \frac{j5}{4 + j5.3} I_S = 58.51 \angle -7.55^\circ A$$

The total power transferred to the rotor is:

$$P_T = 3 \frac{R_S}{S} |I_2|^2 = 41.1 kW$$

$$P_m = P_T - P_{copper\_loss\_in\_rotor} = 41.1 \times 10^3 (1 - s) = 40.25 kW$$

$$\omega_m = (1 - s) \omega_S = 0.98 \times 188.5 = 184.7 \text{ rad/sec}$$

$$T_{dev} = \frac{P_m}{184.7} = 218 N \cdot m = 1880.3 \angle -42.51^\circ V$$

### Problem 5

Consider a 440 V, Y-connected three phase, 6 poles, 60 Hz induction motor. The equivalent circuit parameters are:  $R_S = 0.8 \Omega$ ,  $R_R = 0.3 \Omega$ ,  $X_S = 0.7 \Omega$ ,  $X_R = 0.7 \Omega$ ,  $X_m = 35 \Omega$ . Find the input current and power factor of the motor for a speed of 1200 rpm.

**Solution:**

$$V_S = \frac{440}{\sqrt{3}} = 254 \angle 0^\circ V$$

For  $n_m = n_S = 1200 \text{ rev/min}$ ,  $s = 0$  (no load).

$$Z_{in} = R_S + j(X_S + X_m) = 0.8 + j35.7 = 35.71 \angle 88.7^\circ \Omega$$

$$I_S = 7.11 \angle -88.7^\circ A$$

$$P_{in} = 3 |I_S| |V_S| \cos \theta = 121.4 W$$