

Transmission Lines: Example Problem


A 220-kV, 150 MVA, 60-Hz, three-phase transmission line is 140 km long. The characteristic parameters of the transmission line are:

$$r = 0.09 \Omega/\text{km}; x = 0.88 \Omega/\text{km}; y = 4.1 \times 10^{-6} \text{ S}/\text{km}$$

where, r is the resistance per kilometer, x is the reactance per kilometer, y is the shunt admittance per kilometer.

The voltage at the receiving end of the transmission line is 210 kV. Although this transmission line would normally be considered a medium-length transmission line, we will treat it as short line:

- What is series impedance and shunt impedance of the transmission line?
- What is the sending end voltage if the line is supplying rated voltage and apparent power at 0.85 PF lagging? At unity PF? At 0.85 PF leading?
- What is the voltage regulation of the transmission line for each of the cases in (b)?
- What is the efficiency of the transmission line when it is supplying rated apparent power at 0.85 PF lagging?

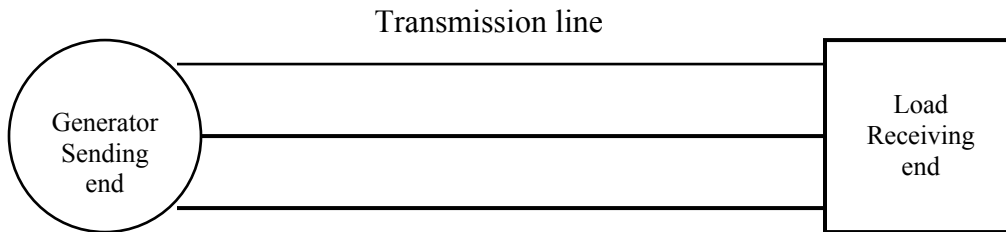

Solution:

- The series resistance, series reactance, and shunt admittance of the transmission line:

$$R = rd = (0.09 \Omega/\text{km})(140 \text{ km}) = 12.6 \Omega$$

$$X = xd = (0.88 \Omega/\text{km})(140 \text{ km}) = 123.2 \Omega$$

$$Y = yd = (4.1 \times 10^{-6} \text{ S}/\text{km})(140 \text{ km}) = 5.74 \times 10^{-4} \text{ S}$$

- The current out of this transmission line is given by. Note that the per-phase equivalent circuit implicitly assumes a wye (Y) connection, so the current is the same in phase or line configuration.

$$S_{out} = \sqrt{3} V_L I_R$$

$$I_R = \frac{S_{out}}{\sqrt{3} V_L} = \frac{150 \text{ MVA}}{\sqrt{3} \times 210 \text{ kV}} = 412 \text{ A}$$

The phase voltage of the transmission line is

$$V_R = \frac{210 \text{ kV}}{\sqrt{3}} = 121 \text{ kV}$$

Since the transmission line is considered as “short”, the admittance (or shunt capacitance) may be ignored. This produces in a per phase transmission line model consisting of a series resistance and inductance only. The phase voltage at the sending end of the line when the power factor is 0.85 lagging will be

$$V_s = V_R + I_R R + I_R X_L$$

$$= 121 \angle 0^\circ + (412 \angle -31.8^\circ)(16.8 + j123.2) = 158.6 \angle 14.4^\circ \text{ kV}$$

The resulting line voltage at the sending end (0.85 PF lagging) is

$$V_L = \sqrt{3} \times 158.6 = 275 \text{ kV}$$

The phase voltage at the sending end of the line when the power factor is unity will be

$$V_s = VR + I_R R + I_R X_L$$

$$= 121 \angle 0^\circ + (412 \angle 0^\circ)(16.8 + j123.2) = 137.6 \angle 21.6^\circ \text{ kV}$$

The resulting line voltage at the sending end (unity PF) is

$$V_L = \sqrt{3} \times 137 = 238 \text{ kV}$$

The phase voltage at the sending end of the line when the power factor is 0.85 leading

$$V_s = VR + I_R R + I_R X_L$$

$$= 121 \angle 0^\circ + (412 \angle 31.8^\circ)(16.8 + j123.2) = 110.5 \angle 25.0^\circ \text{ kV}$$

The resulting line voltage at the sending end (0.85 leading) is

$$V_L = \sqrt{3} \times 110.5 = 191 \text{ kV}$$

The voltage regulation of a transmission line is given by

$$V_R = \frac{V_{nl} - V_{fl}}{V_{fl}} \times 100$$

- The voltage regulation at 0.85 PF lagging; PF unity; and 8.5 PF leading:

$$V_R = \frac{275 - 210}{210} \times 100 = 31.1\%$$

$$V_R = \frac{238 - 210}{210} \times 100 = 13.7\%$$

$$V_R = \frac{191 - 210}{210} \times 100 = -8.7\%$$

- The output power from the transmission line at 0.85 PF lagging

$$\begin{aligned} P_{out} &= 3V_R I_R \cos \theta_R \\ &= 3 \times 121 \times 412 \times 0.85 = 127 \text{ kW} \end{aligned}$$

The input power from the transmission line

$$\begin{aligned} P_{in} &= 3V_S I_S \cos \theta_S \\ &= 3 \times 158.6 \text{ kV} \times 412 \times \cos(14.4 - (-31.8)) = 135.7 \text{ kW} \end{aligned}$$

The transmission line efficiency at full load and 0.85 PF lagging is

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{127 \text{ kW}}{135.7 \text{ kW}} \times 100\% = 93.6\%$$