

Introduction to Power Systems


Expensive! Influential! Intrusive!

Source: Riadh W. Y. Habash, Electromagnetic Fields and Radiation, Marcel Dekker, New York, 2001.


- In North America, power systems operate at a frequency of 60 Hz. However, power companies in Europe, Asia, and many other places in the world supply residential users with 50 Hz electrical powers.
- Aircraft electrical systems use 400 Hz power. Some electric trains use DC. Some high-speed electric trains use 16.67 Hz power.
- Electric commuter trains use 25 Hz electric powers and may have fields as high as 0.5 G.

The electric power network is operated at several voltage levels. This figure shows a simple power system with typical voltage levels from generation to consumption.

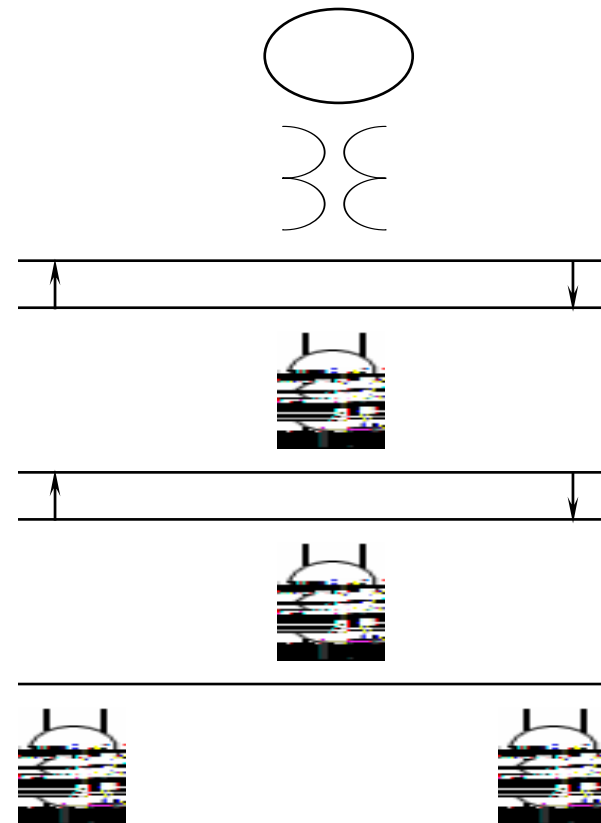- Generation (11-33 kV)
- Transmission (138-765 kV)
- Sub-transmission (23-138 kV)
- Distribution (4.16-34.5 kV)
- Utilization (240-480 V)




Actual Electric Utility System

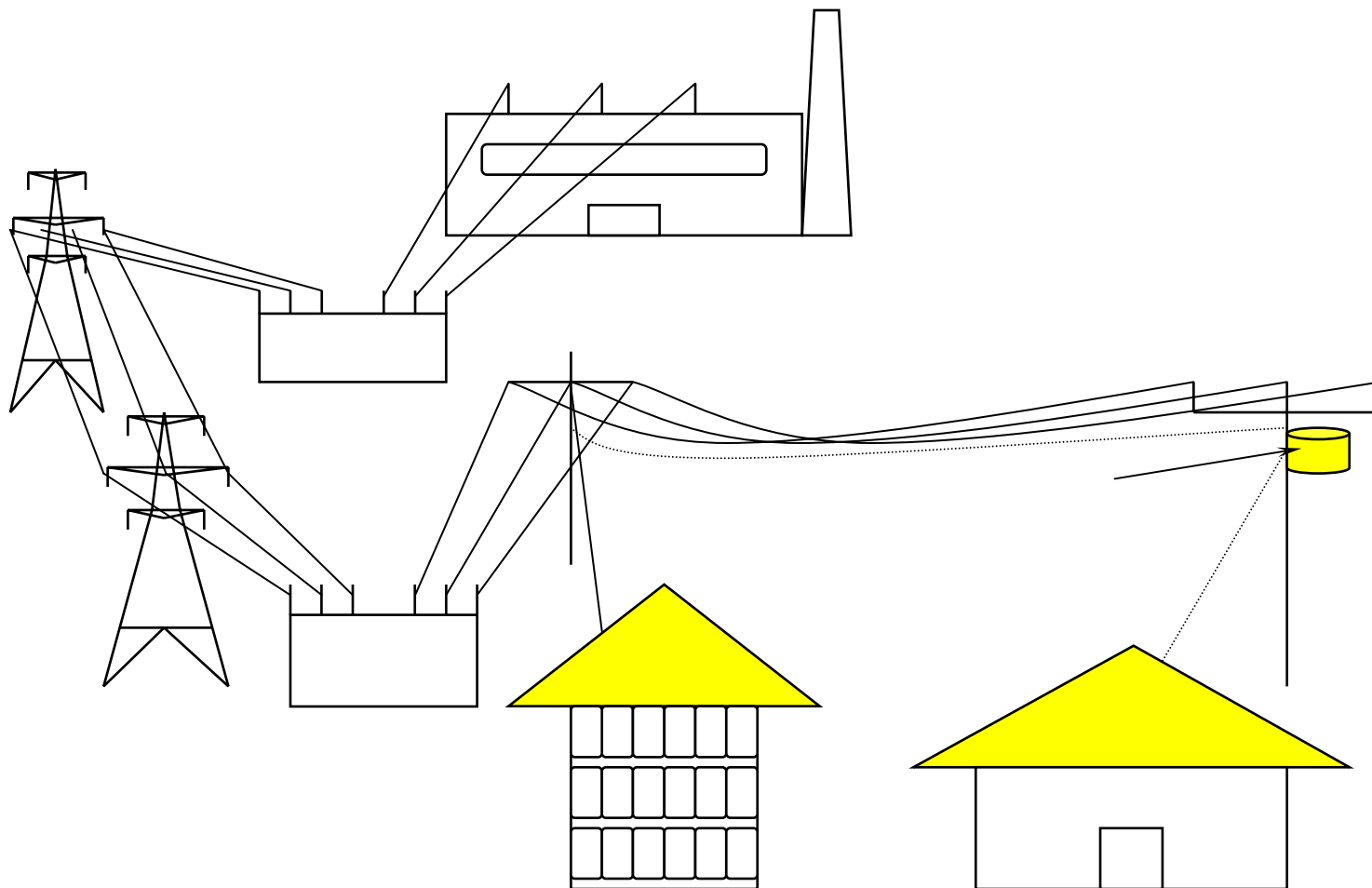

Generation and Transmission

- Electricity is typically generated at voltage levels ranging from 11 to 33 kV for three-phase synchronous generators.
- The output voltage of the generator is stepped up to transmission levels in the generating plant substation.
- Usually, power is transferred on transmission lines at a very high voltage in order to reduce energy losses along the way (the higher the voltage, the lower the losses).
- Transmission voltages typically range from 138 to 765 kV. Currently available are higher voltage overhead transmission lines for up to 1100 kV.

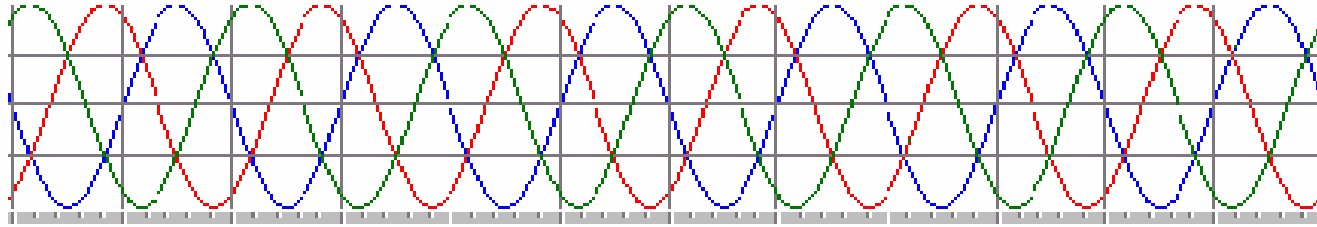

- The three-phase four-wire standard system is common for AC supply. The supply is standard at 50/60 Hz. There are three live conductors, each called the *phase* or *line*.
- The phase means the relationship of two waveforms with respect to time.
- The voltage between any of these three phases is usually 415 V. If a neutral conductor is grounded, then the voltage between any phase conductor and the neutral will be 240 V. Supplies to premises are always connected to different phases to balance the load.


Single Phase and Three Phase Systems

- If the user is a small one, a house for example, the supply cable will have two conductors, live and neutral. The supply voltage is usually 240/120 V, and such configuration is known as single-phase two-wire system.
- The single-phase supply is the most common supply for domestic premises and other single-occupier premises where the demand for energy is relatively small.
- Larger consumers receive three-phase four-wire supplies. The higher voltage is generally used for motors and heavy loads. Other small loads are connected across the outers and the neutral in such a way that when the whole installation is operating, the load across the three phases is reasonably balanced.

Substations!

They serve many functions in controlling and transferring power on electric systems. Several substation layouts are used by electric utilities to achieve reliable system operation. Some of these layouts are used in large commercial and industrial power systems.

- Substations are main components in the power transmission system, which adjust levels of electricity and thereby provide a link with the electricity supply.
- A substation is an assemblage of circuit breakers, disconnecting switches, and transformers designed to change and regulate the voltage of electricity. Power lines carrying high voltages bring the current from the power plant to the substation, where transformers reduce it to lower voltages.

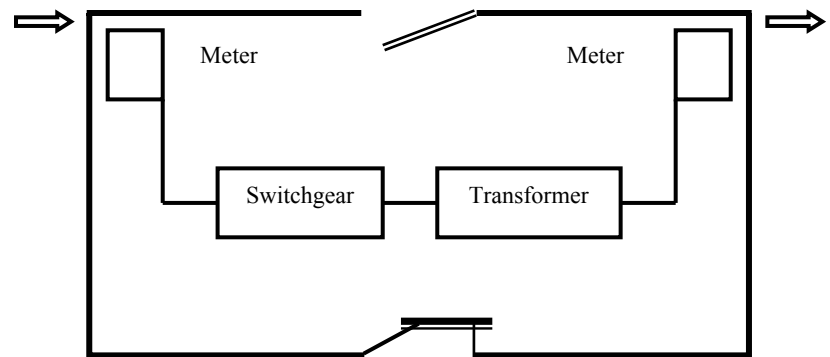


Power Lines!

Overhead power lines are the cheapest method of carrying electrical power. They are usually constructed as parallel wires, which conduct lots of power

very efficiently, but radiate very little.

- Power lines include transmission lines (mounted on large metal towers) and distribution lines (mounted on concrete or wood poles placed on the road reserve).
- Transmission lines carry electricity over long distances and operate at different amounts of voltages and currents, usually above 100 kV.
- Distribution lines operate at lower voltages and bring power from substations to businesses and homes.


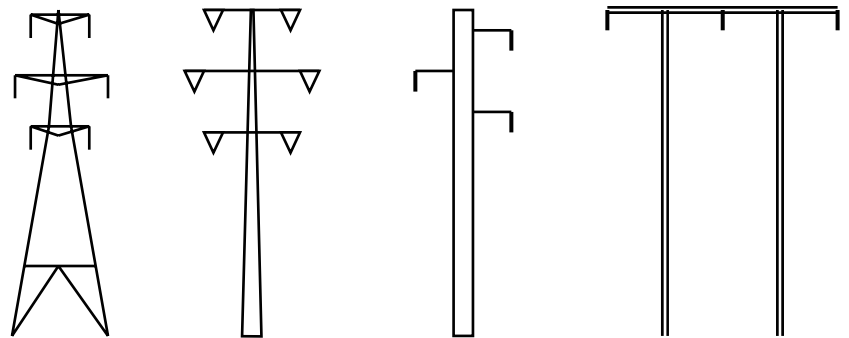




See the three lines hanging from a power line!



From Distribution Lines to Houses via Transformers

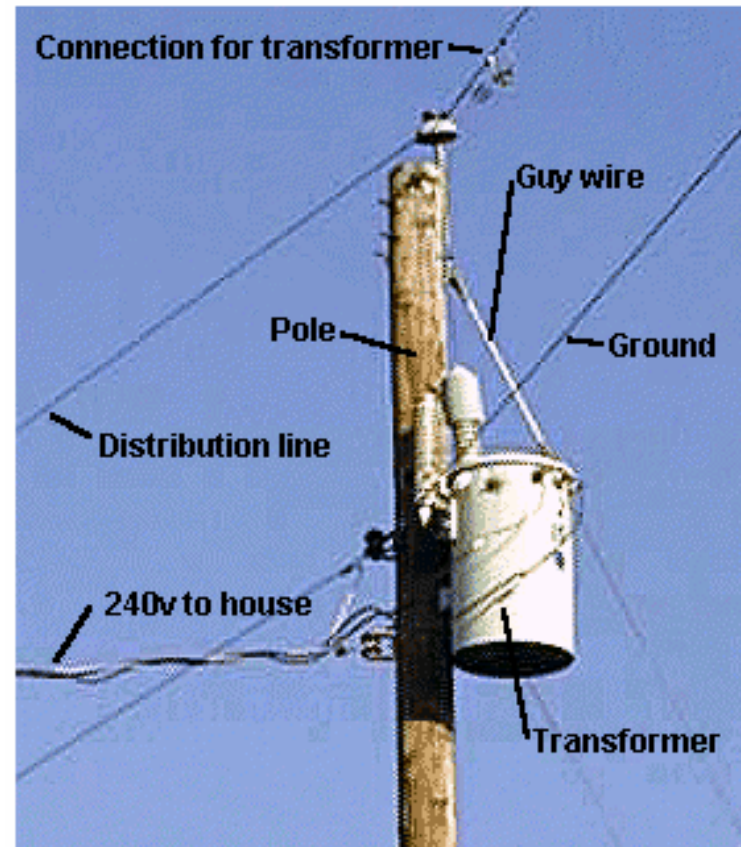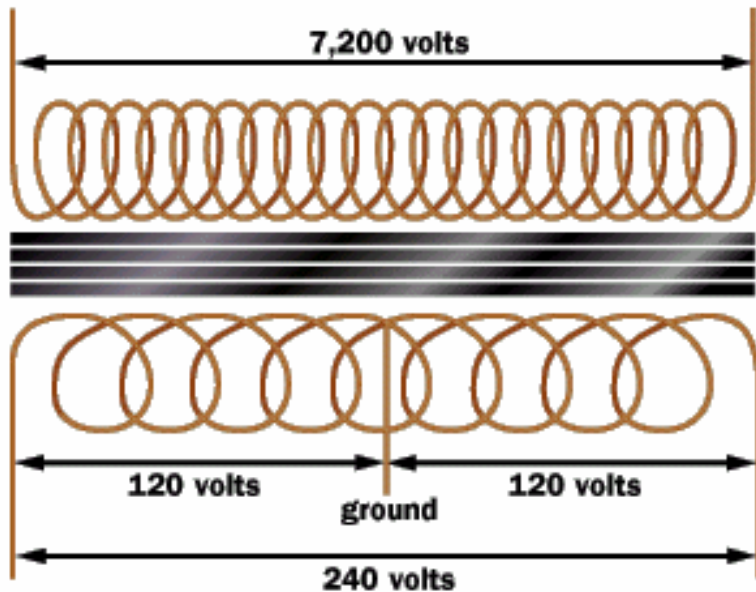Source: <http://howstuffworks.lycoszone.com/power5.htm>



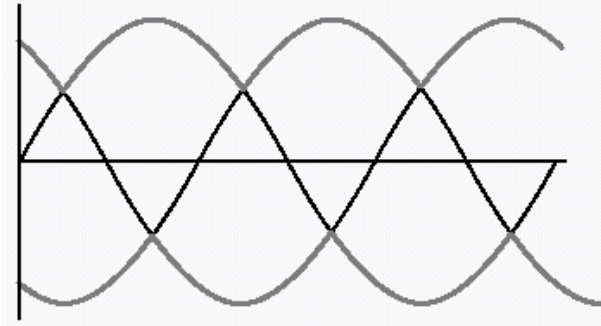
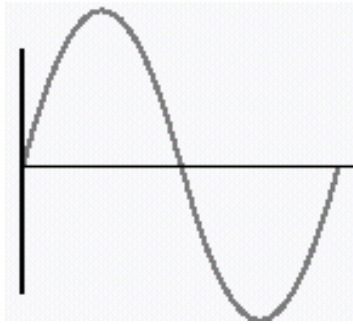


Why Three Phase Circuits!

- Higher Ratings (horsepower and KVA).
- The power delivered by a single-phase system falls to zero three times during each cycle. However, the power delivered by a three-phase circuit never falls to zero.
- In a balanced three-phase system, the conductors need be only about 75% the size of conductors for single-phase two-wire system.

Single- and Three-Phase Voltage

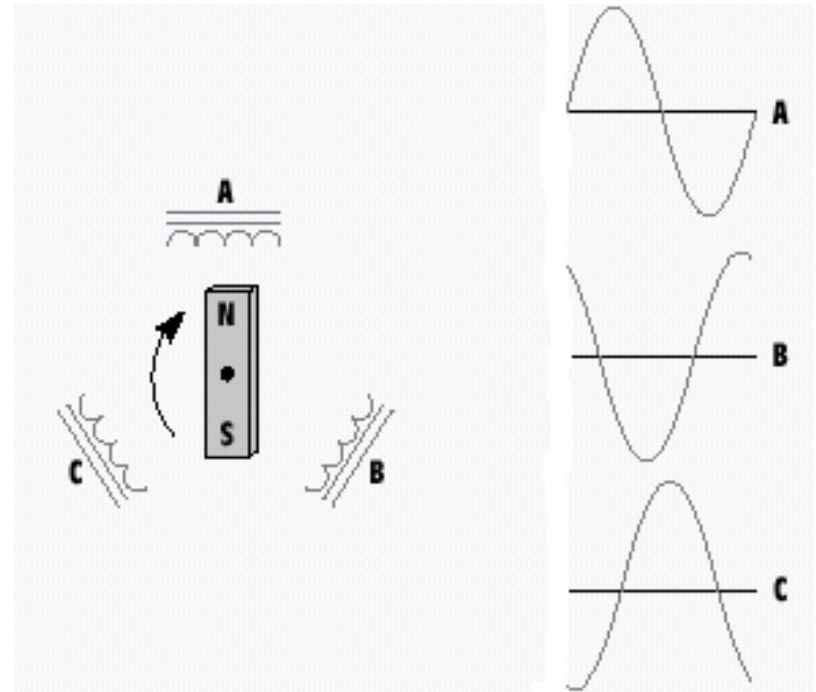
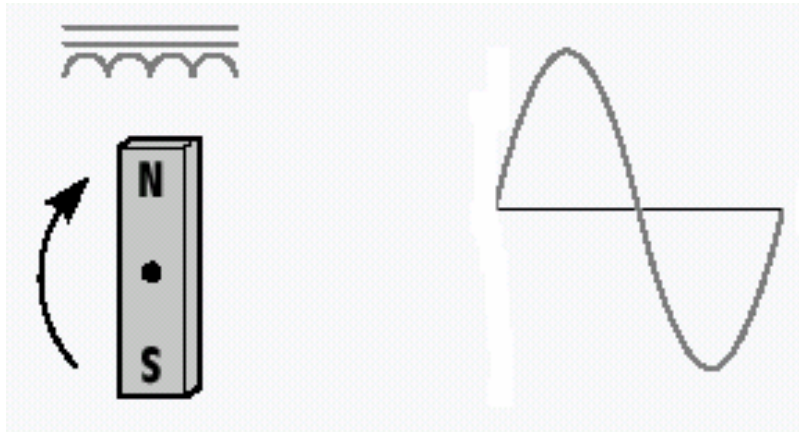
Source: Stephen Herman, Electric Circuits for Trades, Thomas Learning.



WYE (Star) Connection

$$V_{line} = \sqrt{3} V_{phase}$$


$$I_{line} = I_{phase}$$

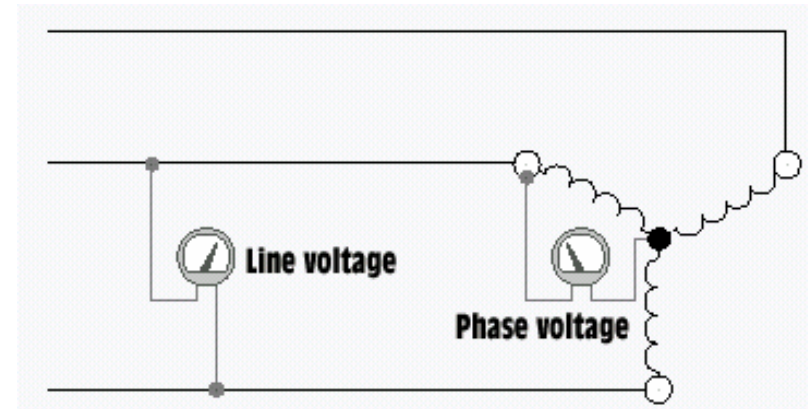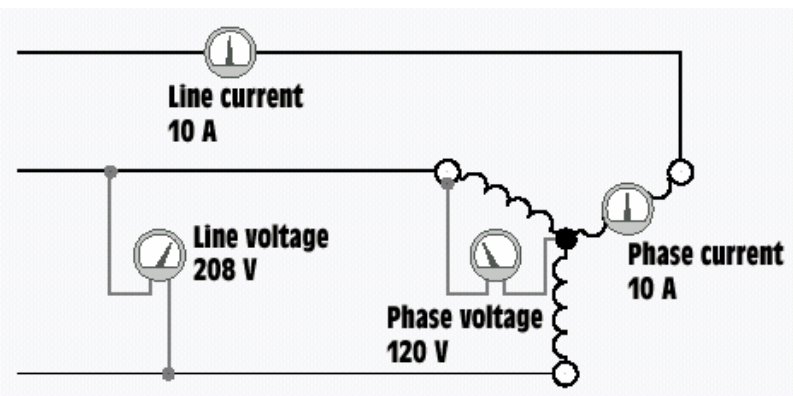

Delta Connection

$$V_{Line} = V_{Phase}$$

$$I_{Line} = \sqrt{3}I_{Phase}$$

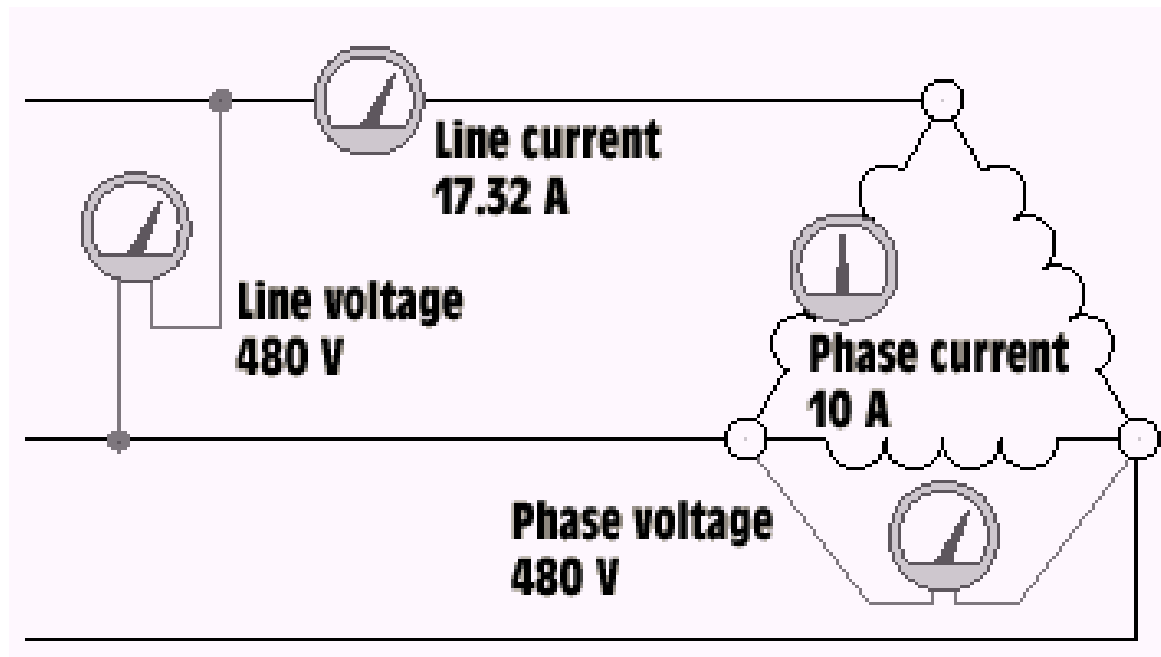

Example 1: A Y-connected three phase generator (line voltage of 480 V) supplies power to a delta-connected resistive load (8 Ω each). Find $E_{L(\text{load})}$, $E_{P(\text{load})}$, and $I_{P(\text{load})}$, $I_{L(\text{load})}$, $I_{L(\text{gen})}$, $I_{P(\text{gen})}$, $E_{P(\text{gen})}$, and the true power..

$$E_{L(\text{load})} = 480 \text{ V}$$

In delta load, the phase voltage is same as the line voltage.

$$E_{P(\text{load})} = E_{L(\text{load})} = 480 \text{ V}$$

$$I_{p(\text{load})} = \frac{E_{P(\text{load})}}{Z} = \frac{480}{8} = 60 \text{ A}$$

$$I_{L(\text{load})} = 60 \times \sqrt{3} = 103.92 \text{ A}$$


$$I_{L(\text{generator})} = 60 \times \sqrt{3} = 103.92 \text{ A}$$

$$I_{P(\text{generator})} = 103.92 \text{ A}$$

$$E_{P(\text{generator})} = \frac{E_{L(\text{generator})}}{\sqrt{3}} = \frac{480}{\sqrt{3}} = 277.13 \text{ V}$$

$$P = \sqrt{3} \times E_{L(\text{generator})} \times I_{L(\text{generator})}$$
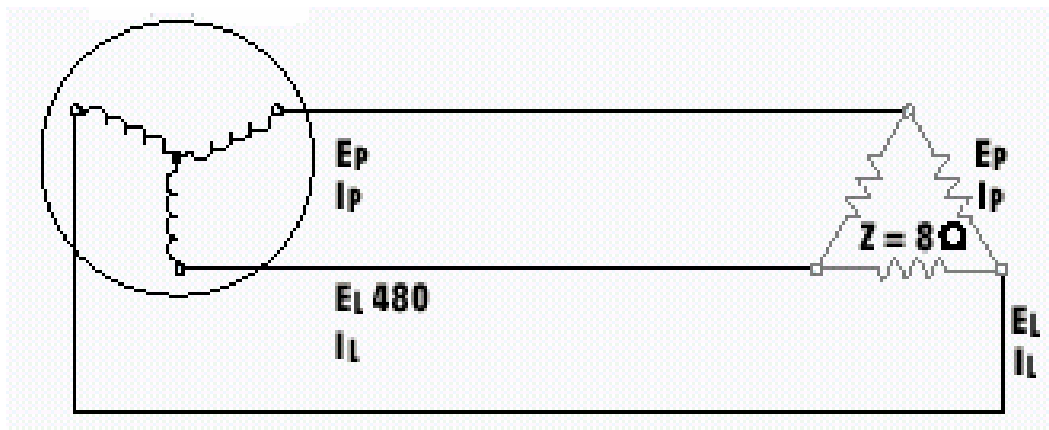
$$= \sqrt{3} \times 480 \times 103.92 = 86395 \text{ W}$$



Example 2: A delta-connected generator is connected to a Y-connected resistive load. The generator produces a line voltage of 240 V and the resistors have a value of $6\ \Omega$ each. Find, $E_{L(\text{load})}$, $E_{P(\text{load})}$, $I_{P(\text{load})}$, $I_{L(\text{load})}$, $I_{L(\text{gen})}$, $I_{P(\text{gen})}$, $E_{P(\text{gen})}$, and the true power.

$$E_{L(\text{load})} = 240\ \text{V}$$

$$E_{P(\text{load})} = \frac{240}{\sqrt{3}} = 138.57\ \text{V}$$

$$I_{P(\text{load})} = \frac{E_{P(\text{load})}}{Z} = \frac{138.57}{6} = 23.1\ \text{A}$$

$$I_{L(\text{load})} = 23.1\ \text{A}$$

$$I_{L(\text{generator})} = 23.1\ \text{A}$$

$$I_{P(\text{generator})} = \frac{I_{L(\text{generator})}}{\sqrt{3}} = \frac{23.1}{\sqrt{3}} = 13.34\ \text{A}$$

$$E_{P(\text{generator})} = 240\ \text{V}$$

$$P = \sqrt{3} \times E_L \times I_L = \sqrt{3} \times 240 \times 23.1 = 9602\ \text{W}$$

