ELG3331: Design of a Regulated Power Supply

Design a power supply that provides a DC voltage of 5 V and a current of 25 mA to a load R_L of 200 Ω . Assume the availability of 5.1-V zener diodes having $r_z = 10 \Omega$ at $I_Z = 20$ mA and the minimum current through the zener should be at least 5 mA.



Design Steps:

- The 120-V (rms) supply is stepped down to provide 12-V peak sinusoid across each of the secondary windings using a 14:1 turns ratio for the center-tapped transformer.
- The choice of 12-V is a reasonable compromise between the need to allow for sufficient voltage above the 5 V across the load R_L .
- Allow for a ripple voltage on the capacitor of 1 V.
- Accordingly, $V_{Smin} = 10.2$ V.
- We that from the requirements that $I_{Lmax} = 25$ mA.
- Also, $I_{Z\min} = 5 \text{ mA}$.
- Accordingly, current flowing through *R* should be 30 mA.
- Then, $R = 5.1 \text{ V} / 30 \text{ mA} = 170 \Omega$.
- Now we need to find the value of the capacitance C. We will use the following equation

$$V_r = \frac{V_p}{2fR_LC}$$
; and $C = \frac{V_p}{2fR_LV_r} = \frac{10.7}{2 \times 60 \times 500 \times 1} = 179 \,\mu F$

• Use safety factor of 2: then C will be around 360 μ F