


ELG4135: Assignment Based on DAC, ADC and Comparators

Problem 1

Design an alarm system that is to be set off when room temperature exceeds 50°C . Given to you are a temperature-to-voltage- transducer for which 50°C produces a voltage $v_1 = 5$ V. The alarm sounds when -15 V is applied, and it is silent when +15 V is applied.

Solution

We should provide a circuit that monitors the transducer voltage and apply the proper voltage to the alarm. We need a circuit that compares v_1 with a 5-V reference and changes its output suddenly when v_1 exceeds 5 V. Such a circuit is called a **comparator**. When v_1 exceeds 5 V, v_o falls from 15 to -15.

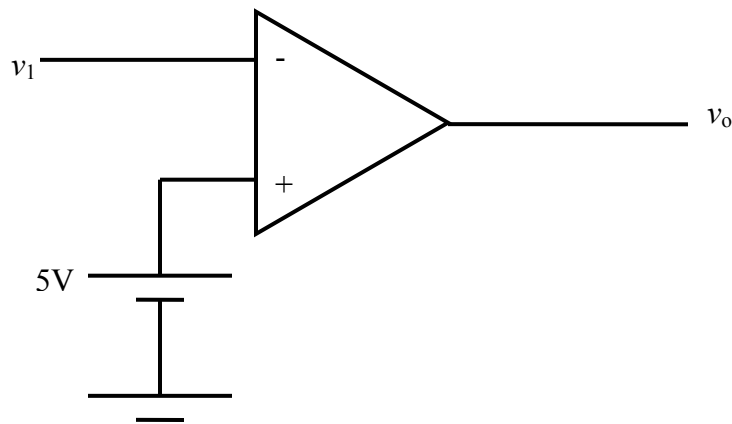


Problem 2

Design a digital-to-analog (DAC) that produces an analog output voltage v_o equal -1 V times the 4-bit number at the input.

Solution

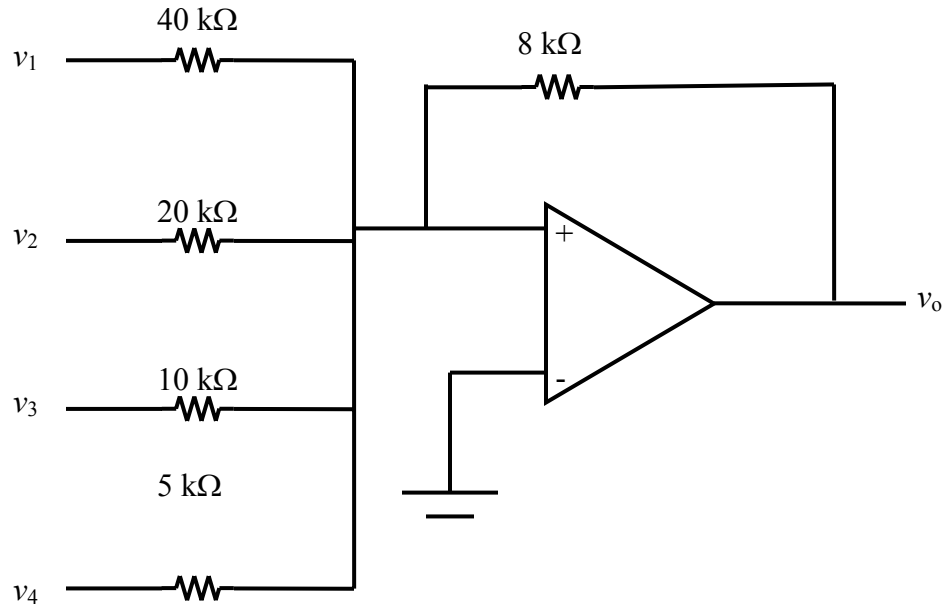The bits (least significant to most significant) are represented by v_1 , v_2 , v_3 , and v_4 . Logic 1 is represented by 5 V and logic 0 by 0 V. One possible design is shown in the following Figure.



v_4	v_3	v_2	v_1	v_o
0	0	0	0	0
0	0	0	5	-1
0	0	5	0	-2
0	0	5	5	-3
0	5	0	0	-4
0	5	0	5	-5
0	5	5	0	-6
0	5	5	5	-7
5	0	0	0	-8
5	0	0	5	-9
5	0	5	0	-10
5	0	5	5	-11
5	5	0	0	-12
5	5	0	5	-13
5	5	5	0	-14
5	5	5	5	-15

In summation, each input receives a different gain or weighting

$$v_o = -1.6v_4 - 0.8v_3 - 0.4v_2 - 0.2v_1$$

Problem 3

Draw the circuit diagram for a 4-bit DAC and determine the expression relating v_o to the binary input bits.

Problem 4

Consider the DAC given in Problem 3. What value of R_F will give the output range $-10\text{ V} \leq v_o \leq 0\text{ V}$

Problem 5

Consider the DAC given in Problem 3. What value of R_F will give the output range $-15\text{ V} \leq v_o \leq 0\text{ V}$

Problem 6

Using a DAC model. Design a 4-bit DAC whose output is given by

$$v_o = \frac{1}{10}(8b_3 + 4b_2 + 2b_1 + b_0)\text{ V}$$

Problem 7

A data acquisition uses a DAC with a range of $\pm 10\text{ V}$. and a resolution of 0.04 V . How many bits must be present in the DAC?

Problem 8

How many comparators are needed in a 4-bit flash ADC?

Problem 9

Consider the ADC (AD574) with the following specifications: $V_{CC} = 15\text{ V}$; $0 \leq V_{in} \leq 15\text{ V}$. What is the accuracy (in volts) of the AD574? What is the highest signal that can be converted by this ADC without violating Nyquist criterion if the conversion time is $35\text{ }\mu\text{s}$?

Problem 10

Sketch the input and output waveforms of a comparator with $V_{ref} = 0.8\text{ V}$.