
Second Order Parallel LCR Resonator


$$\frac{Vo}{I} = \frac{1}{Y} = \frac{1}{(1/sL) + sC + (1/R)} = \frac{s/C}{s^2 + s(1/CR) + (1/LC)}$$
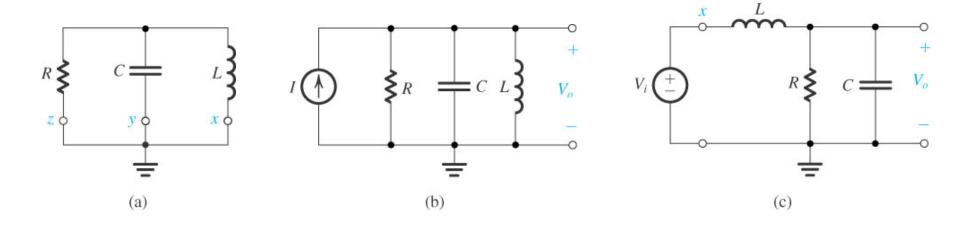
$$\omega_0^2 = 1/LC; \ \omega_0 = 1\sqrt{LC}; \ Q = \omega_0 CR$$



Second Order Filter

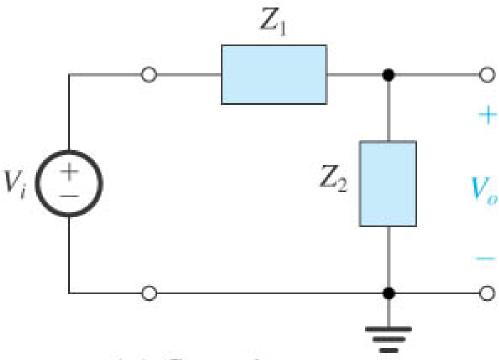
$$T(s) = \frac{V_0(s)}{V_i(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)}$$



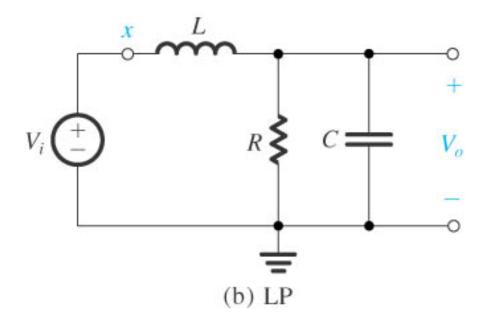
(a) General structure

Low Pass Filter

$$T(s) = \frac{1/LC}{s^2 + s(1/CR) + (1/LC)}$$




High Pass Filter

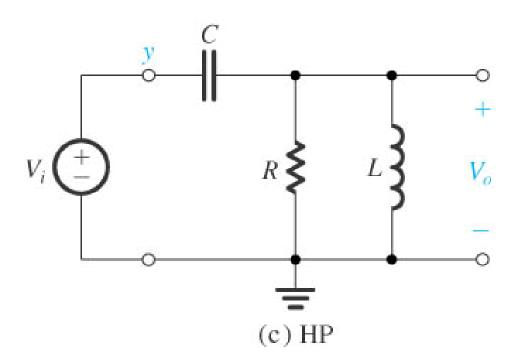


Band Pass Filter
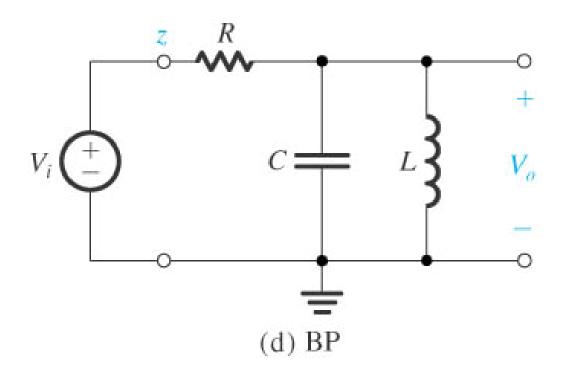
$$T(s) = \frac{s(1/CR)}{s^2 + s(1/CR) + (1/LC)}$$




Notch at ω_0
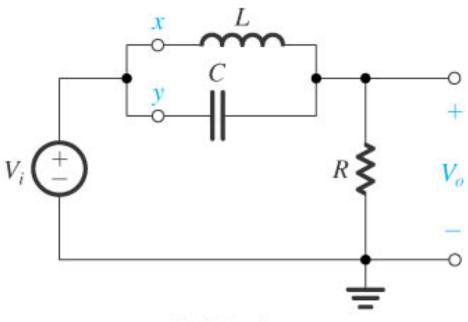
$$T(s) = \frac{s^2 + (1/L1C)}{s^2 + s(1/CR) + [1/(L_1//L_2)C]}$$




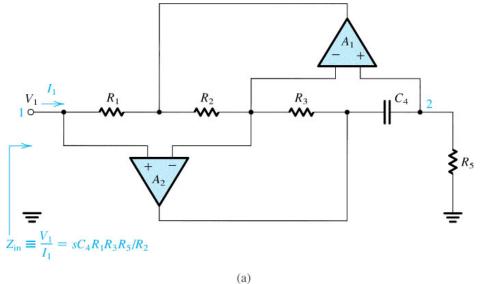(e) Notch at ω_0

Second Order Filters Based on Inductor Replacement





$$L = C_4 R_1 R_3 R_5 / R_2$$

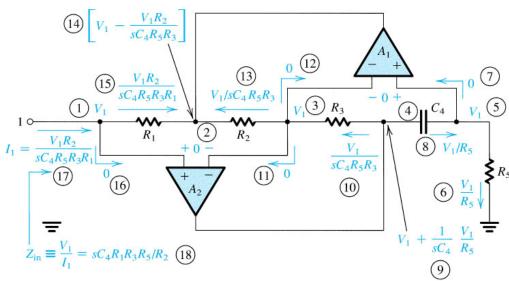



(b)

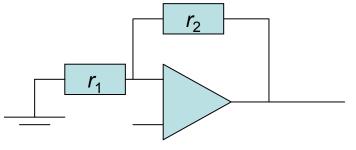An op-amp RC resonator obtained by replacing L in the LCR circuit




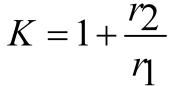

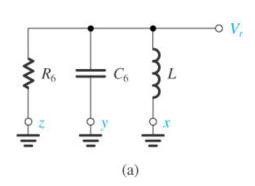


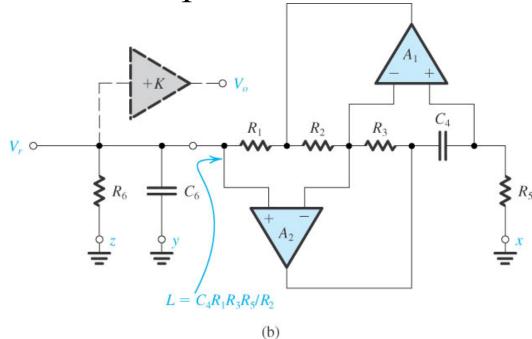

Low Pass Filter

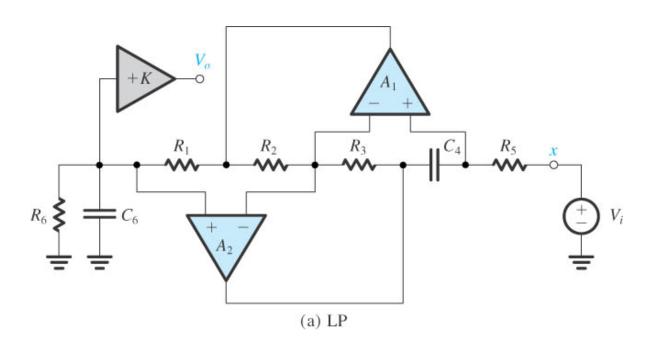

High Pass Filter

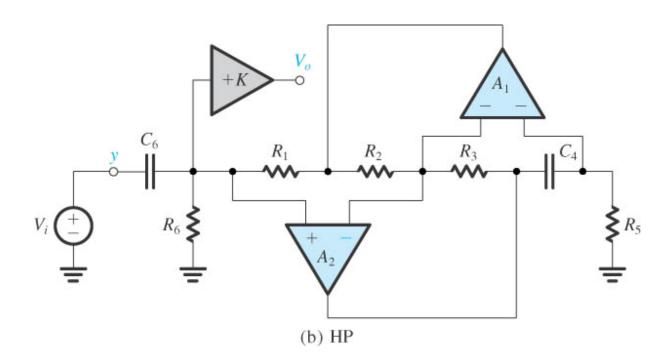

Band Pass Filter

