


OP-Amp Circuit Design

Nonlinear Circuit Applications


- So far we have used linear passive elements in conjunction with the op-amp. Many useful circuits can be fabricated if nonlinear elements, such as diodes or transistors are used in the op-amp circuits. We will consider the following circuits:
 - Precision Half-Wave Rectifier
 - Log Amplifier
 - Antilog or Exponential Amplifier

Precision Half Wave Rectifier

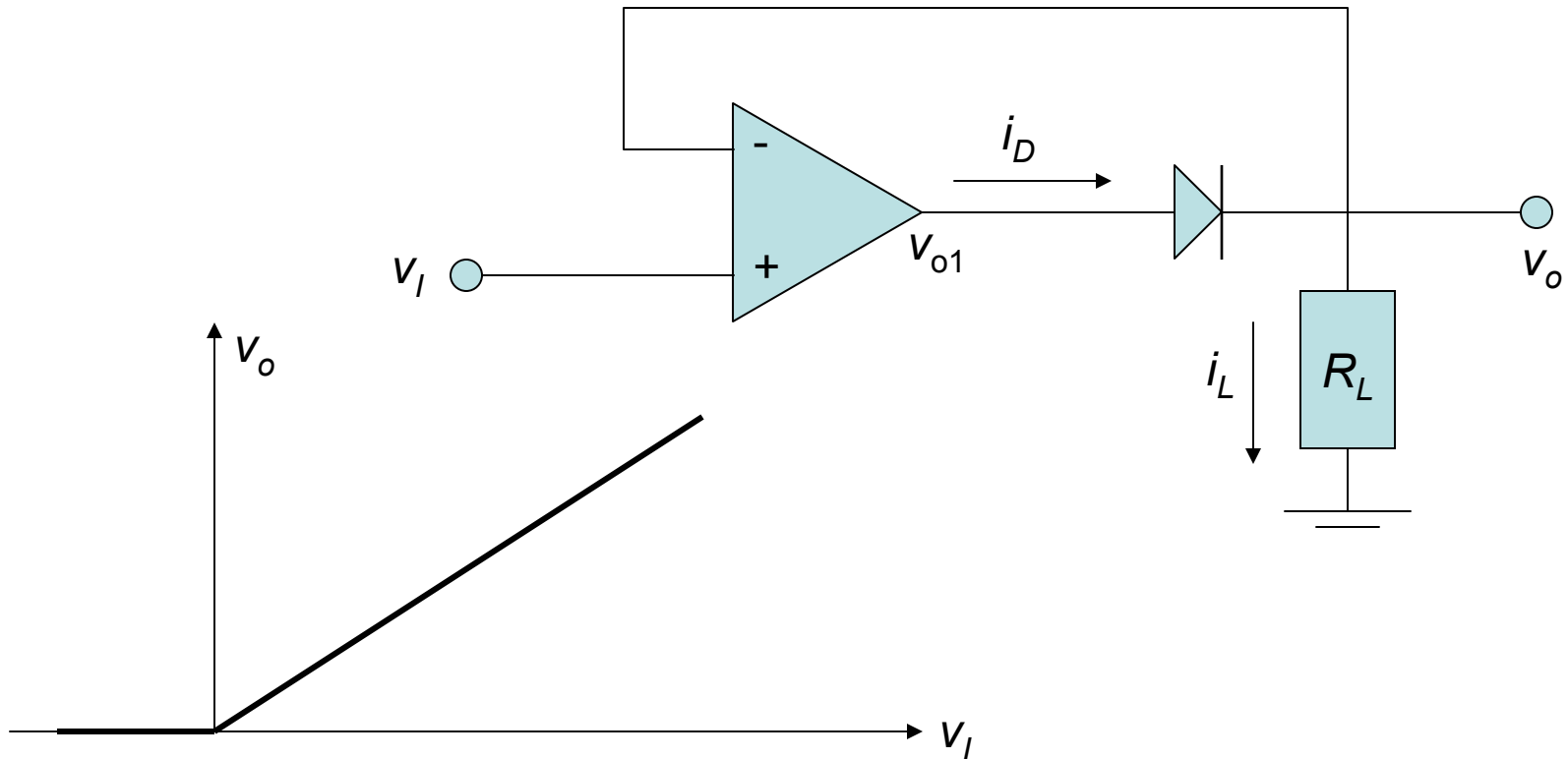For $v_I > 0$, the circuit behaves as voltage follower ($v_O = v_I$) and the load current i_L is positive. For $v_I < 0$, v_O tends to be negative which tends to produce negative diode current which cannot exist.



Log Amplifier

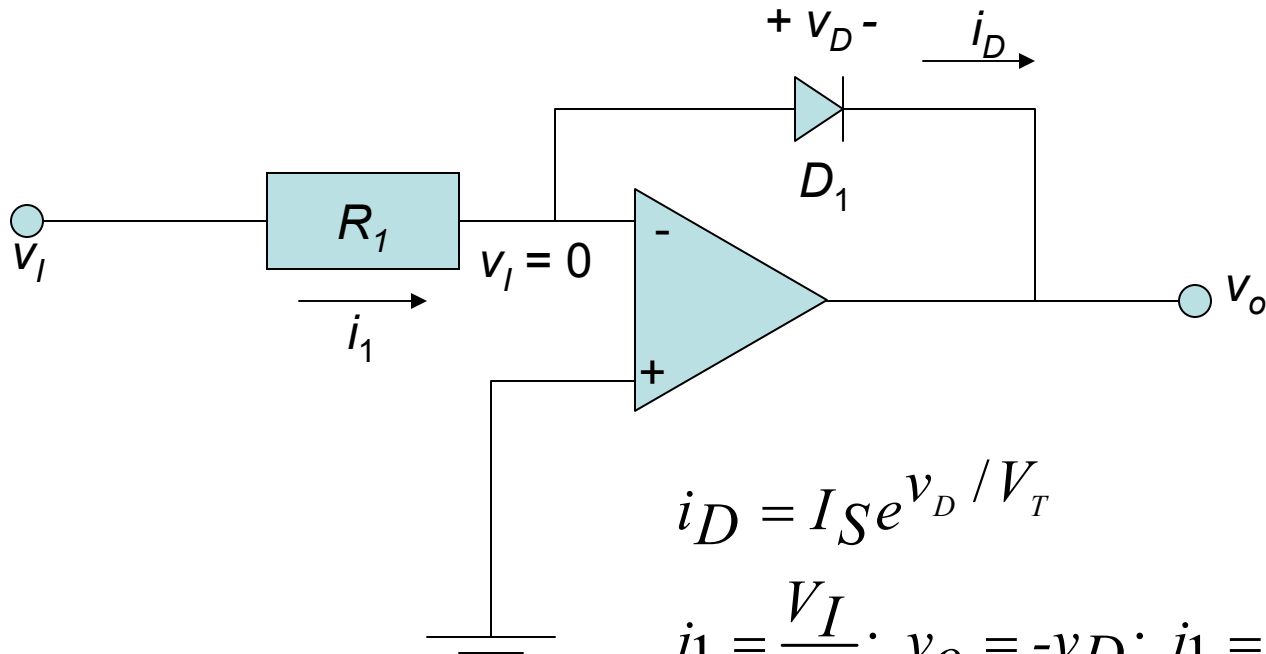


$$i_D = I_S e^{v_D / V_T}$$

$$i_1 = \frac{V_I}{R_1}; \quad v_o = -v_D; \quad i_1 = i_D$$

$$i_1 = \frac{v_I}{R_1} = i_D = I_S e^{-v_o / V_T}$$

$$\ln\left(\frac{v_I}{I_S R_1}\right) = -\frac{v_o}{V_T}; \quad v_o = -V_T \ln\left(\frac{V_I}{I_S R_1}\right)$$

Antilog or Exponential Amplifier

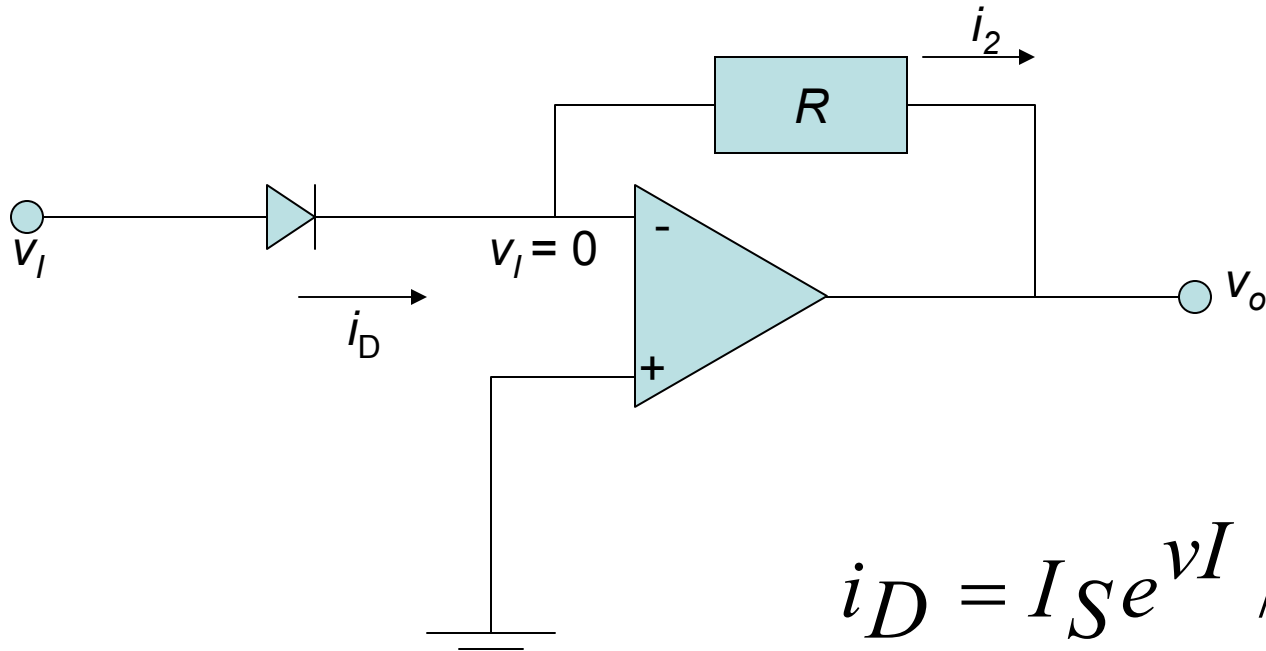


$$i_D = I_S e^{v_I / V_T}$$

$$v_O = -i_2 R = -i_D R$$

$$v_O = -I_S R e^{v_I / V_T}$$

Summing OP-Amp Circuit Design

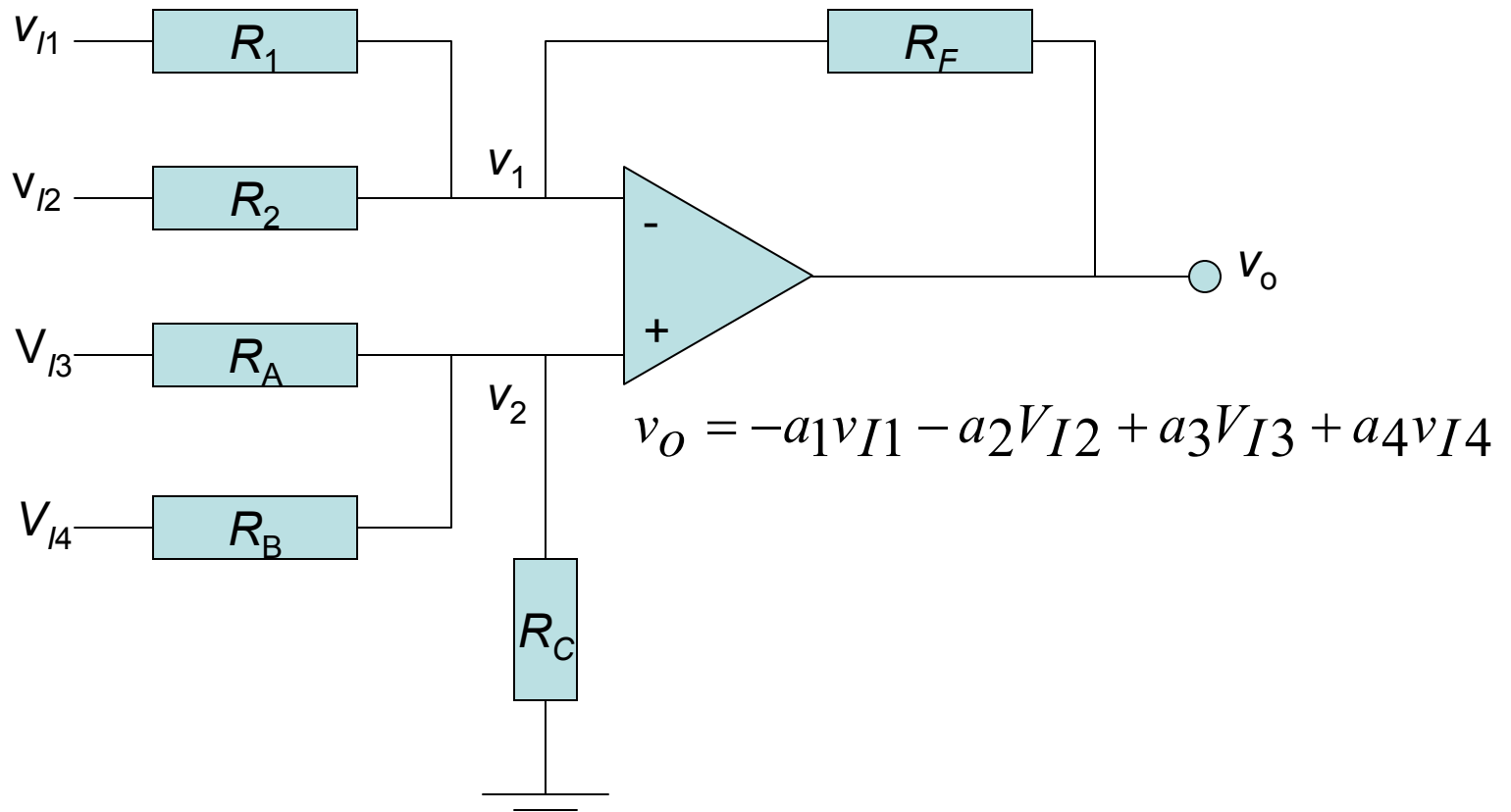

$$v_o(v_{I1}) = -\frac{R_F}{R_1} v_{I1}; \quad v_o(v_{I2}) = -\frac{R_F}{R_2} v_{I2}$$

$$v_2(V_{I3}) = \frac{R_B // R_C}{R_A + R_B // R_C} v_{I3} = v_1(V_{I3})$$

$$v_o(V_{I3}) = \left(1 + \frac{R_F}{R_1 // R_2}\right) v_1(V_{I3}) = \left(1 + \frac{R_F}{R_1 // R_2}\right) \left(\frac{R_B // R_C}{R_A + R_B // R_C}\right) v_{I3}$$

$$v_o(V_{I3}) = \left(1 + \frac{R_F}{R_N}\right) \left(\frac{R_P}{R_A}\right) v_{I3}; \quad R_N = R_1 // R_2; \quad R_P = R_A // R_B // R_C$$

$$v_o(V_{I4}) = \left(1 + \frac{R_F}{R_N}\right) \left(\frac{R_P}{R_A}\right) v_{I4}$$

$$v_o = -\frac{R_F}{R_1} v_{I1} - \frac{R_F}{R_2} v_{I2} + \left(1 + \frac{R_F}{R_N}\right) \left[\frac{R_P}{R_A} v_{I3} + \frac{R_P}{R_B} v_{I4} \right]$$

Design Example: Design a summing op-amp that produces the following equation. The smallest resistor should be 20 k Ω

$$v_O = -10v_{I1} - 4v_{I2} + 5v_{I3} + 2v_{I4}$$

$$\frac{R_F}{R_1} = 10; \frac{R_F}{R_2} = 4; \text{ Choose } R_1 = 20 \text{ k}\Omega$$

$$R_F = 200 \text{ k}\Omega; R_2 = 50 \text{ k}\Omega$$

$$\left(1 + \frac{R_F}{R_1 // R_2}\right) = \left(1 + \frac{200}{20 // 50}\right) = 15$$

$$(15)\left(\frac{R_P}{R_A}\right) = 5; 15\left(\frac{R_P}{R_B}\right) = 2; \frac{R_B}{R_A} = \frac{5}{2}$$

If we choose $R_A = 80 \text{ k}\Omega$, then $R_B = 200 \text{ k}\Omega$,

$$R_P = 26.67 \text{ k}\Omega, R_C = 50 \text{ k}\Omega$$

Reference Voltage Source Gain

