 


ELG4139: Rectifiers and Controlled Rectifiers

AC to DC Converters




	Half-wave	Centre-tap	Bridge type
No. of diode	1	2	4
Transformer necessary	No	Yes	No
Maximum efficiency	40.6%	81.2%	81.2%


Linear Rectifier

Consist of:

 
- Transformer: steps ac voltage up or down.
- Rectifier Diodes: change ac to “bumpy” dc.
- Filter Network: includes capacitors and inductors, smooths out the bumps.
- Voltage Regulator: keeps the voltage constant.
- Protection: usually a zener diode circuit.




Example: Computer Power Supply

 

Example: Adjustable Motor Speed Drive

 

 Power Supply Specifics: Half Wave Rectifier




Source: ARRL


Half-Wave Rectifier

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

 Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Simple half-wave rectifier

 


High ripple factor.

Low rectification efficiency.

 

Same arrangement with freewheeling diode

 


Low transformer utilization factor.

Power Supply Specifics

Full Wave Center-Tapped Rectifier


FULL WAVE CENTER-TAPPED RECTIFIER

 (Electrons flow during both halves of the cycle)



Source: ARRL

Power Supply: Full Wave Bridge Rectifier

 





Source: ARRL

Filtering

Capacitors are used in power supply filter networks. The capacitors smooth out the rippled AC to DC.

HALF WAVE RECTIFIER

EFFECTS OF ADDING A FILTER CAPACITOR

    

Source: ARRL

Rectifier Performance Parameters

$$\eta = P_{dc} / P_{ac} \quad \text{Rectification Efficiency}$$

$$V_{ac} = \sqrt{V_{rms}^2 - V_{dc}^2} \quad P_{ac} = V_{rms} I_{rms}$$

$$FF = V_{rms} / V_{dc} \quad \text{Form Factor}$$

$$\text{Ripple factor} \quad RF = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \sqrt{\frac{V_{rms}^2}{V_{dc}^2} - 1} = \sqrt{FF^2 - 1}$$

Example 1: A half-wave rectifier has a pure resistive load of R . Determine (a) The efficiency, (b) Form factor (c) Ripple factor.

$$V_{dc} = \frac{1}{2\pi} \int_0^{\pi} V_m \sin(\omega t) d\omega t = \frac{V_m}{2\pi} (-\cos\pi - \cos(0)) = \frac{V_m}{\pi} \quad I_{dc} = \frac{V_{dc}}{R} = \frac{V_m}{\pi R}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin \omega t)^2} = \frac{V_m}{2} \quad I_{rms} = \frac{V_m}{2R}$$


$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc} * I_{dc}}{V_{rms} * I_{rms}} = \frac{\frac{V_m}{\pi} * \frac{V_m}{\pi R}}{\frac{V_m}{2} * \frac{V_m}{2R}} = 40.53\%$$

$$FF = \frac{V_{rms}}{V_{dc}} = \frac{\frac{V_m}{2}}{\frac{V_m}{\pi}} = \frac{\pi}{2} = 1.57$$

$$RF = \frac{V_{ac}}{V_{dc}} = \sqrt{FF^2 - 1} = \sqrt{1.57^2 - 1} = 1.211$$


Three-Phase Diode Bridge Rectifier

 Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.





Waveforms and Conduction Times of Three-Phase Bridge Rectifier

 Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Three-Phase Full-Wave Rectifier

  

Example 2: A single-phase diode bridge rectifier has a purely resistive load of $R=15$ ohms and, $V_S=300 \sin 314 t$ and unity transformer ratio. Determine (a) The efficiency, (b) Form factor, (c) Ripple factor, (d) and, (d) Input power factor.

$$V_{dc} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t = \frac{2V_m}{\pi} = 190.956 \, V \quad I_{dc} = \frac{2V_m}{\pi R} = 12.7324 \, A$$

$$V_{rms} = \left[\frac{1}{\pi} \int_0^{\pi} (V_m \sin \omega t)^2 \, d\omega t \right]^{1/2} = \frac{V_m}{\sqrt{2}} = 212.132 \, V$$


$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc} I_{dc}}{V_{rms} I_{rms}} = 81.06 \, \% \quad FF = \frac{V_{rms}}{V_{dc}} = 1.11$$

$$RF = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \sqrt{\frac{V_{rms}^2}{V_{dc}^2} - 1} = \sqrt{FF^2 - 1} = 0.482$$

$$\text{Input power factor} = \frac{\text{Real Power}}{\text{Apperant Power}} = \frac{V_S I_S \cos \phi}{V_S I_S} = 1$$




Alternative! Controlled Switching Mode

 - By using linear regulator, the AC to DC converter is not efficient and of large size and weight!
- Using Switching-Mode
- High efficiency
- Small size and light weight
- For high power (density) applications.
- **Use Power Electronics!**




Thyristors and Controlled Rectifiers

   Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display. Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.





 Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Controlled Rectifier Circuit

  Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display. Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$V_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_p \sin \omega t d\omega t = \frac{V_p}{2\pi} (1 + \cos \alpha)$$

$$V_{rms} = \left[\frac{1}{2\pi} \int_{\alpha}^{\pi} V_p^2 \sin^2 \omega t d\omega t \right]^{1/2}$$


$$= \frac{V_p}{2} \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}$$

 Example: Consider the following SCR-based variable voltage supply. For $R_L=240\ \Omega$, derive the RMS value of the load voltage as a function of the firing angle, and then calculate the load power when the firing angle α is 0 , $\pi/2$, and π .


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



 
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



 Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Full-Wave Rectifiers Using SCR

 

$$V_{dc} = \frac{2}{2\pi} \int_{\alpha}^{\pi+\alpha} V_p \sin \omega t d\omega t = \frac{2V_p}{\pi} (\cos \alpha)$$

$$V_{rms} = \left[\frac{2}{2\pi} \int_{\alpha}^{\pi+\alpha} V_p^2 \sin^2 \omega t d\omega t \right]^{1/2}$$

$$= \frac{V_p}{\sqrt{2}} = V_s$$

With a purely resistive load, SCRs S_1 and S_2 can conduct from α to π , and SCRs S_3 and S_4 can conduct from $\alpha+\pi$ to 2π .