

## ELG4139 Lab 1: Operational Amplifier Characteristics

**Objectives:** To study the characteristics of a voltage follower.

### Case 1: Voltage Follower (Multisim and Hands-on)

1. Calculate  $v_{out}$  with the switch open (no load) and with the switch closed ( $500\ \Omega$ ) for the following circuit.
2. Repeat the calculation using a voltage follower as a buffer between the voltage divider and the  $500\ \Omega$ .
3. Build the circuit and repeat 1 and 2.
4. What effect does the simulation predict if you lower the load to  $4\ \Omega$ ?
5. What happens with a  $500\ \Omega$  load at  $1\ \text{MHz}$ ? Explain

