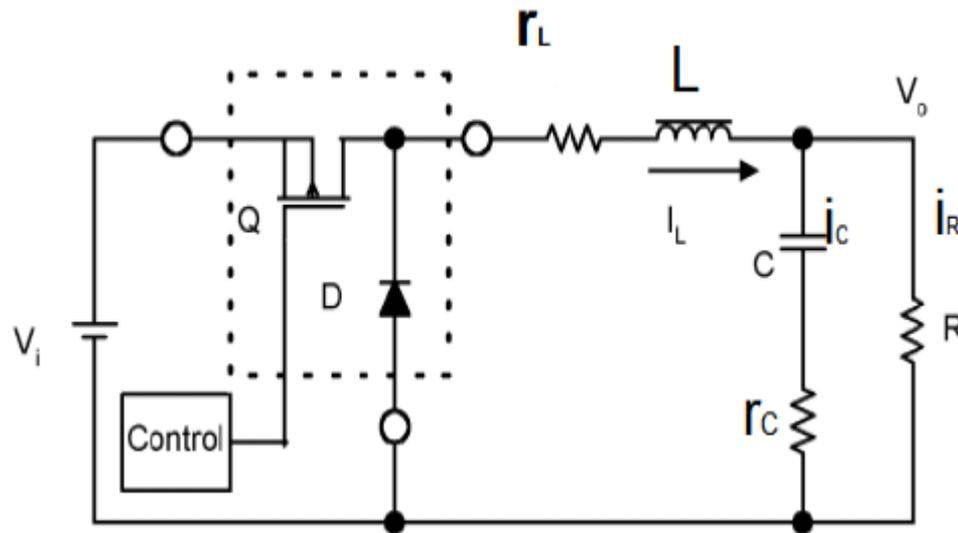


ELG4156


State Space Averaging of DC to DC Converters



Introduction

- A few applications of interest of DC-DC converters are where 5V DC on a personal computer motherboard must be stepped down to 3V, 2V or less for one of the latest CPU chips.
- DC to DC converters are widely used in hybrid cars which is our main focus to alter DC energy from a particular level to other with minimum loss.
- The need for converters is in demand due to the fact that transformers are unable to operate on DC.
- A converter is not producing power. Whatever comes at the output has to come only from input. Efficiency cannot be made equal to 100%.

Buck Converter

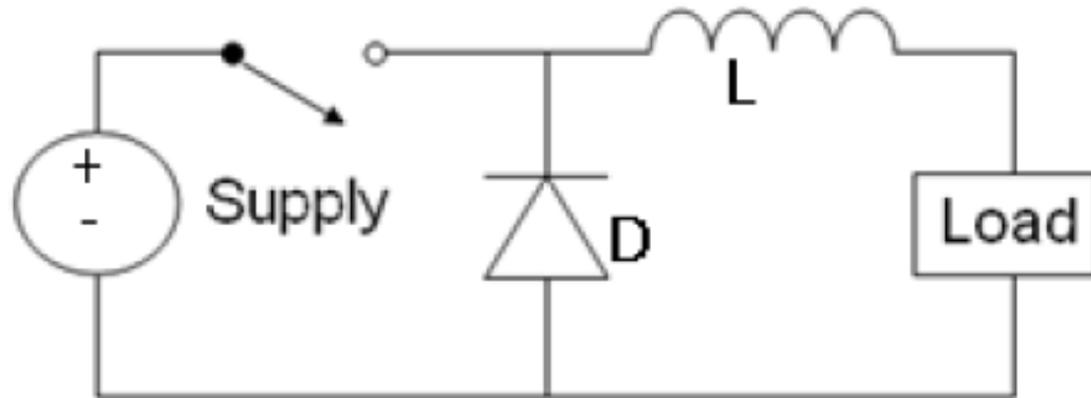

When the switch is closed, the voltage across the inductor is $V_L = V_i - V_o$. The current through inductor linearly rises. The diode does not allow current to flow through it, since it is reverse-biased by voltage V .

For Off state, diode is forward biased and voltage is $V_L = -V_o$ across inductor. The inductor current which was rising in ON case, now decreases.

Buck Modes of Operation

$d_1 T_S = \text{ON Period time}$


$d_2 T_S = \text{OFF Period time}$

$T_S = \text{Total time period for one cycle}$

$i_{pk} = \text{peak value of inductor current after ON period}$


$\bar{i}_L = \text{Average value of current}$

$V_{in} = \text{input voltage}$

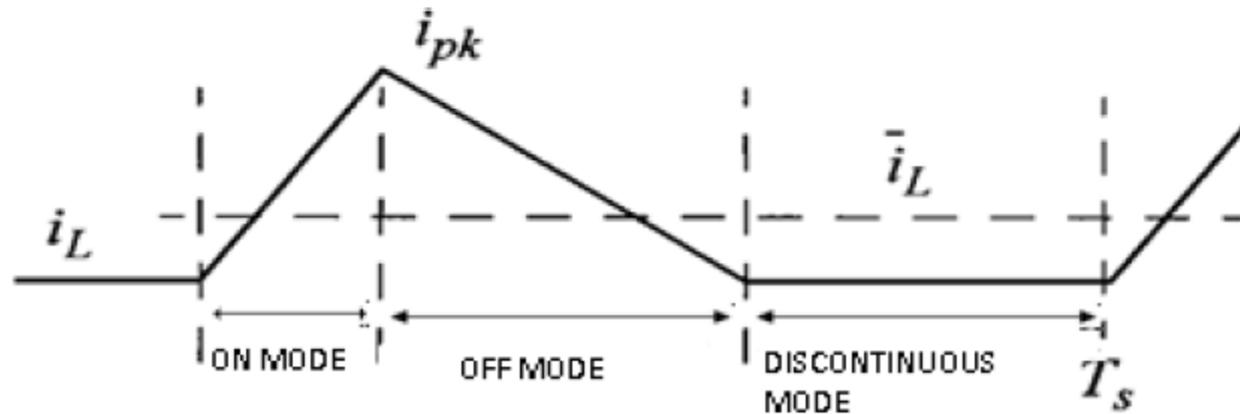

Buck Converter During ON Mode

Write the State Space Model

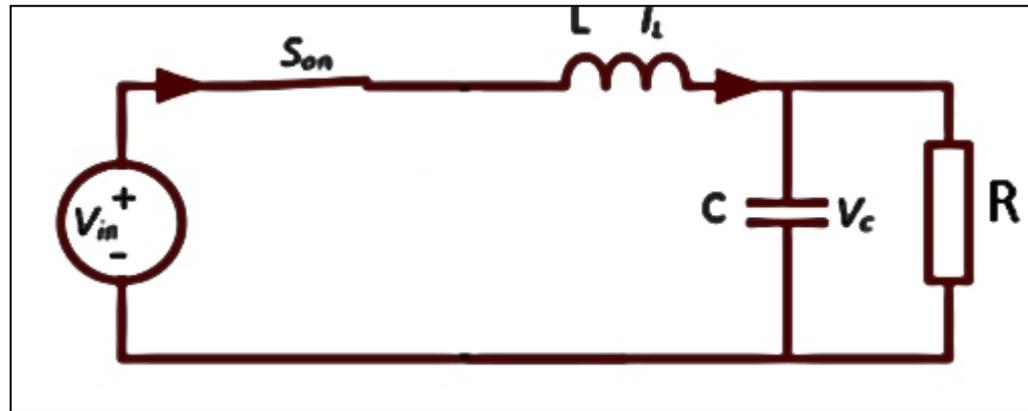

From KVL $v_{in} - L \frac{di_L}{dt} - v_C = 0$


From KCL $\frac{v_C}{R} + C \frac{dv_C}{dt} - i_L = 0$

Write

$$- \begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{bmatrix} = \begin{bmatrix} \cdot \\ \cdot \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} \cdot \\ \cdot \end{bmatrix} v_{in} ; V_o = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

Buck Converter During Off Mode

Write State Space Model

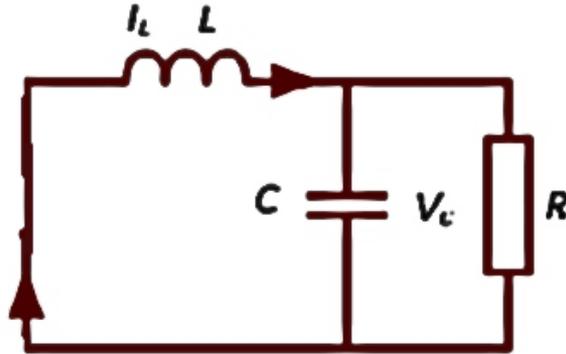

From KVL $v_C + L \frac{di_L}{dt} = 0$

From KCL $i_L - \frac{v_C}{R} - C \frac{dv_C}{dt} = 0$

Write


$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{bmatrix} = \begin{bmatrix} 0 \\ -\frac{1}{R} - \frac{1}{L} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} v_{in} ; V_o = [0 \quad 1] \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

During Discontinuous Conduction Mode

$$\text{From KVL} \quad \frac{di_L}{dt} = 0$$

$$\text{From KCL} \quad \frac{v_C}{R} + C \frac{dv_C}{dt} = 0$$

Write

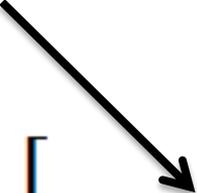
$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{bmatrix} = \begin{bmatrix} \quad \\ \quad \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} v_{in}; V_o = \begin{bmatrix} 0 & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

Buck Modelling Analysis

- Averaging
- Inductor current analysis
- Duty-ratio constraint.

State space averaging techniques are employed to get a set of equations that describe the system over one switching period.

$$\dot{\bar{X}} = [A_1 d_1 + A_2 d_2 + A_3(1 - d_1 - d_2)]\bar{X} + [B_1 d_1 + B_2 d_2 + B_3(1 - d_1 - d_2)]u$$

$$\bar{i}_L = \frac{i_{pk}}{2} \cdot (d_1 + d_2)$$

The Final Model

The state space averaged model for the above equation is

$$\frac{d}{dt} \begin{bmatrix} \bar{l}_L \\ \bar{v}_C \end{bmatrix} = \begin{bmatrix} \cdot \\ \cdot \end{bmatrix} \begin{bmatrix} \bar{l}_L \\ \bar{v}_C \end{bmatrix} + \begin{bmatrix} \frac{d_1}{L} \\ 0 \end{bmatrix} v_{in}$$



Write

$$\frac{d}{dt} \begin{bmatrix} \bar{l}_L \\ \bar{v}_C \end{bmatrix} = \begin{bmatrix} \cdot \\ \cdot \end{bmatrix} K \begin{bmatrix} \bar{l}_L \\ \bar{v}_C \end{bmatrix} + \begin{bmatrix} \frac{d_1}{L} \\ 0 \end{bmatrix} v_{in} \quad K = \begin{bmatrix} \frac{1}{d_1+d_2} & 0 \\ 0 & 1 \end{bmatrix}$$


$$\begin{bmatrix} \cdot \\ \cdot \end{bmatrix} \begin{bmatrix} \bar{l}_L \\ \bar{v}_C \end{bmatrix} + \begin{bmatrix} \frac{d_1}{L} \\ 0 \end{bmatrix} v_{in}$$

Boost Converter

Write the State Space Model

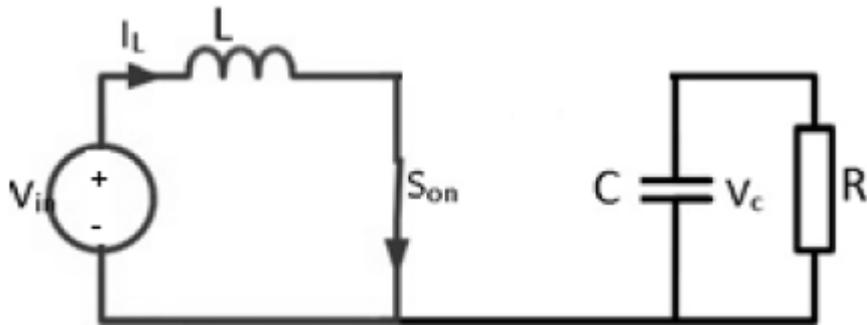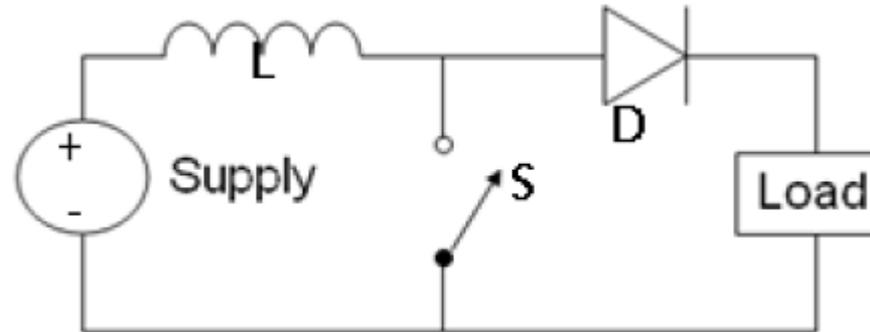

On

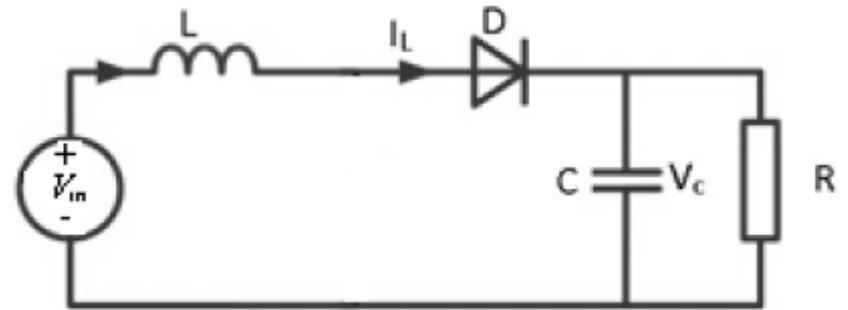

Off