


Switched Mode Power Supply (SMPS)

Control, Modeling, and Simulation

Why Use a Switching Regulator?



SMPS

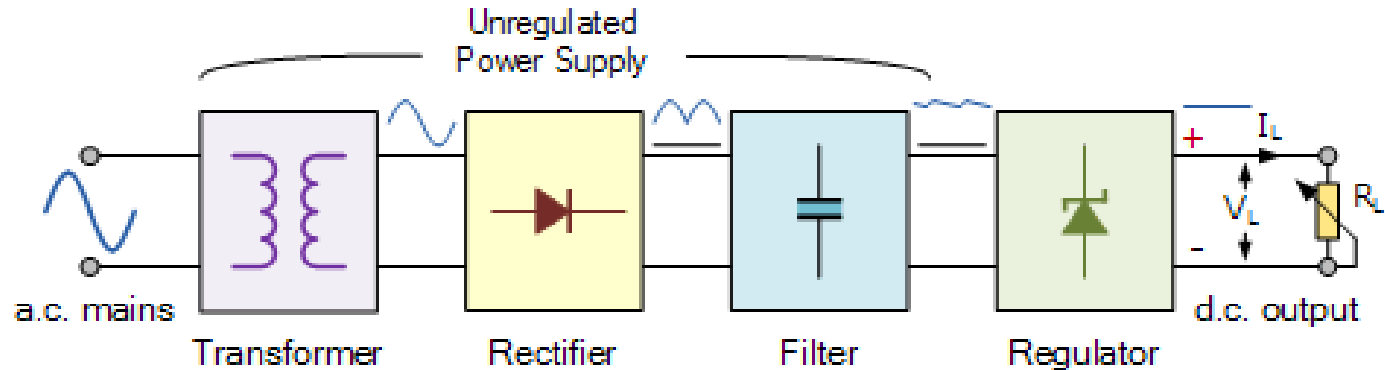



- Various types of voltage regulators, used in Linear Power Supplies (LPS), are dissipative regulator, as they have a voltage control element usually transistor or zener diode which dissipates power equal to the voltage difference between an unregulated input voltage and a fixed supply voltage multiplied by the current flowing through it.
- The switching regulator acts as a continuously variable power converter and hence its efficiency is negligibly. Hence the switching regulator is 'non-dissipative regulator'.
- In a SMPS, the active device that provides regulation is always operated in cut-off or in saturation mode.

Buck Switching Regulator



Maximum Duty Cycle: $D = \frac{V_{OUT}}{V_{IN(max)} \times \eta}$

$$L = \frac{V_{OUT} \times (V_{IN} - V_{OUT})}{\Delta I_L \times f_S \times V_{IN}}$$

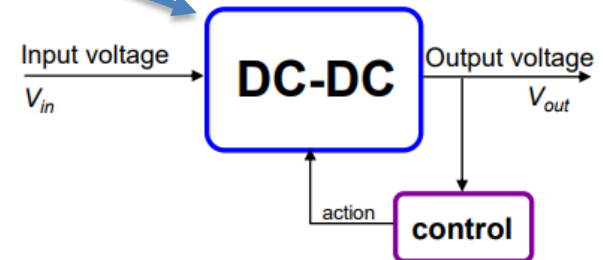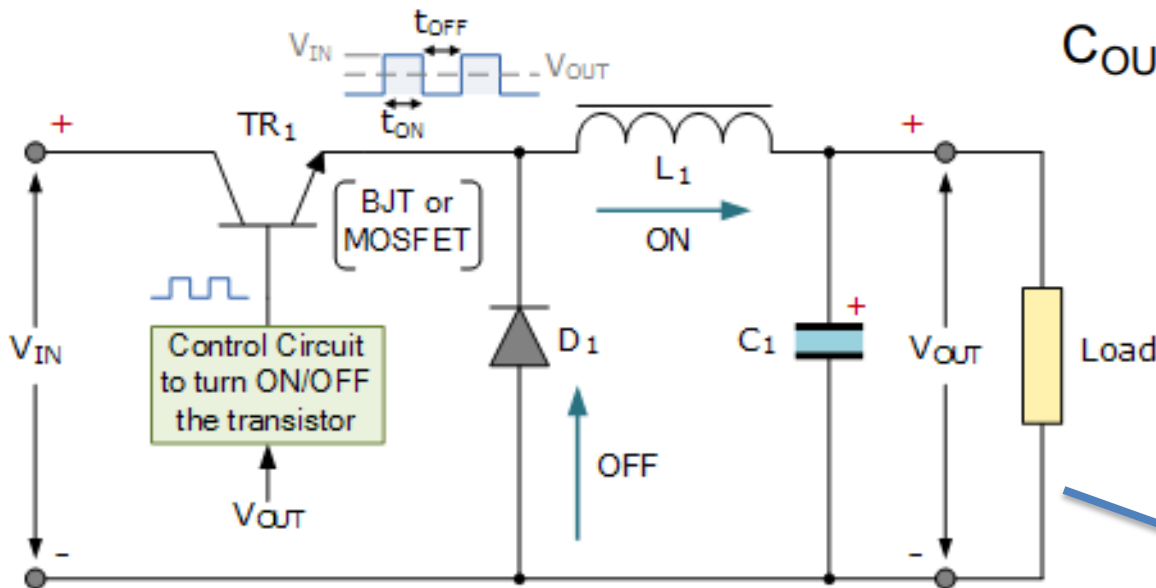
$$C_{OUT(min)} = \frac{\Delta I_L}{8 \times f_S \times \Delta V_{OUT}}$$




Control Design Using Pole Placement

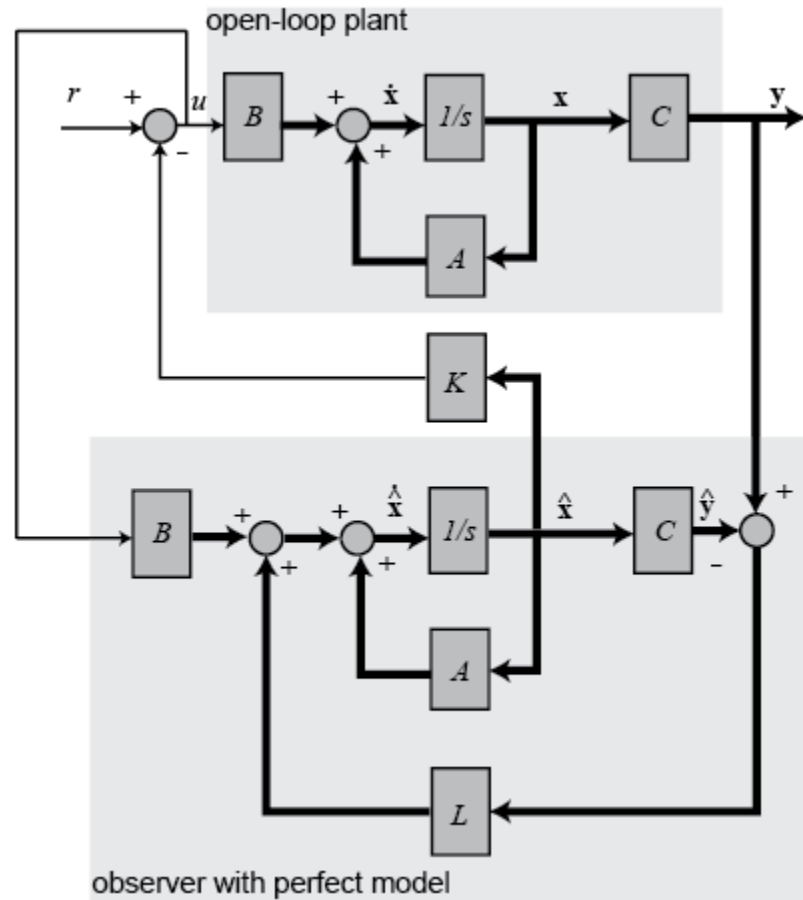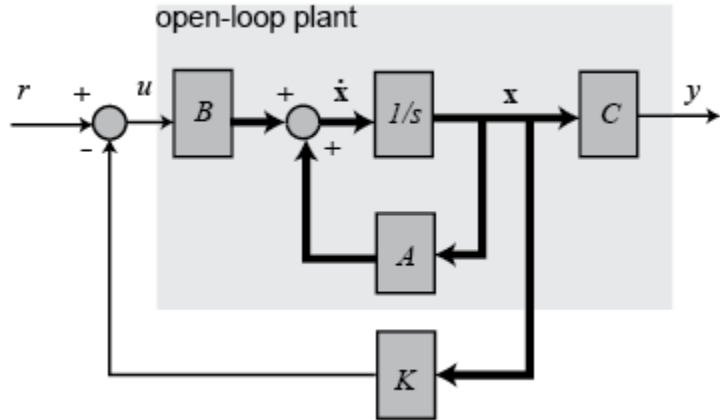

Voltage Mode Control of Buck Converter

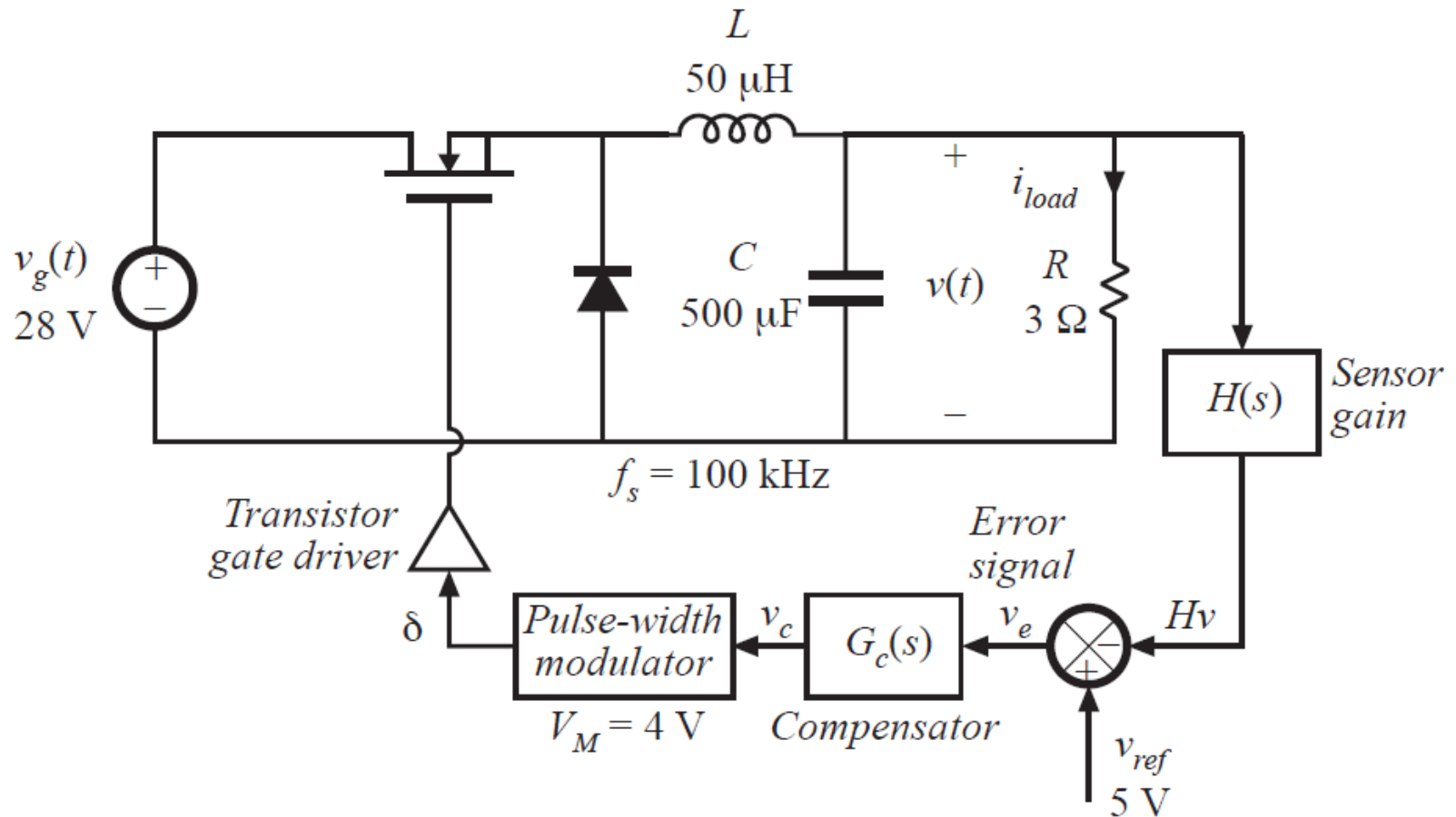

Current Mode Control of Buck Converter

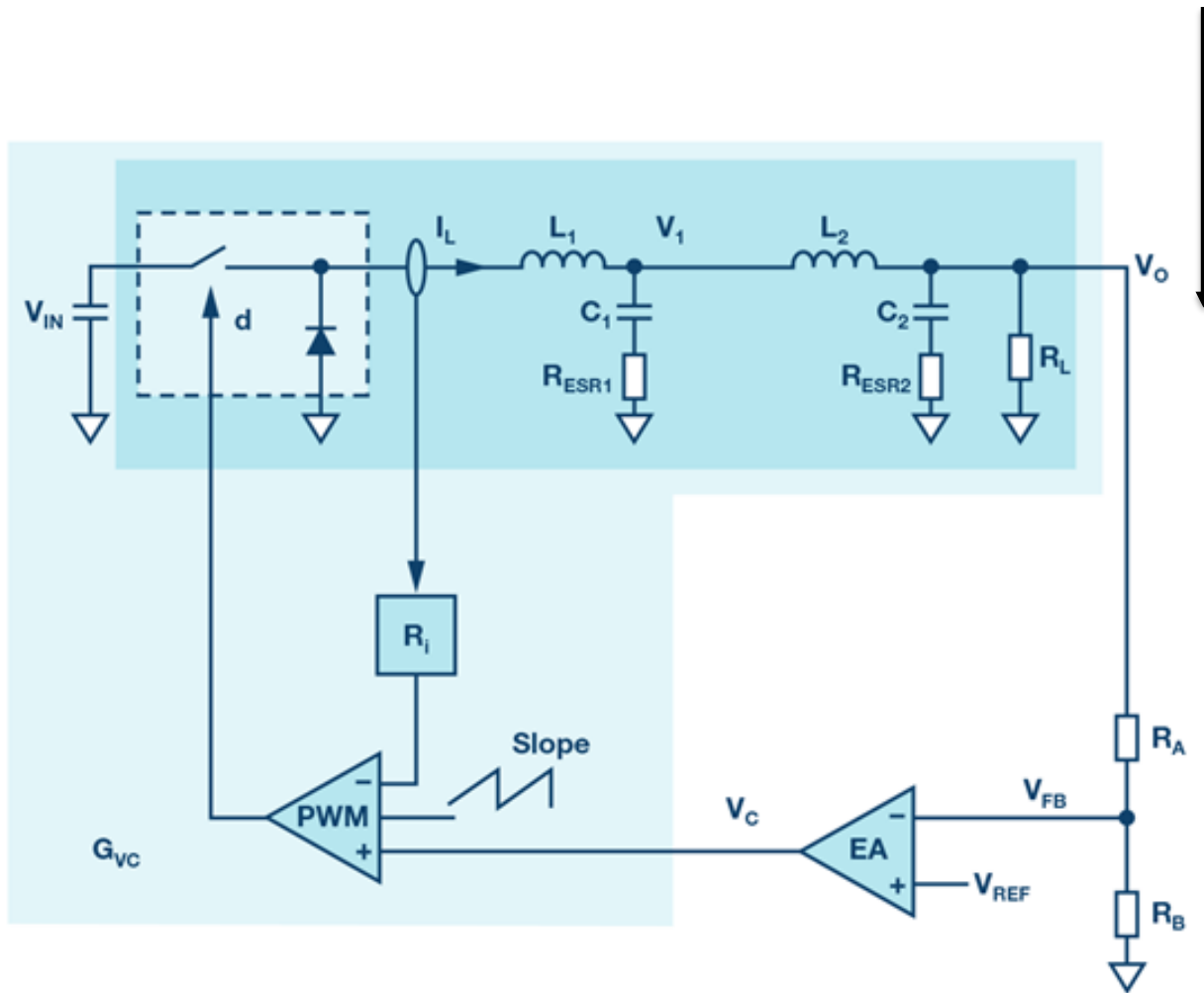


Boost SMPS


$$D = 1 - \frac{V_{IN(min)} \times \eta}{V_{OUT}}$$

$$L = \frac{V_{IN} \times (V_{OUT} - V_{IN})}{\Delta I_L \times f_S \times V_{OUT}}$$
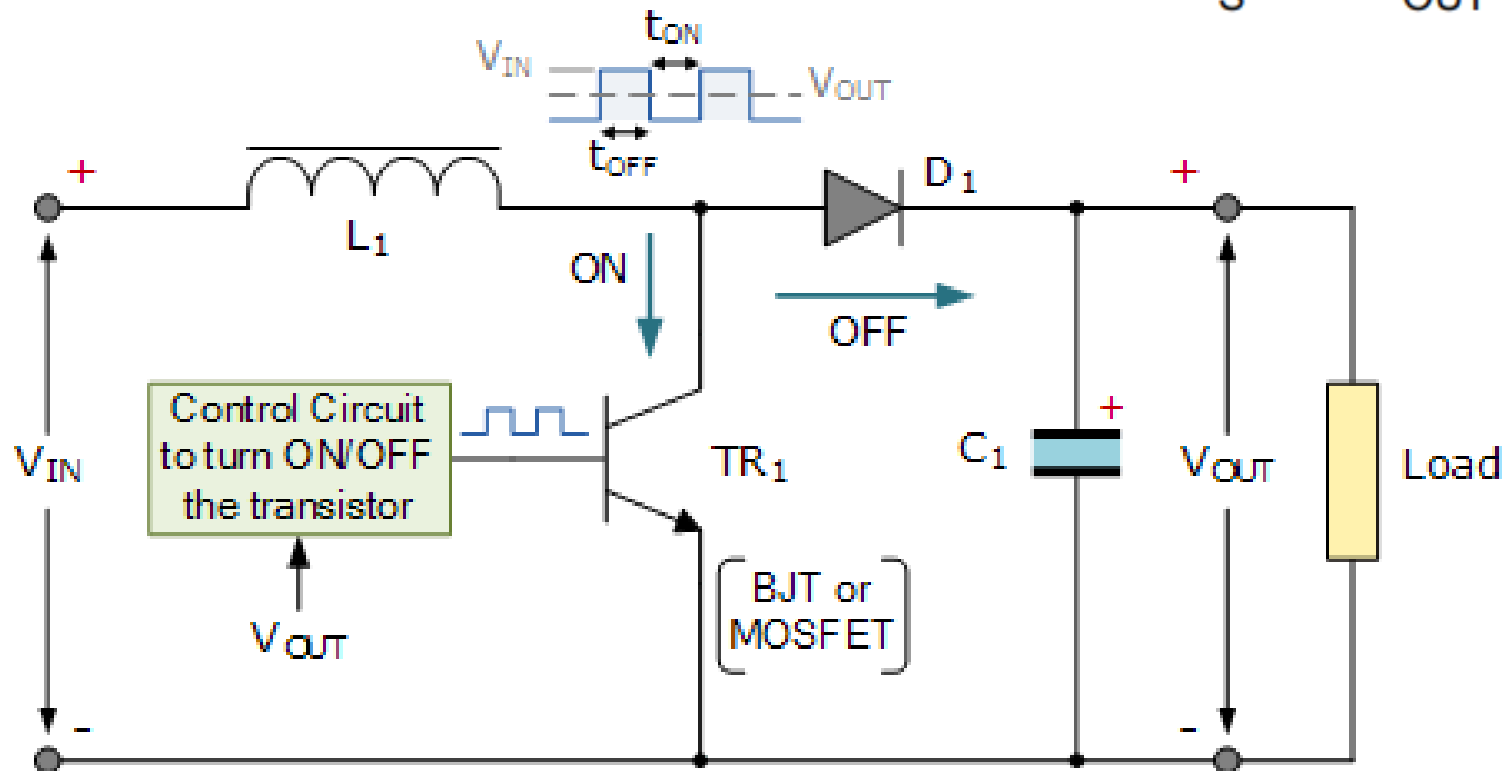
$$C_{OUT(min)} = \frac{I_{OUT(max)} \times D}{f_S \times \Delta V_{OUT}}$$



Feedback Control of Boost Converter

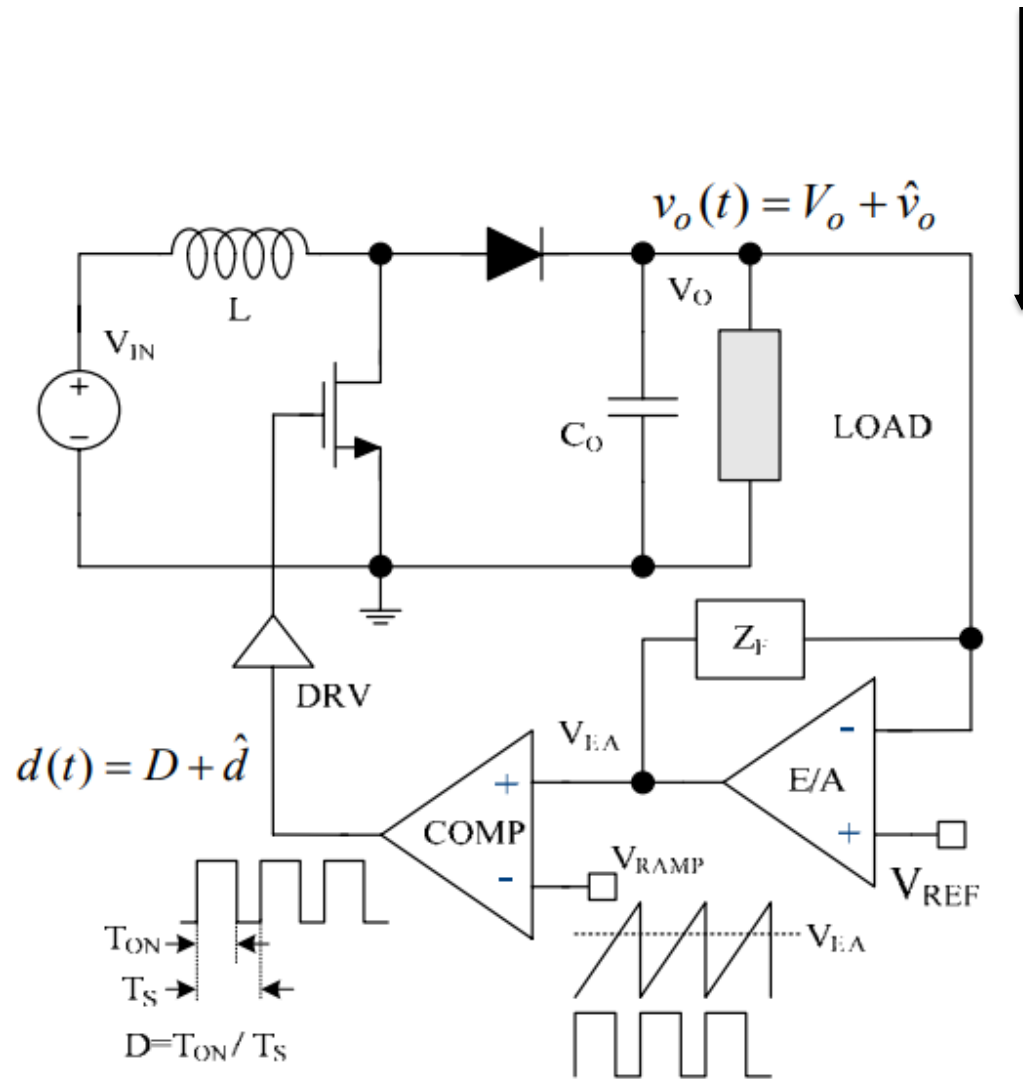

Buck Modes of Operation

$d_1 T_s = \text{ON Period time}$


$d_2 T_s = \text{OFF Period time}$

$T_s = \text{Total time period for one cycle}$

$i_{pk} = \text{peak value of inductor current after ON period}$

$\bar{i}_L = \text{Average value of current}$

$V_{in} = \text{input voltage}$

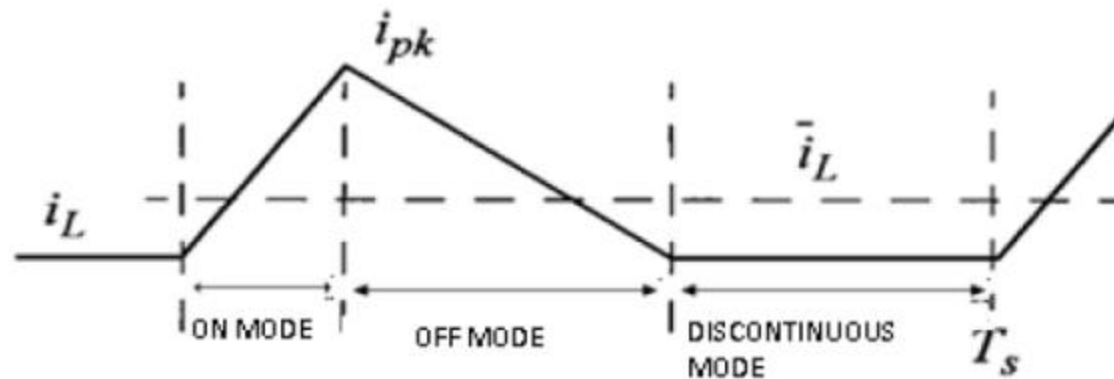


State Space Modeling

- If the system is linear, then the derivatives of the state variables are expressed as linear combinations of the system independent inputs and state variables themselves.
- The physical state variables of a system are usually associated with the storage of energy.
- For a typical converter circuit, the physical state variables are the inductor currents and capacitor voltages.

Buck Converter During ON Mode

Write the State Space Model

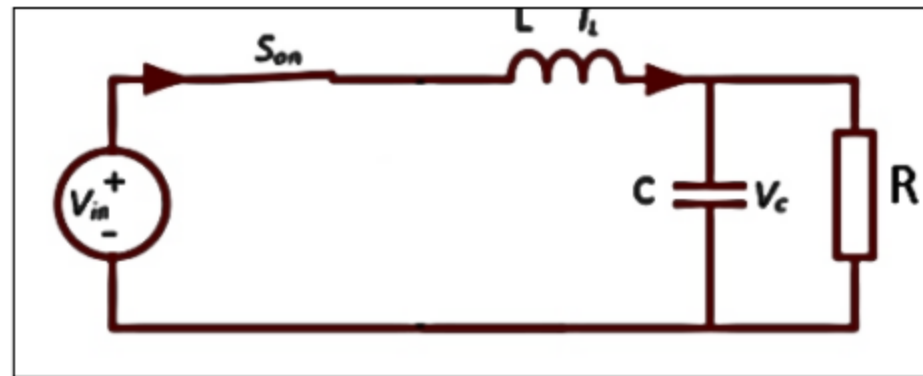


From KVL $v_{in} - L \frac{di_L}{dt} - v_C = 0$

From KCL $\frac{v_C}{R} + C \frac{dv_C}{dt} - i_L = 0$

Write

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{bmatrix} = \begin{bmatrix} 0 \\ -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} v_{in} ; v_o = [0 \quad 1] \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

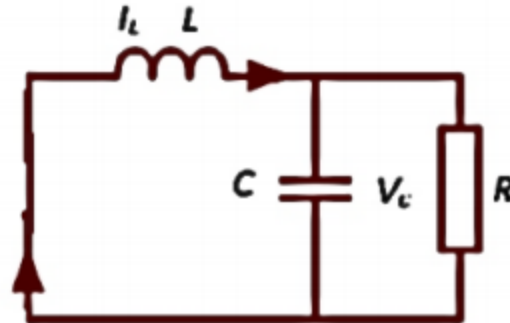Buck Converter During Off Mode Write State Space Model



From KVL $v_C + L \frac{di_L}{dt} = 0$

From KCL $i_L - \frac{v_C}{R} - \frac{Cdv_C}{dt} = 0$

Write

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{1}{L} \\ \frac{1}{C} - \frac{1}{R} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} v_{in}; V_o = [0 \quad 1] \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

During Discontinuous Conduction Mode

$$\text{From KVL} \quad \frac{di_L}{dt} = 0$$

$$\text{From KCL} \quad \frac{v_C}{R} + C \frac{dv_C}{dt} = 0$$

Write

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{bmatrix} = \begin{bmatrix} \quad \\ \quad \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} v_{in} ; V_o = \begin{bmatrix} 0 & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

Buck Modelling Analysis

- Averaging
- Inductor current analysis
- Duty-ratio constraint.

State space averaging techniques are employed to get a set of equations that describe the system over one switching period.

$$\dot{\bar{X}} = [A_1 d_1 + A_2 d_2 + A_3(1 - d_1 - d_2)]\bar{X} + [B_1 d_1 + B_2 d_2 + B_3(1 - d_1 - d_2)]u$$

$$\bar{i}_L = \frac{i_{pk}}{2} \cdot (d_1 + d_2)$$

The Final Model

The state space averaged model for the above equation is

$$\frac{d}{dt} \begin{bmatrix} \bar{l}_L \\ \bar{v}_C \end{bmatrix} = \begin{bmatrix} \cdot \\ \cdot \end{bmatrix} \begin{bmatrix} \bar{l}_L \\ \bar{v}_C \end{bmatrix} + \begin{bmatrix} \frac{d_1}{L} \\ 0 \end{bmatrix} v_{in}$$

Write

$$\frac{d}{dt} \begin{bmatrix} \bar{l}_L \\ \bar{v}_C \end{bmatrix} = \begin{bmatrix} \cdot \\ \cdot \end{bmatrix} K \begin{bmatrix} \bar{l}_L \\ \bar{v}_C \end{bmatrix} + \begin{bmatrix} \frac{d_1}{L} \\ 0 \end{bmatrix} v_{in} \quad K = \begin{bmatrix} \frac{1}{d_1+d_2} & 0 \\ 0 & 1 \end{bmatrix}$$

$$\begin{bmatrix} \cdot \\ \cdot \end{bmatrix} \begin{bmatrix} \bar{l}_L \\ \bar{v}_C \end{bmatrix} + \begin{bmatrix} \frac{d_1}{L} \\ 0 \end{bmatrix} v_{in}$$